

## Bilinear Filtering

Recall that the blend equation was:

$$C_{new} = C_a * f + C_b * (1-f)$$

Where  $C_a$ ,  $C_b$  were two 8-bit colors, and  $C_{new}$  was a blend of these two colors using the blend factor 'f' (a 9-bit value).

A similar operation is performed when a texture is mapped onto an object in 3D graphics, except that 2 blend factors and four colors are used:

$$T_{new} = (1-v)*(1-u)*T_{00} + (1-v)*u*T_{01} + v*(1-u)*T_{10} + u*v*T_{11}$$

$T_{00}$ ,  $T_{01}$ ,  $T_{10}$ ,  $T_{11}$  are 8-bit color values as before, with two 9-bit factors  $v$ ,  $u$  used to determine  $T_{new}$ .

9/30/2002

BR

1

## Bilinear Filtering (cont)

We will use 9-bits to represent  $u$ ,  $v$  as with the blend equation in order to represent 1.0 accurately.

Sample calculations:

$$u=1.0, v=1.0, \text{ then } T_{new} = T_{11}$$

$$u=0.0, v=1.0, \text{ then } T_{new} = T_{10}$$

$$u=1.0, v=0.0, \text{ then } T_{new} = T_{01}$$

$$u=0.0, v=0.0, \text{ then } T_{new} = T_{00}$$

$$u = 0.5, v=0.5 \text{ then}$$

$$T_{new} = 0.25*T_{00} + 0.25*T_{01} + 0.25*T_{10} + 0.25*T_{11}$$

9/30/2002

BR

2

## The Problem


- Implement a datapath + FSM that computes 8  $T_{new}$  values from 32  $T_{xx}$  values stored in a RAM for fixed values of  $u$ ,  $v$ .
- Will use a minimum resource approach – only 1 multiplier, 1 adder.
  - Note that 8 multiplies and 3 adds are required to implement the bilinear filter equation
- You will be provided with a datapath
  - You must schedule the operations on the datapath
  - Write an ASM chart that implements the schedule
  - Implement the FSM for the datapath and test your design

9/30/2002

BR

3

## Datapath for Bilinear Filter

 

9/30/2002

BR

4

## How to Compute $T_{new}$ ?


- The Sync RAM holds the values for  $T_{xx}$ 
  - Each calculation of  $T_{new}$  requires 4 values from the Sync Ram
  - Each 4-tuple stored in order of  $T_{00}$ ,  $T_{01}$ ,  $T_{10}$ ,  $T_{11}$
  - Sync Ram has 32 locations, so 8  $T_{new}$  calculations
- Each calculation of  $T_{xx} * u|1-u * v|1-v$  requires:
  - 1<sup>st</sup> multiply:  $T_{xx}$  (from Sync Ram) \*  $v|1-v$  (use 4/1 mux to select appropriate  $v$  or  $1-v$ ). Store result in *mult reg*.
  - 2<sup>nd</sup> multiply: compute *mult reg* \*  $u|1-u$ . Use the mult feedback path and mult muxes to select proper operands
- The saturating adder + accumulator register is used to accumulate the result.

9/30/2002

BR

5




 
## Step 1: $1-v * T_{00}$ (active paths shown in RED)



9/30/2002

BR

6

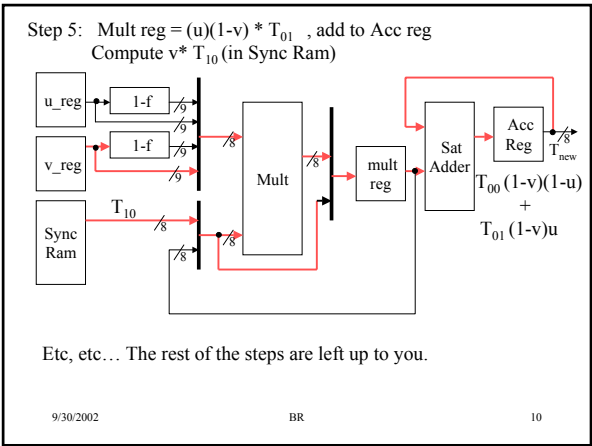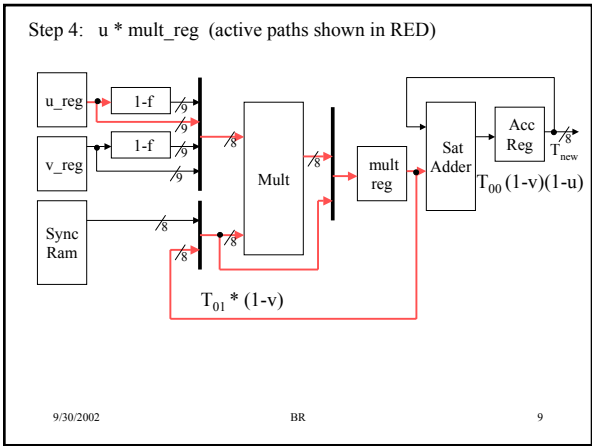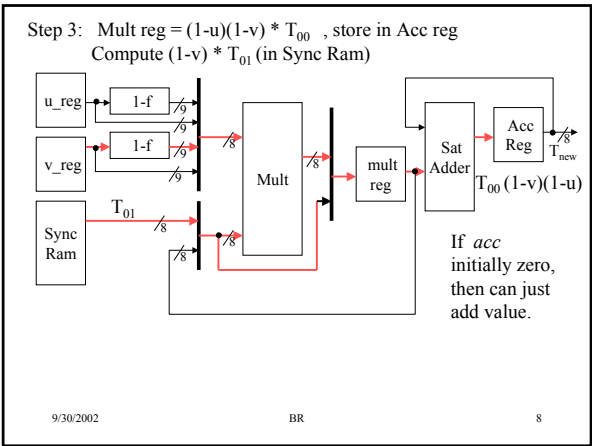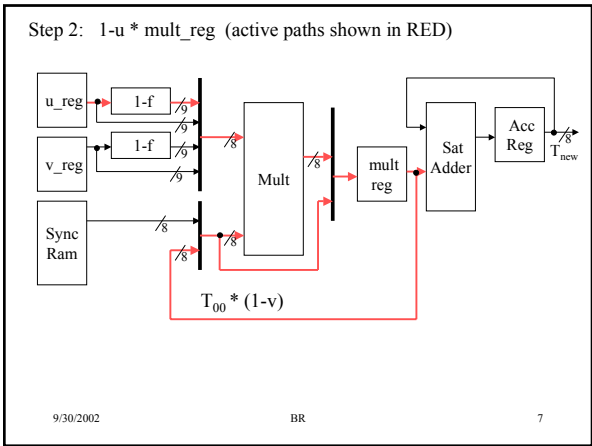

### Datapath - *bifilt.gdf*

- The ZIP archive contains a datapath (*bifilt.gdf*) that you can use.
  - Cannot change the interface signals (inputs/outputs) or their functionality
  - Cannot change number of multipliers (1) or satadds (1), or size of sync SRAM (32 locations)
  - Make any other changes that you want
- Your datapath + FSM has to compute 8 values of  $T_{\text{new}}$  in 100 clock cycles (this constraint is easy to meet)
  - If your number of clock cycles matches or is less than the number of clock cycles in the golden waveform, then you will get 10 points added to any test grade.
- You will have to add a FSM to *bifilt.gdf* to complete the functionality
  - The exact number of states and the sequencing of datapath operations is up to you.
  - You cannot use more than 16 states in your FSM.

9/30/2002 BR 11

### Datapath - *bifilt.gdf* Interface

- Inputs
  - clk, reset* : clock and asynchronous reset
  - addr[5..0]* : drives address bus to SRAM when datapath is not in operation
  - din[8..0]* : 9-bit input bus used to initialize *u\_reg*, *v\_reg*, SRAM contents
  - ld\_uv* : when asserted, then writing to *v\_reg* (addr0 = '0') or *u\_reg* (addr0 = '1')
  - we* : when asserted, writing to SRAM using *addr*, *din*. Assume only asserted if datapath is not in operation
  - start* : when asserted, start *bifilt* operation starting at SRAM location 0 and processing all 32 values in SRAM.
- SRAM, *u\_reg*, *v\_reg* are initialized externally to FSM control.

9/30/2002 BR 12

### Datapath - *bifilt.gdf* Interface (cont)

- Outputs
  - *busy* : asserted for duration of bifiltering operation
  - *o\_rdy* : asserted when *dout* bus contains *Tnew* value
  - *dout[7..0]* : 8-bit output bus for *Tnew* value
- It is very important that *o\_rdy* only be asserted when *dout* bus contains a valid value for *Tnew*.
- When *o\_rdy* is negated, the value *dout* is undefined
  - Will depend on your particular implementation

9/30/2002

BR

13

### Other Comments on *bifilt.gdf*

- The RAM is synchronous – registered Address, Control, Data
  - You cannot change this because external testbench expects this operation
- A counter is included in the datapath to drive the address lines during the bifiltering operation
- The golden waveform is *bifilt\_gold.scf*
  - Loads the SRAM with 32 values
  - Then tests all of the sample calculations shown on slide #2 plus one more

9/30/2002

BR

14

### Testing Your Design

- Cannot do a waveform compare against the golden waveform because you may have a different number of clock cycles
- The *tb\_bifilt.gdf* schematic and *tb\_bifilt.scf* is a testbench that can be used for checking.
- Includes a counter that will record the number of clock cycles that *busy* remains high during *bifilter* operation
- Includes an XOR-checksum that will checksum all values on *dout* when *o\_rdy* is asserted
  - you can use this as a quick check – if your checksum matches the golden checksum then your design is functional

9/30/2002

BR

15

### The Next Assignment

- This lab is worth 200 pts and is the first part of a 2-part series
- In the next part, you will be able to add more multipliers/satadders to reduce the number of clocks
  - Single SRAM is still a constraint
  - Interface does not change
  - You will have to change the datapath and your FSM
  - 2<sup>nd</sup> part is also worth 200 pts

9/30/2002

BR

16

### Due Dates

- Schedule:
  - Week 0 (Sept 30): Demo Lab #5, begin working on Lab #6, Part #1
  - Week 1 (Oct 7): Must have ASM chart ready for checkoff and FSM VHDL code written/compiled and debug in datapath in progress. Part #2 will be assigned at this time.
  - Week 2 (Oct 14): Complete checkoff for Part #1 at beginning of lab.
  - Week 3 (Oct 21): Must demo Part #2 at the beginning of the lab period. Begin work on Lab #7.
- You must attend lab session for entire time each week until Lab #6 (both parts) is completed.
  - If you have a laptop, bring it to the lab. If you work on a desktop at home, then ftp the files to ECE machines. If you do not show up for lab, or do not remain for the entire time you will lose 30% credit of the 400 total points.
- No late labs accepted for either parts #1 or #2.

9/30/2002

BR

17

### A Guaranteed Way to get a 0 for both labs and perhaps wreck your lab grade

- Don't do anything the first week.
- Show up for lab in week #1 not even having thought about the first part.
  - Now you have only 2 weeks to complete two tough labs
- In week #2, won't have first part working and understanding the first part is the key to performing the second part
  - You madly try to finish the 2<sup>nd</sup> part in week #3 but are clueless, so at the end of the 3 weeks you have 0/400 pts.
  - Total lab points for first 5 labs = 600 pts, so lab average is 600/1000 = 60% (assuming perfect scores on first 5 labs).
  - Remember that you must have at least a 60% on all out of class material to pass the course.

9/30/2002

BR

18