

Table A-20 strengths


| value | %v | drive0 | drive1 | Description |
|-------|----|---------|---------|------------------|
| 0 | Hi | highz0 | highz1 | High impedance |
| 1 | Sm | - | - | Small capacitor |
| 2 | Me | - | - | Medium capacitor |
| 3 | We | weak0 | weak1 | Weak drive |
| 4 | La | - | - | Large capacitor |
| 5 | Pu | pull0 | pull1 | Pull drive |
| 6 | St | strong0 | strong1 | Strong drive |
| 7 | Su | supply1 | supply0 | Supply drive |

Table A-21 Switch Strength Reduction

| Input Strength | Ideal Device Output Strength | Resistive Device Output Strength |
|----------------|------------------------------|----------------------------------|
| supply | strong | pull |
| strong | strong | pull |
| pull | pull | weak |
| weak | weak | medium |
| large | large | medium |
| medium | medium | small |
| small | small | small |
| high impedance | high impedance | high impedance |

Differential Logic

 
DCVSL – Differential Cascade Voltage Switch Logic



Both PDN networks are never conducting at same time

We can reduce transistor count by sharing transistors.

Xor gate with shared transistors

 


Can share the B transistor

HW Assignment

- Zip archive has verilog file *tb_xorgate_dcvs1.v*, *xorgate_dcvs1.v*
 - Tb_xorgate_dcvs1.v* is testbench for XOR gate
 - xorgate_dcvs1.v* has empty module named *xorgate_dcvs1*
- Complete switch level model of *xorgate_dcvs1*
 - Be careful of drive strengths.
 - A supply strength going through a pmos/nmos always comes out as strong strength.
 - A supply strength going through a rpmos/mmos comes out as pull strength


Supply strength

 

pmos

strong strength

Supply strength

 


rpmos

pull strength

Dual Edge Triggered Flip-Flop Model

- Write a Verilog transistor level model that simulates the DETFF on the next two pages
 - The DETFF consists of two modules which must be connected together
 - Zip archive has *detff.v* (fill this module in) and *tb_detff.v* (testbench).
 - There is also a link for a sample Makefile.
- In my model, I had to use delays at a couple of nodes in order to get the model to function correctly (there are solutions that do not require delays).
 - I also had to use strength reduction transistors in a couple of places
 - There are multiple correct solutions to this problem
 - You must understand how the DETFF works before trying to model it.

 Module A of Dual Edge Triggered Flip-Flop¹




| SIZE (w/l in microns) | |
|-----------------------|-------|
| M1 | 4/1.6 |
| M2 | 4/1.6 |
| M3 | 8/1.6 |
| M4 | 8/1.6 |
| M5 | 8/1.6 |
| M6 | 8/1.6 |
| M7 | 4/2.6 |
| M8 | 4/2.6 |
| M9 | 8/1.6 |
| M10 | 8/1.6 |

(a)

Transistor sizes give strength hints

¹A. Gago, "Reduced Implementation of D-Type DET Flip-Flops, IEEE Journal of Solid-State Circuits, Vol 28, No 3., March 1993

 Module B of Dual Edge Triggered Flip-Flop



| SIZE (w/l in microns) | |
|-----------------------|-------|
| M3 | 4/1.6 |
| M4 | 4/1.6 |
| M7 | 8/1.6 |
| M8 | 8/1.6 |
| M11 | 4/2.6 |
| M12 | 4/2.6 |
| M15 | 8/1.6 |
| M16 | 8/1.6 |

(b)

Simulation of DETFF

