



36th Design Automation Conference
New Orleans, June 21-25, 1999

Analog and Mixed-Signal Modeling Using the VHDL-AMS Language

Ernst Christen
Beaverton, OR



Kenneth Bakalar
Rockville, MD



Allen M. Dewey
Durham, NC



Eduard Moser
Stuttgart, Germany





Tutorial Organization

- ◆ Part I: Introduction to the VHDL-AMS Language
 - Continuous Time Concepts
 - Mixed Continuous/Discrete Time Concepts
 - Frequency Domain and Noise Modeling

- ◆ Part II: VHDL-AMS in Practical Applications
 - VHDL-AMS Modeling Guidelines
 - VHDL-AMS Modeling Techniques
 - IC Applications
 - Modeling at Different Levels of Abstraction
 - Telecom Applications
 - Modeling Multi-Disciplinary Systems
 - Automotive Applications
 - MEMS Modeling Using the VHDL-AMS Language




Part I:

**Introduction
to the
VHDL-AMS Language**



Outline

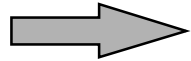

- ◆ Introduction
- ◆ Brief Overview of VHDL-AMS
- ◆ Basic Concepts: DAEs
- ◆ Systems with Conservation Semantics: Diode
- ◆ Mixed Technology: Diode with Self Heating
- ◆ Piecewise Defined Behavior: Compressor, Voltage Limiter
- ◆ Procedural Modeling: Weighted Summer
- ◆ Signal-Flow Modeling: Adder-Integrator, Conversions
- ◆ Solvability: Voltage Source, Signal Flow Amplifier
- ◆ Initial Conditions: Capacitor
- ◆ Implicit Quantities
- ◆ Mixed-Signal Modeling: Comparators, D/A Converter
- ◆ VHDL-AMS Model Execution
- ◆ Discontinuities: SCR, Voltage Limiter, Bouncing Ball
- ◆ Time-Dependent Modeling: Sinusoid Voltage Source
- ◆ Frequency Domain Modeling: Current Source, Filter
- ◆ Noise Modeling: Resistor, Diode
- ◆ Conclusion



What is VHDL-AMS

- ◆ IEEE Std. 1076-1993:
 - VHDL (VHSIC Hardware Description Language) supports the description and simulation of event-driven systems.
- ◆ IEEE Std. 1076.1-1999:
 - Extension to VHDL to support the description and simulation of analog and mixed-signal circuits and systems
- ◆ IEEE Std. 1076.1-1999 together with IEEE Std. 1076-1993 is informally known as VHDL-AMS
- ◆ VHDL-AMS is a strict superset of IEEE Std. 1076-1993
 - Any model valid in VHDL 1076 is valid in VHDL-AMS and yields the same simulation results




Why is VHDL-AMS needed?

- ◆ VHDL 1076 is suitable for modeling and simulating discrete systems
- ◆ Many of today's designs include at least some continuous characteristics:
 - System design
 - Mixed-signal electrical designs
 - Mixed electrical/non-electrical designs
 - Modeling design environment
 - Analog design
 - Analog behavioral modeling and simulation
 - Digital design
 - Detailed modeling (e.g. submicron effects)
- ◆ Designers want a uniform description language



Outline

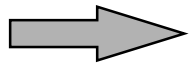

- ◆ Introduction
- ◆ Brief Overview of VHDL-AMS
- ◆ Basic Concepts: DAEs
- ◆ Systems with Conservation Semantics: Diode
- ◆ Mixed Technology: Diode with Self Heating
- ◆ Piecewise Defined Behavior: Compressor, Voltage Limiter
- ◆ Procedural Modeling: Weighted Summer
- ◆ Signal-Flow Modeling: Adder-Integrator, Conversions
- ◆ Solvability: Voltage Source, Signal Flow Amplifier
- ◆ Initial Conditions: Capacitor
- ◆ Implicit Quantities
- ◆ Mixed-Signal Modeling: Comparators, D/A Converter
- ◆ VHDL-AMS Model Execution
- ◆ Discontinuities: SCR, Voltage Limiter, Bouncing Ball
- ◆ Time-Dependent Modeling: Sinusoid Voltage Source
- ◆ Frequency Domain Modeling: Current Source, Filter
- ◆ Noise Modeling: Resistor, Diode
- ◆ Conclusion




VHDL 1076 Overview

- ◆ Entity defines interface of the model of a subsystem or physical device
- ◆ Each entity has one or more architectures, each implementing the behavior or structure of the subsystem or physical device
- ◆ Packages define collections of re-usable declarations and definitions: types, constants, functions etc.
- ◆ Strong type system
- ◆ Event-driven behavior described by processes that are sensitive to signals
- ◆ Well-defined simulation cycle, based on a canonical engine
- ◆ Predefined language environment



VHDL-AMS Language Architecture

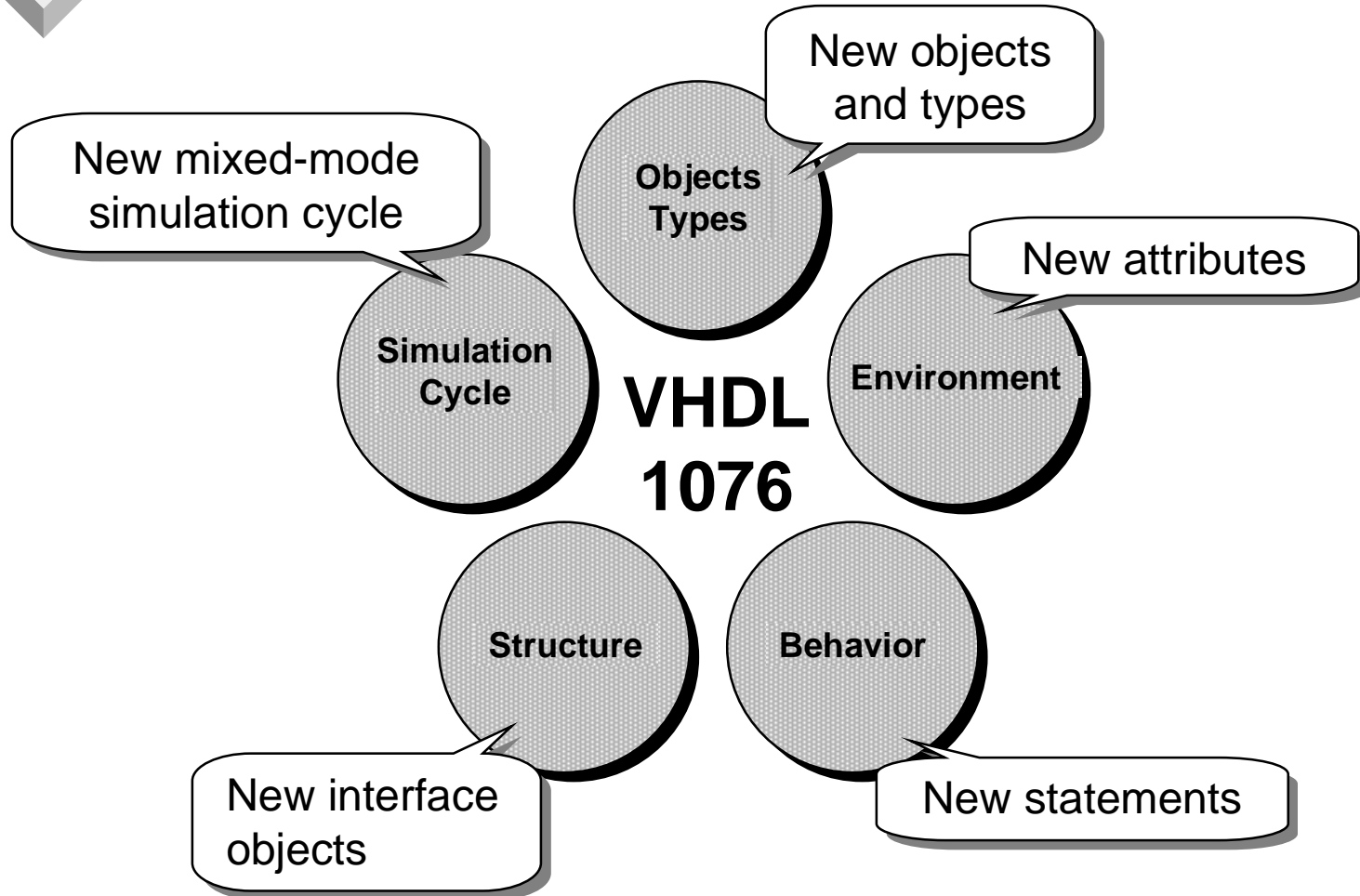



VHDL-AMS Highlights (1)

- ◆ **Superset of VHDL 1076-1993**
 - Full VHDL 1076-1993 syntax and semantics is supported
- ◆ **Adds new simulation model supporting continuous behavior**
 - Continuous models based on differential algebraic equations (DAEs)
 - DAEs solved by dedicated simulation kernel: the analog solver
 - Handling of initial conditions, piecewise-defined behavior, and discontinuities
 - Optimization of the set of DAEs being solved and how the analog solver computes its solution are outside the scope of VHDL-AMS




VHDL-AMS Highlights (2)

- ◆ **Extended structural semantics**
 - Conservative semantics to model physical systems
e.g. Kirchhoff's laws for electrical circuits
 - Non-conservative semantics for abstract models
Signal-flow descriptions
 - Mixed-signal interfaces
Models can have digital and analog ports
- ◆ **Mixed-signal semantics**
 - Unified model of time for a consistent synchronization of mixed event-driven/continuous behavior
 - Mixed-signal initialization and simulation cycle
 - Mixed-signal descriptions of behavior
- ◆ **Frequency domain support**
 - Small-signal frequency and noise modeling and simulation




Outline

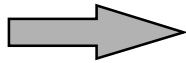

- ◆ Introduction
- ◆ Brief Overview of VHDL-AMS
- ◆ Basic Concepts: DAEs
- ◆ Systems with Conservation Semantics: Diode
- ◆ Mixed Technology: Diode with Self Heating
- ◆ Piecewise Defined Behavior: Compressor, Voltage Limiter
- ◆ Procedural Modeling: Weighted Summer
- ◆ Signal-Flow Modeling: Adder-Integrator, Conversions
- ◆ Solvability: Voltage Source, Signal Flow Amplifier
- ◆ Initial Conditions: Capacitor
- ◆ Implicit Quantities
- ◆ Mixed-Signal Modeling: Comparators, D/A Converter
- ◆ VHDL-AMS Model Execution
- ◆ Discontinuities: SCR, Voltage Limiter, Bouncing Ball
- ◆ Time-Dependent Modeling: Sinusoid Voltage Source
- ◆ Frequency Domain Modeling: Current Source, Filter
- ◆ Noise Modeling: Resistor, Diode
- ◆ Conclusion

Vibration in biatomic molecule

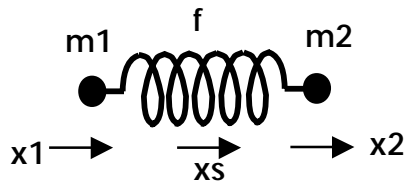- ◆ First approximation: one-dimensional spring model



$$m_1 \ddot{x}_1 = -f \cdot (x_1 - x_2)$$

$$m_2 \ddot{x}_2 = -f \cdot (x_2 - x_1)$$

$$x_s = (m_1 x_1 + m_2 x_2) / (m_1 + m_2)$$

$$\text{Energy} = 0.5 \cdot (m_1 \dot{x}_1^2 + m_2 \dot{x}_2^2 + f \cdot (x_1 - x_2)^2)$$

```


use work.types.all;
entity Vibration is
end entity Vibration;

architecture H2 of Vibration is -- hydrogen molecule
  quantity x1, x2, xs: displacement;
  quantity energy: REAL;
  constant m1, m2: REAL := 1.00794*1.6605655e-24;
  constant f: REAL := 496183.3;
begin
  x1'dot'dot == -f*(x1 - x2) / m1;
  x2'dot'dot == -f*(x2 - x1) / m2;
  xs == (m1*x1 + m2*x2)/(m1 + m2);
  energy == 0.5*(m1*x1'dot**2 + m2*x2'dot**2 + f*(x1-x2)**2);
end architecture H2;

```



Quantities (1)



```
architecture H2 of Vibration is
  ...
  quantity x1, x2, xs: displacement;
  quantity energy: REAL;
  ...
begin
  ...
```

- ◆ New object in VHDL 1076.1
- ◆ Represents an unknown in the set of DAEs implied by the text of a model
- ◆ Continuous-time waveform
- ◆ Scalar subelements must be of a floating-point type
- ◆ Default initial value for scalar subelements is 0.0




Quantities (2)

```
quantity x1, x2, xs: displacement;
...
begin
x1'dot'dot == -f*(x1 - x2) / m1;
...
energy == 0.5*(m1*x1'dot**2 +
             m2*x2'dot**2 + f*(x1-x2)**2);
```

- ◆ For any quantity Q , the attribute name Q' Dot denotes the derivative of Q w.r.t. time
- ◆ Q' Dot is itself a quantity

Simultaneous Statements (1)



```
architecture H2 of Vibration is
    ...
begin
    x1'dot'dot == -f*(x1 - x2) / m1;
    x2'dot'dot == -f*(x2 - x1) / m2;
    xs == (m1*x1 + m2*x2)/(m1 + m2);
    energy == 0.5*(m1*x1'dot**2 +
                 m2*x2'dot**2 + f*(x1-x2)**2);
end architecture H2;
```

- ◆ New class of statements in VHDL 1076.1
- ◆ Simple simultaneous statements express relationships between quantities
 - Left-hand side and right-hand side must be expressions with scalar subelements of a floating point type
 - Statement is symmetrical w.r.t. its left-hand and right-hand sides
 - Expressions may involve quantities, constants, literals, signals, and (possibly user-defined) functions
 - At least one quantity must appear in a simultaneous statement



Simultaneous Statements (2)

- ◆ Analog solver is responsible for computing the values of the quantities such that the relationships hold (subject to tolerances)
- ◆ Simultaneous statements may appear anywhere a concurrent statements may appear
- ◆ The order of simultaneous statements does not matter
- ◆ Other forms for simultaneous statements:
 - Simultaneous if statement
 - Simultaneous case statement
 - Simultaneous procedural statement



Tolerances (1)

- ◆ Numerical algorithms used by analog solver can only find an approximation of the exact solution
- ◆ Tolerances are used to specify how good the solution must be
- ◆ Each quantity and each simultaneous statement belongs to a tolerance group indicated by a string expression
 - All members of a tolerance group have the same tolerance characteristics
- ◆ The language does not define how a tool uses tolerance groups
 - For example, abstol and reltol in SPICE-like algorithms



Tolerances (2)

- ◆ A quantity gets its tolerance group from its subtype


```
package types is
  subtype displacement is REAL
                        tolerance "default_displacement";
  ...
end package types;
```

```
architecture H2 of Vibration is -- hydrogen molecule
  quantity x1, x2, xs: displacement;
  quantity energy: REAL;
  ...
```

- ◆ Type REAL belongs to an unnamed tolerance group: its tolerance code is ""

Tolerances (3)

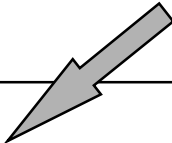
- ◆ A simple simultaneous statement whose LHS or RHS is a quantity gets its tolerance group from the quantity, otherwise the tolerance group must be specified



```
x1'dot'dot == -f*(x1 - x2) / m1;  
m2 * x2'dot'dot == -f*(x2 - x1) tolerance "displacement";  
xs == (m1*x1 + m2*x2)/(m1 + m2);  
energy == 0.5*(m1*x1'dot**2 + m2*x2'dot**2 + f*(x1-x2)**2);
```



Outline

 


- ◆ Introduction
- ◆ Brief Overview of VHDL-AMS
- ◆ Basic Concepts: DAEs
- ◆ Systems with Conservation Semantics: Diode
- ◆ Mixed Technology: Diode with Self Heating
- ◆ Piecewise Defined Behavior: Compressor, Voltage Limiter
- ◆ Procedural Modeling: Weighted Summer
- ◆ Signal-Flow Modeling: Adder-Integrator, Conversions
- ◆ Solvability: Voltage Source, Signal Flow Amplifier
- ◆ Initial Conditions: Capacitor
- ◆ Implicit Quantities
- ◆ Mixed-Signal Modeling: Comparators, D/A Converter
- ◆ VHDL-AMS Model Execution
- ◆ Discontinuities: SCR, Voltage Limiter, Bouncing Ball
- ◆ Time-Dependent Modeling: Sinusoid Voltage Source
- ◆ Frequency Domain Modeling: Current Source, Filter
- ◆ Noise Modeling: Resistor, Diode
- ◆ Conclusion



Parameterized Diode

 
- ◆ Example of a conservative model of an electrical component



- ◆ Simple large-signal model

$$i_d = i_s \cdot \left(e^{(v_d - r_s \cdot i_d) / n \cdot v_t} - 1 \right)$$
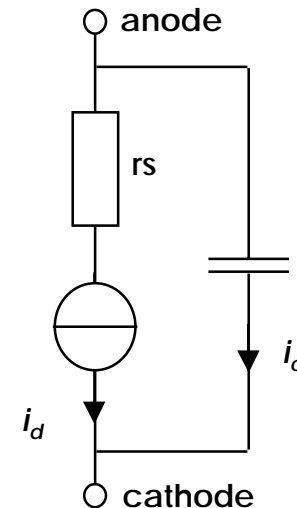
$$i_c = \frac{d}{dt} \left(t_t \cdot i_d - 2 \cdot c_j 0 \cdot \sqrt{v_j^2 - v_j \cdot v_d} \right)$$



VHDL-AMS Model of Diode

```
library IEEE, Disciplines;
use Disciplines.electrical_system.all;
use IEEE.math_real.all;
entity Diode is
  generic (iss: REAL := 1.0e-14;
          n, af: REAL := 1.0;
          tt, cj0, vj, rs, kf: REAL := 0.0);
  port (terminal anode, cathode: electrical);
end entity Diode;

architecture Level0 of Diode is
  quantity vd across id, ic through anode to cathode;
  quantity qc: charge;
  constant vt: REAL := 0.0258;      -- thermal voltage
begin
  id == iss * (exp((vd-rs*id)/(n*vt)) - 1.0);
  qc == tt*id - 2.0*cj0 * sqrt(vj**2 - vj*vd);
  ic == qc'dot;
end architecture Level0;
```



Terminal

```
library IEEE, Disciplines;
use Disciplines.electrical_system.all;
...
entity Diode is
    ...
    port (terminal anode, cathode: electrical);
end entity Diode;
```

Two grey arrows are present. One points from the right towards the word 'all' in the 'use' statement. The other points from the left towards the word 'terminal' in the port declaration.

- ◆ New object in VHDL 1076.1
- ◆ Basic support for structural composition with conservative semantics
- ◆ Belongs to a nature
 - Nature `electrical` defined in package `electrical_system`



Nature

- ◆ Represents a physical discipline or energy domain
 - Electrical and non-electrical disciplines
- ◆ Has two aspects related to physical effects
 - Across: effort like effects (voltage, velocity, temperature, etc.)
 - Through: flow like effects (current, force, heat flow rate, etc.)
- ◆ A nature defines the types of the across and through quantities incident to a terminal of the nature
- ◆ A scalar nature additionally defines the reference terminal for all terminals whose scalar subelements belong to the scalar nature
- ◆ A nature can be composite: array or record
 - All scalar subelements must have the same scalar nature
- ◆ No predefined natures in VHDL 1076.1

Electrical Systems Environment

```
package electrical_system is
  subtype voltage is REAL tolerance "default_voltage";
  subtype current is REAL tolerance "default_current";
  subtype charge is REAL tolerance "default_charge";
  nature electrical is
    voltage      across      -- across type
    current      through     -- through type
    electrical_ref reference; -- reference terminal
  alias ground is electrical_ref;
  nature electrical_vector is
    array(NATURAL range <>) of electrical;
end package electrical_system;
```

- ◆ Assume package is compiled into a library
- ## Disciplines

Branch Quantities (1)


```
architecture Level0 of Diode is
  quantity vd across id, ic through anode to cathode;
  ...
begin
  ...
end architecture Level0;
```

- ◆ Declared between two terminals
 - Plus terminal and minus terminal
 - Minus terminal defaults to reference terminal of nature
- ◆ `vd` is an across quantity: it represents the voltage between terminals `anode` and `cathode`
 - $vd = v_{\text{anode}} - v_{\text{cathode}}$
- ◆ `id` and `ic` are through quantities: they represent the currents in the two parallel branches
 - Both currents flow from terminal `anode` to terminal `cathode`




Branch Quantities (2)

 - ◆ A branch quantity gets its type from the nature of its plus and minus terminals
- ◆ The scalar subelements of the plus and minus terminal of a branch quantity must belong to the same scalar nature
- ◆ Multiple across quantities declared between the same terminals have the same value
- ◆ Multiple through quantities declared between the same terminals define distinct parallel branches



Terminal Attributes

- ◆ T'Reference
 - Implicit across quantity with terminal T of nature N as plus terminal and reference terminal of N as minus terminal (e.g. voltage to ground)
- ◆ T'Contribution
 - Implicit through quantity
 - Value equals the sum of the values of all through quantities incident to T (with the appropriate sign)
- ◆ For the diode model
 - Reference terminal is `electrical_ref`, aliased to ground
 - $v_d = \text{anode}'\text{reference} - \text{cathode}'\text{reference}$
 - $\text{anode}'\text{contribution} = i_d + i_c$
 - $\text{cathode}'\text{contribution} = -(i_d + i_c)$

 




Outline



- ◆ Introduction
- ◆ Brief Overview of VHDL-AMS
- ◆ Basic Concepts: DAEs
- ◆ Systems with Conservation Semantics: Diode
- ◆ Mixed Technology: Diode with Self Heating
- ◆ Piecewise Defined Behavior: Compressor, Voltage Limiter
- ◆ Procedural Modeling: Weighted Summer
- ◆ Signal-Flow Modeling: Adder-Integrator, Conversions
- ◆ Solvability: Voltage Source, Signal Flow Amplifier
- ◆ Initial Conditions: Capacitor
- ◆ Implicit Quantities
- ◆ Mixed-Signal Modeling: Comparators, D/A Converter
- ◆ VHDL-AMS Model Execution
- ◆ Discontinuities: SCR, Voltage Limiter, Bouncing Ball
- ◆ Time-Dependent Modeling: Sinusoid Voltage Source
- ◆ Frequency Domain Modeling: Current Source, Filter
- ◆ Noise Modeling: Resistor, Diode
- ◆ Conclusion

Diode with Self Heating

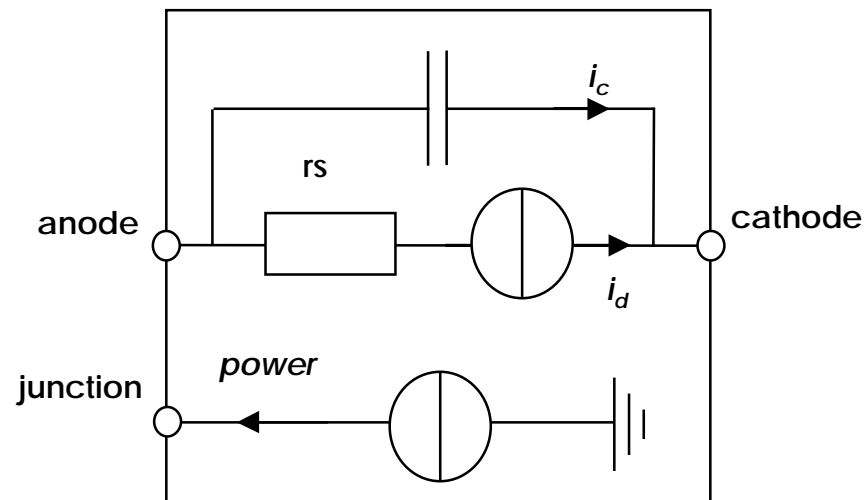- ◆ Example of a mixed-technology model:
Electro-thermal interaction in a diode



- ◆ Thermal voltage V_T now depends on temperature
- ◆ Thermal branch is a through source that represents the power dissipated in the diode

Diode with Self Heating

VHDL-AMS Model Environment

◆ Thermal nature

```
package thermal_system is
  subtype temperature is REAL
                    tolerance "default_temperature";
  subtype heatflow is REAL
                    tolerance "default_heatflow";
  nature thermal is
    temperature across
    heatflow      through
    thermal_ref  reference;
end package thermal_system;
```


◆ Physical constants, ambient temperature

```
package environment is
  constant boltzmann      : REAL := 1.381e-23;  -- in J/K
  constant elec_charge    : REAL := 1.602e-19;  -- in C
  constant ambient_temp  : REAL := 300.0;      -- in K
  ...
end package environment;
```





VHDL
AMS

Diode with Self Heating VHDL-AMS Entity Declaration



```
library IEEE, Disciplines;
use Disciplines.electrical_system.all;
use Disciplines.thermal_system.all;
use Disciplines.environment.all;
use IEEE.math_real.all;
entity DiodeTh is
    generic (iss: REAL := 1.0e-14;
            n, af: REAL := 1.0;
            tt, cj0, vj, rs, kf: REAL := 0.0);
    port (terminal anode, cathode: electrical;
          terminal junction: thermal);
end entity DiodeTh;
```





Diode with Self Heating VHDL-AMS Architecture Body

```
architecture Level0 of DiodeTh is
  quantity vd across id, ic through anode to cathode;
  quantity temp across power through
                                thermal_ref to junction;
  quantity qc: charge;
  quantity vt: voltage;          -- thermal voltage
begin
  qc == tt*id - 2.0*cj0 * sqrt(vj**2 - vj*vd);
  ic == qc'dot;
  id == iss * (exp((vd-rs*id)/(n*vt)) - 1.0);
  vt == temp * boltzmann / elec_charge;
  power == vd * id;
end architecture Level0;
```


Test Bench for Diode with Self Heating

```

library Disciplines;
use Disciplines.electrical_system.all;
use Disciplines.thermal_system.all;
entity TestBench is
end entity TestBench;

architecture DiodeWithHeatSink of TestBench is
  terminal a, b: electrical;
  terminal j, h: thermal;
begin
  v0: entity Vdc generic map (dc => 1.0)
    port map (p => a, m => ground);
  r1: entity Resistor generic map (r => 1.0e3)
    port map (p => a, m => b);
  d1: entity DiodeTh port map (anode => b,
    cathode => ground, junction => j);
  heatres: entity ResistorTh generic map (r => 0.1)
    port map (p => j, m => h);
  heatsink: entity CapacitorTh generic map (c => 0.008)
    port map (p => h, m => thermal_ref);
  rad: entity ResistorTh generic map (r => 10.0)
    port map (p => h, m => thermal_ref);
end architecture DiodeWithHeatSink;

```

 

Basic Thermal Elements

```
library Disciplines;
use Disciplines.thermal_system.all;
entity ResistorTh is
    generic (r: REAL);
    port (terminal p, m: thermal);
end entity ResistorTh;

architecture Ideal of ResistorTh is
    quantity temp across power through p to m;
begin
    power == temp / r;
end architecture Ideal;
```

```
library Disciplines;
use Disciplines.thermal_system.all;
entity CapacitorTh is
    generic (c: REAL);
    port (terminal p, m: thermal);
end entity CapacitorTh;

architecture Ideal of CapacitorTh is
    quantity temp across power through p to m;
begin
    power == c * temp'dot;
end architecture Ideal;
```



Outline



- ◆ Introduction
- ◆ Brief Overview of VHDL-AMS
- ◆ Basic Concepts: DAEs
- ◆ Systems with Conservation Semantics: Diode
- ◆ Mixed Technology: Diode with Self Heating
- ◆ Piecewise Defined Behavior: Compressor, Voltage Limiter
- ◆ Procedural Modeling: Weighted Summer
- ◆ Signal-Flow Modeling: Adder-Integrator, Conversions
- ◆ Solvability: Voltage Source, Signal Flow Amplifier
- ◆ Initial Conditions: Capacitor
- ◆ Implicit Quantities
- ◆ Mixed-Signal Modeling: Comparators, D/A Converter
- ◆ VHDL-AMS Model Execution
- ◆ Discontinuities: SCR, Voltage Limiter, Bouncing Ball
- ◆ Time-Dependent Modeling: Sinusoid Voltage Source
- ◆ Frequency Domain Modeling: Current Source, Filter
- ◆ Noise Modeling: Resistor, Diode
- ◆ Conclusion

Piecewise Defined Behavior (1)

```
library IEEE, Disciplines;
use Disciplines.electrical_system.all;
use IEEE.math_real.all;
entity Compressor is
  generic (vmax : REAL := 10.0;
          a     : REAL := 100.0;
          gain  : REAL := 1.0 );
  port (terminal ip, im, op, om : electrical);
end entity Compressor;
```

```
architecture A_law of Compressor is
  quantity vin across ip to im;
  quantity vout across iout through op to om;
  constant alog: REAL := 1.0 + log(a);
begin
  if -vmax/a < vin and vin < vmax/a use
    vout == gain * a * vin / ( alog * vmax );
  elsif vin > 0.0 use
    vout == gain * ( alog + log( vin/vmax) ) / alog;
  else
    vout == -gain * ( alog + log(-vin/vmax) ) / alog;
  end use;
end architecture A_law;
```



Piecewise Defined Behavior (2)

- ◆ Simultaneous if statement selects one of the statement parts based on the value of one or more conditions
- ◆ Each of the statement parts of a simultaneous if statement can include any of the simultaneous statements
 - Simple simultaneous statement
 - Simultaneous if statement
 - Simultaneous case statement
 - Simultaneous procedural statement
- ◆ Watch out for discontinuities in quantities and their derivatives!

Piecewise Defined Behavior (3)

```

library Disciplines;
use Disciplines.electrical_system.all;
entity VoltageLimiter is
  generic (vlim: REAL);          -- open loop gain
  port (terminal ip, im, op, om: electrical);
end entity VoltageLimiter;


```

```

architecture Bad of VoltageLimiter is
  quantity vin across ip to im;
  quantity vout across iout through op to om;
begin
  if vin > vlim use
    vout == vlim;
  elsif vin < -vlim use
    vout == -vlim;
  else
    vout == vin;
  end use;
end architecture Bad;

```


Discontinuity
in first
derivative

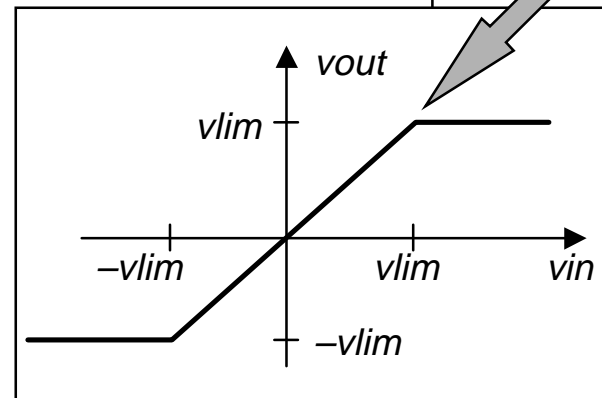




Outline

- ◆ Introduction
- ◆ Brief Overview of VHDL-AMS
- ◆ Basic Concepts: DAEs
- ◆ Systems with Conservation Semantics: Diode
- ◆ Mixed Technology: Diode with Self Heating
- ◆ Piecewise Defined Behavior: Compressor, Voltage Limiter
- ◆ Procedural Modeling: Weighted Summer
- ◆ Signal-Flow Modeling: Adder-Integrator, Conversions
- ◆ Solvability: Voltage Source, Signal Flow Amplifier
- ◆ Initial Conditions: Capacitor
- ◆ Implicit Quantities
- ◆ Mixed-Signal Modeling: Comparators, D/A Converter
- ◆ VHDL-AMS Model Execution
- ◆ Discontinuities: SCR, Voltage Limiter, Bouncing Ball
- ◆ Time-Dependent Modeling: Sinusoid Voltage Source
- ◆ Frequency Domain Modeling: Current Source, Filter
- ◆ Noise Modeling: Resistor, Diode
- ◆ Conclusion

 

Weighted Summer

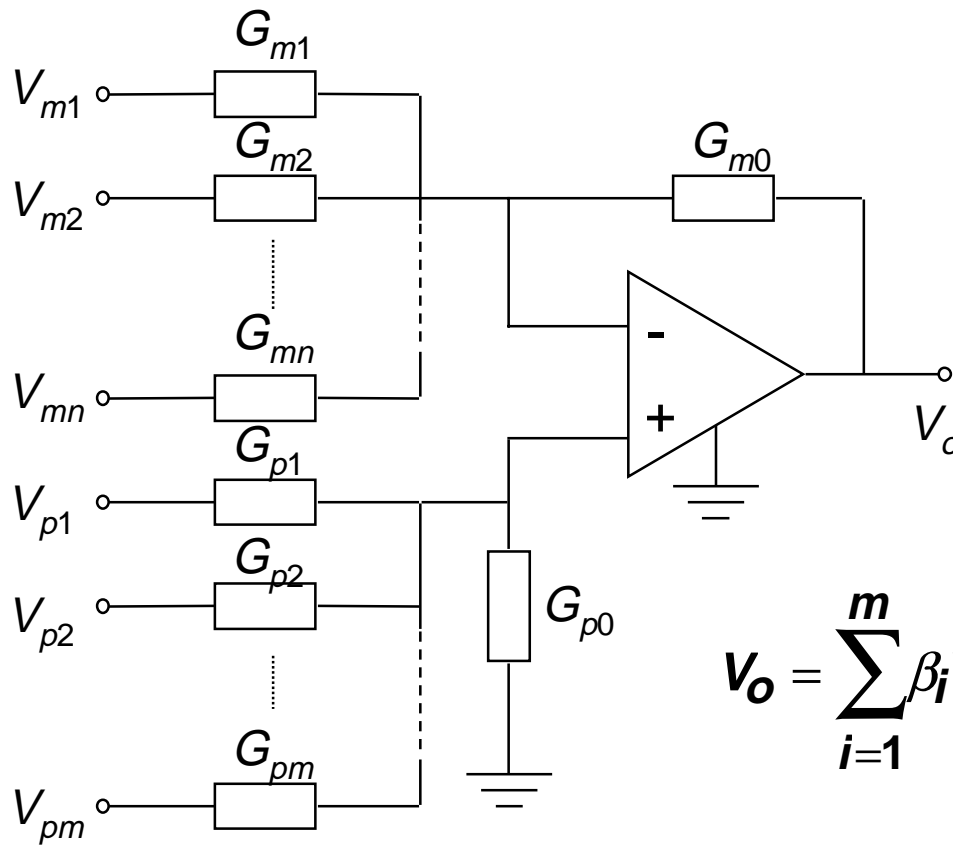

$$V_o = \sum_{i=1}^m \beta_i V_{pi} - \sum_{i=1}^n \gamma_i V_{mi}$$

Generic Weighted Summer VHDL-AMS Entity Declaration

```
library Disciplines;
use Disciplines.electrical_system.all;


entity WeightedSummer is
  generic (beta, gamma: REAL_VECTOR);
  port (terminal inp, inm: electrical_vector;
        terminal o: electrical);
end entity WeightedSummer;
```

◆ New predefined type `real_vector`

```
type REAL_VECTOR is array (NATURAL range <>) of REAL;
```

Generic Weighted Summer

VHDL-AMS Architecture Body: Declarations



```
architecture Proc of WeightedSummer is
    quantity vp across inp to ground;
    quantity vm across inm to ground;
    quantity vo across io through o to ground;
begin
    ...
end architecture Proc;
```

- ◆ Branch quantities `vp` and `vm` are composite because terminals `inp` and `inm` are composite



Generic Weighted Summer VHDL-AMS Architecture Body: Statements

- ◆ Using a simultaneous procedural statement

```
    ...  
begin  
    procedural is  
        variable bvs, gvs: REAL := 0.0;  
    begin  
        for i in beta'range loop  
            bvs := bvs + beta(i) * vp(i);  
        end loop;  
        for i in gamma'range loop  
            gvs := gvs + gamma(i) * vm(i);  
        end loop;  
        vo := bvs - gvs;  
    end procedural;  
end architecture Proc;
```

- ◆ Allows writing equations using a sequential language
 - Supports all sequential statements except wait, signal assignment, break

Generic Weighted Summer



VHDL-AMS Architecture Body Revisited

- ◆ Using a simple simultaneous statement and an overloaded function

```
architecture Simult of WeightedSummer is
  ... -- same declarations as in Proc

  function "*" (a: REAL_VECTOR;
               b: electrical_vector'across)
              return REAL is
    variable result: REAL := 0.0;
  begin      -- compute dot product
    for i in a'range loop
      result := result + a(i) * b(i);
    end loop;
    return result;
  end function "*";

  begin
  vo == beta * vp - gamma * vm;
end architecture Simult;
```






Outline

- ◆ Introduction
- ◆ Brief Overview of VHDL-AMS
- ◆ Basic Concepts: DAEs
- ◆ Systems with Conservation Semantics: Diode
- ◆ Mixed Technology: Diode with Self Heating
- ◆ Piecewise Defined Behavior: Compressor, Voltage Limiter
- ◆ Procedural Modeling: Weighted Summer
- ➔ ◆ Signal-Flow Modeling: Adder-Integrator, Conversions
- ◆ Solvability: Voltage Source, Signal Flow Amplifier
- ◆ Initial Conditions: Capacitor
- ◆ Implicit Quantities
- ◆ Mixed-Signal Modeling: Comparators, D/A Converter
- ◆ VHDL-AMS Model Execution
- ◆ Discontinuities: SCR, Voltage Limiter, Bouncing Ball
- ◆ Time-Dependent Modeling: Sinusoid Voltage Source
- ◆ Frequency Domain Modeling: Current Source, Filter
- ◆ Noise Modeling: Resistor, Diode
- ◆ Conclusion

Signal-Flow Modeling (1)



```
entity AdderIntegrator is
  generic (k1, k2: REAL := 1.0);
  port(quantity in1, in2: in REAL;
        quantity output: out REAL);
end entity AdderIntegrator;

architecture Sfg of AdderIntegrator is
  quantity qint: REAL;
begin
  qint == k1*in1 + k2*in2;
  output == qint'integ;
end architecture Sfg;
```

- ◆ Interface quantities have mode **in** or **out**



Signal Flow Modeling (2)


- ◆ Modes are used for solvability checks
- ◆ Modes are also used to determine correctness of a port association:
 - A quantity port with mode `in` can be associated with any kind of quantity as an actual
 - A quantity port with mode `out` can only be associated with an actual that is:
 - A quantity port with mode `out`
 - A free quantity
 - A branch quantity
 - The same quantity can be associated as an actual with at most one quantity port with mode `out`

Signal Flow Test Bench

```

library IEEE;
use IEEE.math_real.all;
architecture Sfg of TestBench is
  quantity in1, in2, s: REAL;
  terminal t1, t2: electrical;
begin
  in1 == exp(-NOW);      -- NOW is current time
  i1: entity Isine
      generic map (ampl => 1.0, freq => 1.0e3)
      port map (p => ground, m => t1);
  r1: entity Resistor generic map (r => 1.0e3)
      port map (p => t1, m => t2);
  c1: entity Capacitor generic map (c => 1.0e-9)
      port map (p => t2, m => ground);
  cv: entity Electrical2Sfg(Across2Sfg)
      port map (p => t2, m => ground, output => in2);
  ai: entity AdderIntegrator port map (in1 => in1,
      in2 => in2, output => s);
end architecture Sfg;

```

 

Signal Flow Modeling: Conversion

- ◆ Terminals and quantities cannot be connected directly, conversion models are needed

```
library Disciplines;  
use Disciplines.electrical_system.all;  
entity Electrical2Sfg is  
    port (terminal p, m: electrical;  
          quantity output: out REAL);  
end entity Electrical2Sfg;
```


```
architecture Across2Sfg of Electrical2Sfg is  
    quantity v across p to m;  
begin  
    output == v; ←  
end architecture Across2Sfg;
```

```
architecture Through2Sfg of Electrical2Sfg is  
    quantity v across i through p to m;  
begin  
    v == 0.0;  
    output == i;  
end architecture Through2Sfg;
```



Outline

- ◆ Introduction
- ◆ Brief Overview of VHDL-AMS
- ◆ Basic Concepts: DAEs
- ◆ Systems with Conservation Semantics: Diode
- ◆ Mixed Technology: Diode with Self Heating
- ◆ Piecewise Defined Behavior: Compressor, Voltage Limiter
- ◆ Procedural Modeling: Weighted Summer
- ◆ Signal-Flow Modeling: Adder-Integrator, Conversions
- ◆ Solvability: Voltage Source, Signal Flow Amplifier
- ◆ Initial Conditions: Capacitor
- ◆ Implicit Quantities
- ◆ Mixed-Signal Modeling: Comparators, D/A Converter
- ◆ VHDL-AMS Model Execution
- ◆ Discontinuities: SCR, Voltage Limiter, Bouncing Ball
- ◆ Time-Dependent Modeling: Sinusoid Voltage Source
- ◆ Frequency Domain Modeling: Current Source, Filter
- ◆ Noise Modeling: Resistor, Diode
- ◆ Conclusion

 



Solvability Checks (1)

```
entity Vdc is
  generic (dc: REAL);
  port (terminal p, m: electrical);
end entity Vdc;
```

```
architecture Bad of Vdc is
  quantity v across p to m;
begin
  v == dc;
end architecture Bad;
```

~~OK~~

```
architecture Good of Vdc is
  quantity v across i through p to m;
begin
  v == dc;
end architecture Good;
```

OK

- ◆ A necessary condition for solvability is that there be as many equations as unknowns in the model
- ◆ In a VHDL-AMS design entity the number of equations must equal the number of through quantities, free quantities and interface quantities with mode out
- ◆ Each (scalar) simultaneous statement creates one equation
- ◆ In the example:
 - One equation is defined in both architectures
 - Only architecture Good has declaration for a through quantity
 - The language defines an implicit equation for each across quantity

Solvability Checks (2)

```
entity SfgAmp is
  generic (gain: REAL := REAL'high);
  port (quantity input: in REAL;
        quantity output: out REAL);
end entity SfgAmp;


architecture Ideal of SfgAmp is
begin
  if gain /= REAL'high use
    output == gain * input;
  else
    input == 0.0;    -- infinite gain
  end use;
end architecture Ideal; OK
```

- ◆ There is one interface quantity with mode out
- ◆ For any value of gain there is one equation



Outline

- ◆ Introduction
- ◆ Brief Overview of VHDL-AMS
- ◆ Basic Concepts: DAEs
- ◆ Systems with Conservation Semantics: Diode
- ◆ Mixed Technology: Diode with Self Heating
- ◆ Piecewise Defined Behavior: Compressor, Voltage Limiter
- ◆ Procedural Modeling: Weighted Summer
- ◆ Signal-Flow Modeling: Adder-Integrator, Conversions
- ◆ Solvability: Voltage Source, Signal Flow Amplifier
- ◆ Initial Conditions: Capacitor
- ◆ Implicit Quantities
- ◆ Mixed-Signal Modeling: Comparators, D/A Converter
- ◆ VHDL-AMS Model Execution
- ◆ Discontinuities: SCR, Voltage Limiter, Bouncing Ball
- ◆ Time-Dependent Modeling: Sinusoid Voltage Source
- ◆ Frequency Domain Modeling: Current Source, Filter
- ◆ Noise Modeling: Resistor, Diode
- ◆ Conclusion

 

Initial Conditions (1)

- ◆ An initial condition specifies the value of a quantity at the beginning of a continuous interval
 - Beginning of a time domain simulation
 - After a discontinuity
- ◆ Initial conditions are specified with the break statement:

➔ `break v => 0.0, s => 10.0;`

- The initial condition for quantity v is 0.0, for quantity s, 10.0
- ◆ Initial conditions replace implicit equations while finding an analog solution point. An initial condition for Q replaces
 - the equation $Q'_{\text{Dot}} == 0$ while finding the quiescent state
 - the equation $Q == Q(t-)$ when re-initializing after discontinuity
- ◆ If an initial condition must be specified for a quantity Q whose derivative Q'_{Dot} does not appear in the model, the user must specify which implicit equation to replace

Initial Conditions (2)

```
entity Capacitor is
  generic (C: REAL; ic: REAL := REAL'low);
  port (terminal p, m: electrical);
end entity Capacitor;
```

```
architecture One of Capacitor is
  quantity v across i through p to m;
begin
  i == C * v'dot;
  break v => ic when ic /= REAL'low;
end architecture One;
```

v == ic replaces
v'dot == 0


```
architecture Two of Capacitor is
  quantity v across i through p to m;
  quantity q : charge;
begin
  q == c * v;
  i == q'dot;
  break for q use v => ic
    when ic /= REAL'low;
end architecture Two;
```

v == ic replaces
q'dot == 0



Outline

- ◆ Introduction
- ◆ Brief Overview of VHDL-AMS
- ◆ Basic Concepts: DAEs
- ◆ Systems with Conservation Semantics: Diode
- ◆ Mixed Technology: Diode with Self Heating
- ◆ Piecewise Defined Behavior: Compressor, Voltage Limiter
- ◆ Procedural Modeling: Weighted Summer
- ◆ Signal-Flow Modeling: Adder-Integrator, Conversions
- ◆ Solvability: Voltage Source, Signal Flow Amplifier
- ◆ Initial Conditions: Capacitor
- ◆ Implicit Quantities
- ◆ Mixed-Signal Modeling: Comparators, D/A Converter
- ◆ VHDL-AMS Model Execution
- ◆ Discontinuities: SCR, Voltage Limiter, Bouncing Ball
- ◆ Time-Dependent Modeling: Sinusoid Voltage Source
- ◆ Frequency Domain Modeling: Current Source, Filter
- ◆ Noise Modeling: Resistor, Diode
- ◆ Conclusion

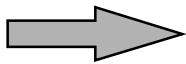



Implicit Quantities (1)

- ◆ Q'Dot
 - The derivative of quantity Q with respect to time
- ◆ Q'Integ
 - The integral of quantity Q over time from zero to current time
- ◆ Q'Slew(max_rising_slope, max_falling_slope)
 - Follows Q, but its derivative w.r.t. time is limited by the specified slopes. Default for max_falling_slope is max_rising_slope, default for max_rising_slope is infinity.
- ◆ Q'Delayed(T)
 - Quantity Q delayed by T (ideal delay, $T \geq 0$)


Implicit Quantities (2)

- ◆ $Q'Ltf(num, den)$
 - Laplace transfer function whose input is Q
- ◆ $Q'ZOH(T, initial_delay)$
 - A sampled version of quantity Q (zero-order hold)
- ◆ $Q'Ztf(num, den, T, initial_delay)$
 - Z-domain transfer function whose input is Q
- ◆ $S'Ramp(tr, tf)$
 - A quantity that follows signal S , but with specified rise and fall times. Default for tf is tr , default for tr is 0.0
- ◆ $S'Slew(max_rising_slope, max_falling_slope)$
 - A quantity that follows signal S , but its derivative w.r.t. time is limited by the specified slopes.
Default for $max_falling_slope$ is max_rising_slope , default for max_rising_slope is infinity.




Outline

- ◆ Introduction
- ◆ Brief Overview of VHDL-AMS
- ◆ Basic Concepts: DAEs
- ◆ Systems with Conservation Semantics: Diode
- ◆ Mixed Technology: Diode with Self Heating
- ◆ Piecewise Defined Behavior: Compressor, Voltage Limiter
- ◆ Procedural Modeling: Weighted Summer
- ◆ Signal-Flow Modeling: Adder-Integrator, Conversions
- ◆ Solvability: Voltage Source, Signal Flow Amplifier
- ◆ Initial Conditions: Capacitor
- ◆ Implicit Quantities
- ◆ Mixed-Signal Modeling: Comparators, D/A Converter
- ◆ VHDL-AMS Model Execution
- ◆ Discontinuities: SCR, Voltage Limiter, Bouncing Ball
- ◆ Time-Dependent Modeling: Sinusoid Voltage Source
- ◆ Frequency Domain Modeling: Current Source, Filter
- ◆ Noise Modeling: Resistor, Diode
- ◆ Conclusion

 



 Ideal Comparator VHDL-AMS Entity Declaration




```
entity Comparator is
  generic (vthresh: REAL);      -- threshold
  port (terminal ain, ref: electrical;
        signal dout: out BOOLEAN);
end entity Comparator;
```

- ◆ Keyword **signal** is optional but indicates intent:
 - Interface *terminals* ain and ref
 - Interface *signal* dout



Ideal Comparator VHDL-AMS Architecture Body
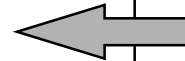
```
architecture Ideal of Comparator is
    quantity vin across ain to ref;
begin
    dout <= vin'above(vthresh);
end architecture Ideal;
```




- ◆ Threshold crossing detected with Q'Above(E), a boolean signal that
 - is FALSE when the value of quantity Q is below threshold E
 - is TRUE when the value of quantity Q is above threshold E
- ◆ Q must be a scalar quantity, E must be an expression of the same type as Q
- ◆ An event occurs on signal Q'Above(E) at the exact time of the threshold crossing
- ◆ A process can be sensitive to Q'Above(E), since it is a signal



Comparator with Hysteresis

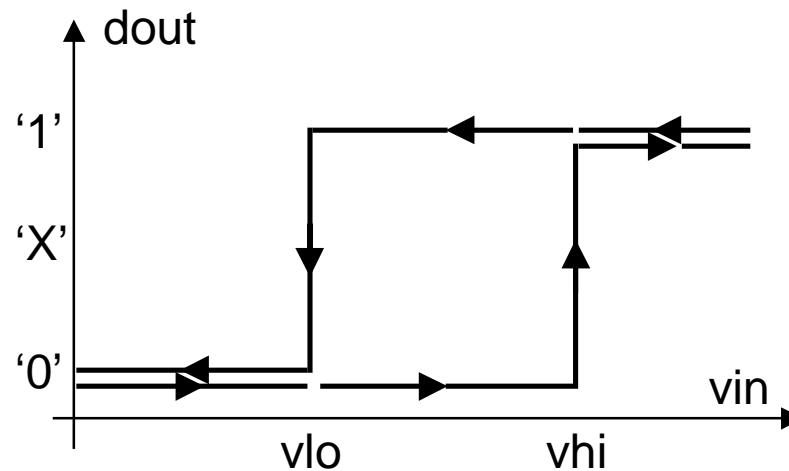
- ◆ Conversion of electrical quantity to std_logic signal
- ◆ Hysteresis



- dout becomes 'X' if vin stays in transition region for longer than the specified timeout




Comparator with Hysteresis State Diagram

 

Comparator with Hysteresis

VHDL-AMS Declarations

```
library IEEE, Disciplines;
use IEEE.std_logic_1164.all;
use Disciplines.electrical_system.all;
entity ComparatorHyst is
    generic (vlo, vhi: REAL; -- thresholds
            timeout: DELAY_LENGTH);
    port (terminal ain, ref: electrical;
          signal dout: out std_logic);
end entity ComparatorHyst;
```




```
architecture Hysteresis of ComparatorHyst is
    type states is (unknown, zero, one, unstable);
    quantity vin across ain to ref;
    function level(vin, vlo, vhi: REAL) return states is
    begin
        if    vin < vlo then return zero;
        elsif vin > vhi then return one;
        else
            return unknown;
        end if;
    end function level;
begin
    ...
```



VHDL
AMS

Comparator with Hysteresis

VHDL-AMS Process Implementing FSM




```
...
process
  variable state: states := level(vin, vlo, vhi);
begin
  case state is
    when one =>
      dout <= '1';
      wait on vin'Above(vhi);      -- wait for change
      state := unstable;
    when zero =>
      dout <= '0';
      wait on vin'Above(vlo);      -- wait for change
      state := unstable;
    when unknown =>
      dout <= 'X';
      wait on vin'Above(vhi), vin'Above(vlo);
      state := level(vin, vlo, vhi);
    when unstable =>
      wait on vin'Above(vhi), vin'Above(vlo) for timeout;
      state := level(vin, vlo, vhi);
  end case;
end process;
end architecture Hysteresis;
```



D/A Converter

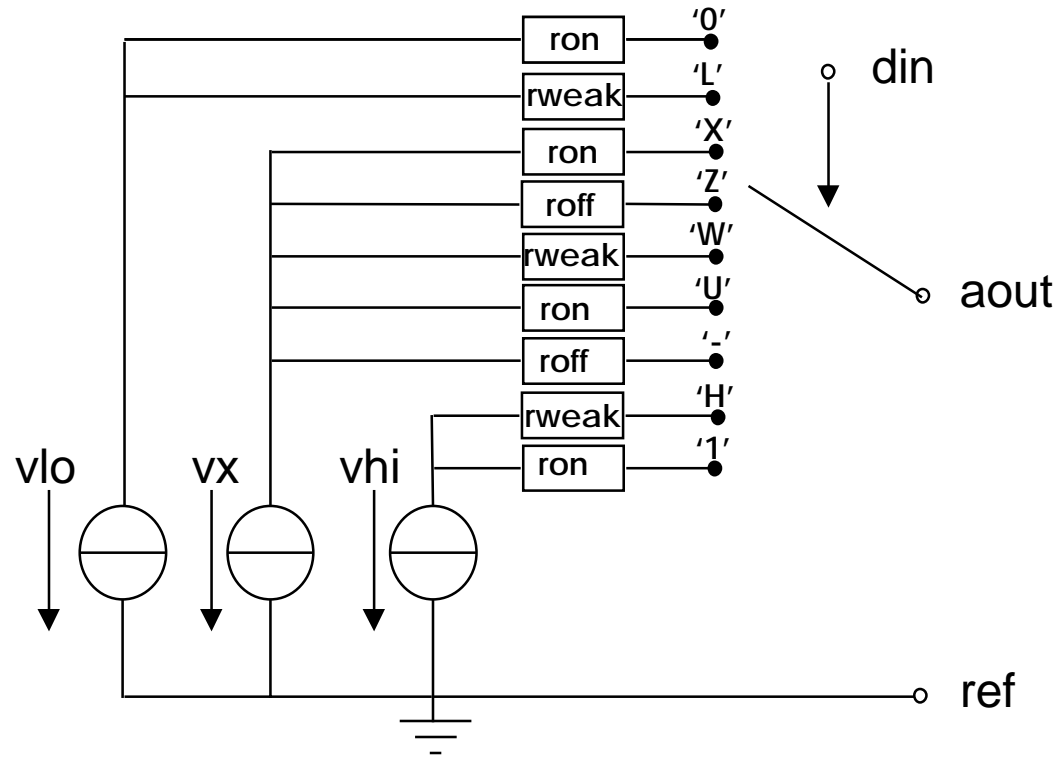- ◆ Conversion of a std_logic signal to a voltage:
 - Signal-controlled voltage source with output resistance





D/A Converter VHDL-AMS Entity Declaration

```
library ieee;
use ieee.std_logic_1164_pkg.all;
entity Dac is
  generic (vlo   : REAL := 0.2;      -- output voltage low
           vx    : REAL := 2.5;      -- output voltage unknown
           vhi   : REAL := 4.8;      -- output voltage high
           ron   : REAL := 0.1;      -- output resist. strong states
           rweak: REAL := 1.0e4;     -- output resist. weak states
           roff  : REAL := 1.0e9;    -- output resist. high imp.
           tt    : REAL := 1.0e-9); -- transition time
  port (signal din: in std_logic;
        terminal aout, ref: electrical);
end entity Dac;
```

D/A Converter

VHDL-AMS Architecture Body


```
architecture Simple of Dac is
  type real_table is array(std_logic) of REAL;
  constant r_table: real_table :=
    (ron, ron, ron, ron, roff, rweak, rweak, rweak, roff);
  constant v_table: real_table :=
    (vx, vx, vlo, vhi, vx, vx, vlo, vhi, vx);
  quantity vout across iout through aout to ref;
  signal reff: REAL; -- effective output resistance
  signal veff: REAL; -- effective output voltage
begin
  reff <= r_table(din);
  veff <= v_table(din);
  vout == veff'ramp(tt) - iout * reff'ramp(tt);
end architecture Simple;
```

- ◆ Tables ordered according to type `std_logic`
- ◆ Output voltage and resistance ramp linearly from previous value



Outline

- ◆ Introduction
- ◆ Brief Overview of VHDL-AMS
- ◆ Basic Concepts: DAEs
- ◆ Systems with Conservation Semantics: Diode
- ◆ Mixed Technology: Diode with Self Heating
- ◆ Piecewise Defined Behavior: Compressor, Voltage Limiter
- ◆ Procedural Modeling: Weighted Summer
- ◆ Signal-Flow Modeling: Adder-Integrator, Conversions
- ◆ Solvability: Voltage Source, Signal Flow Amplifier
- ◆ Initial Conditions: Capacitor
- ◆ Implicit Quantities
- ◆ Mixed-Signal Modeling: Comparators, D/A Converter
- ◆ VHDL-AMS Model Execution
- ◆ Discontinuities: SCR, Voltage Limiter, Bouncing Ball
- ◆ Time-Dependent Modeling: Sinusoid Voltage Source
- ◆ Frequency Domain Modeling: Current Source, Filter
- ◆ Noise Modeling: Resistor, Diode
- ◆ Conclusion

 




VHDL-AMS Model Execution

- ◆ A VHDL-AMS model is the result of the elaboration of the design hierarchy
 - Digital part => set of processes + digital simulation kernel
 - Analog part => set of equations + analog solver
- ◆ Two phases
 - Determination of quiescent state of the model
 - Includes initialization phase and simulation cycles at time 0 ns
 - Simulation: time domain, small-signal frequency, or noise
 - For time domain simulation, time ≥ 0 ns
- ◆ Reduces to the VHDL 1076 initialization and simulation cycle if the model does not include any quantities
- ◆ Only the analog solver is executed after initialization if the model does not include any signals



VHDL-AMS Initialization

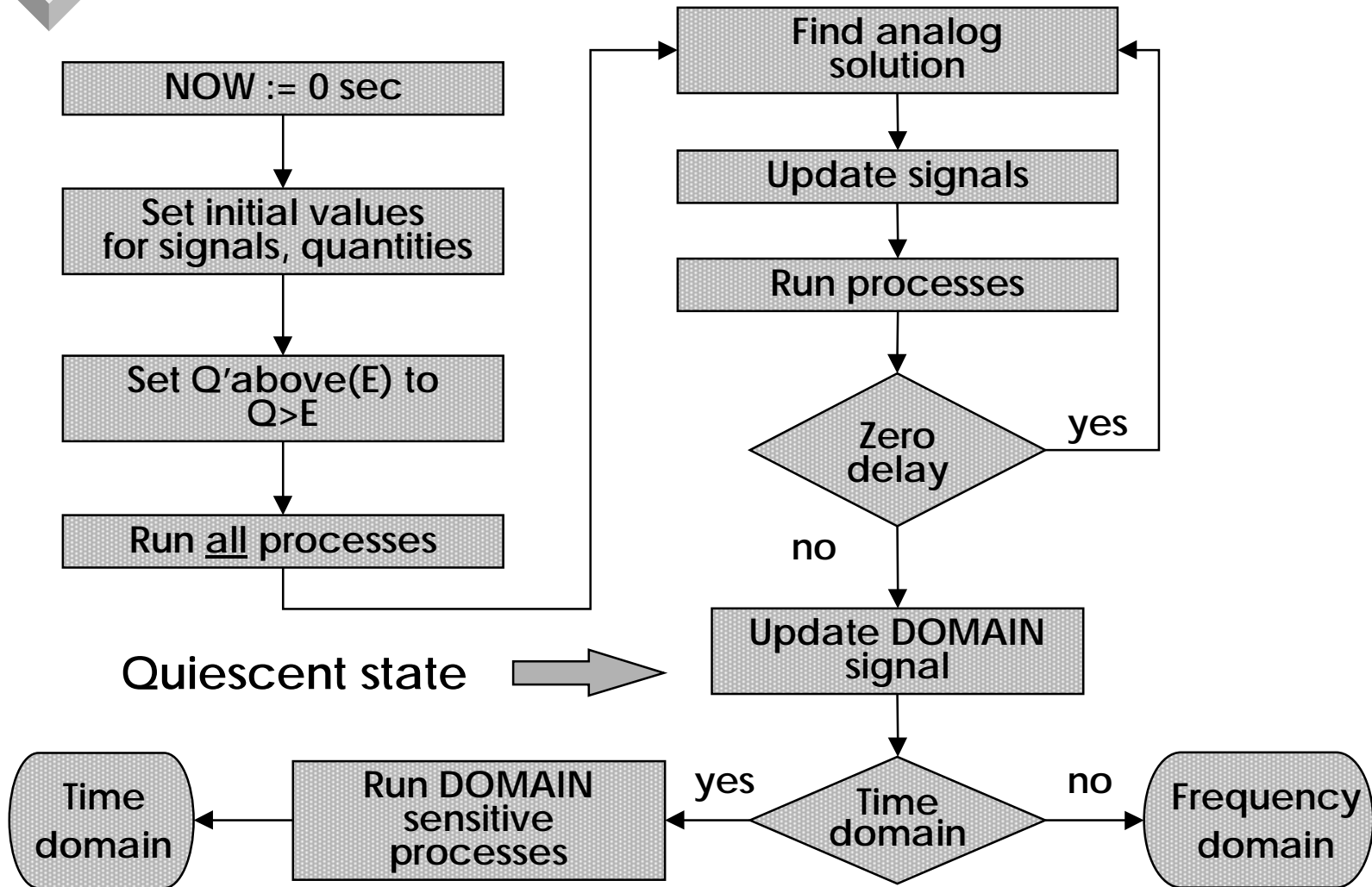



DOMAIN Signal


- ◆ New predefined signal DOMAIN of type DOMAIN_TYPE
 - Enumerated type with values QUIESCENT_DOMAIN, TIME_DOMAIN, FREQUENCY_DOMAIN
 - Set to QUIESCENT_DOMAIN during initialization
 - Set to TIME_DOMAIN or FREQUENCY_DOMAIN when the quiescent state has been reached (i.e., when there are no pending events at time 0), depending on whether a time domain or a frequency domain simulation follows

- ◆ DOMAIN can be used to write models that exhibit different behavior in different domains



VHDL-AMS Simulation Cycle


Time Domain Simulation

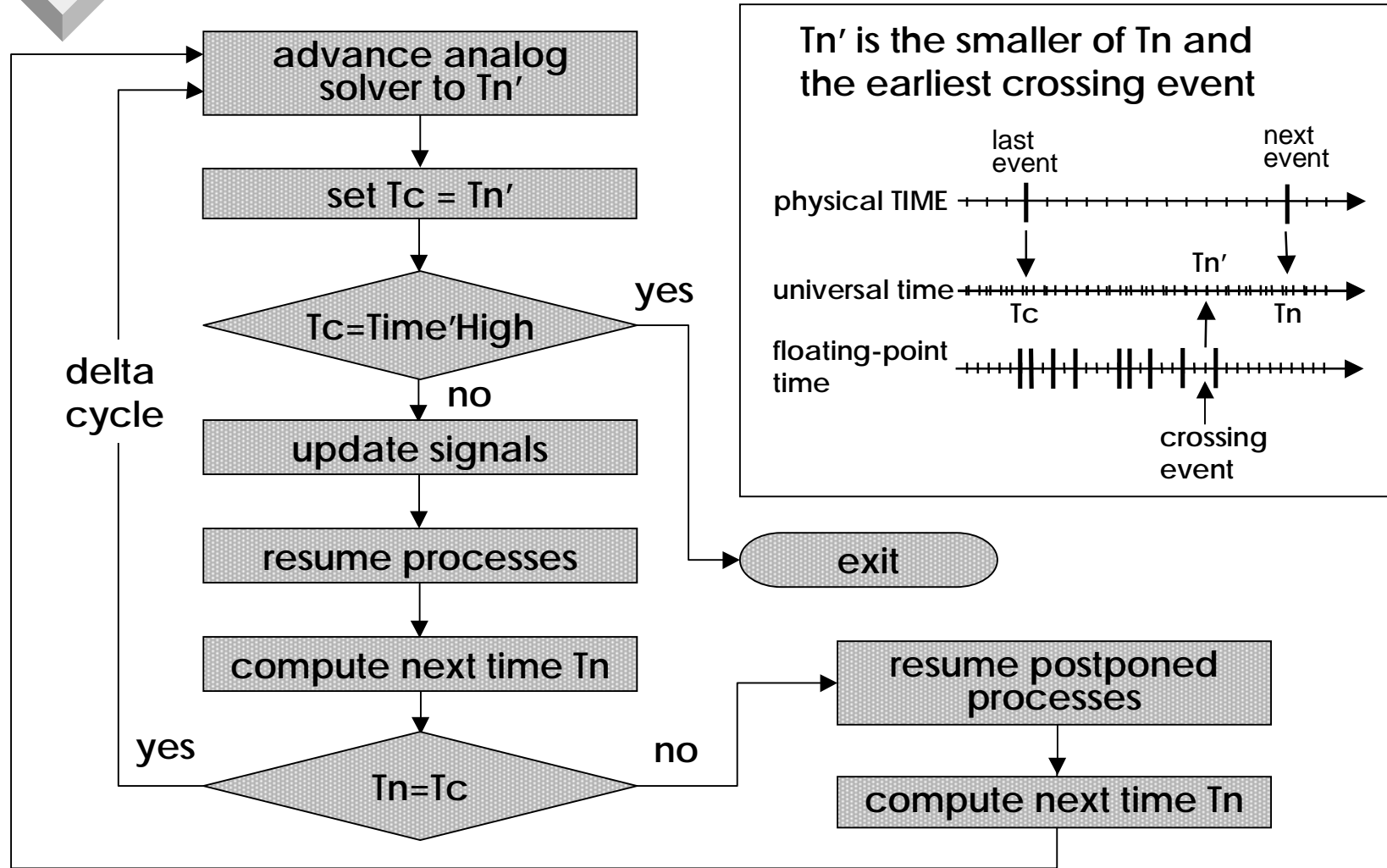



Outline


- ◆ Introduction
- ◆ Brief Overview of VHDL-AMS
- ◆ Basic Concepts: DAEs
- ◆ Systems with Conservation Semantics: Diode
- ◆ Mixed Technology: Diode with Self Heating
- ◆ Piecewise Defined Behavior: Compressor, Voltage Limiter
- ◆ Procedural Modeling: Weighted Summer
- ◆ Signal-Flow Modeling: Adder-Integrator, Conversions
- ◆ Solvability: Voltage Source, Signal Flow Amplifier
- ◆ Initial Conditions: Capacitor
- ◆ Implicit Quantities
- ◆ Mixed-Signal Modeling: Comparators, D/A Converter
- ◆ VHDL-AMS Model Execution
- ◆ Discontinuities: SCR, Voltage Limiter, Bouncing Ball
- ◆ Time-Dependent Modeling: Sinusoid Voltage Source
- ◆ Frequency Domain Modeling: Current Source, Filter
- ◆ Noise Modeling: Resistor, Diode
- ◆ Conclusion

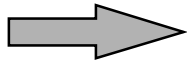

Silicon Controlled Rectifier VHDL-AMS Entity Declaration

```
library IEEE, Disciplines;
use IEEE.math_real.all;
use Disciplines.electrical_system.all;
entity Scr is
  generic (von    : voltage := 0.7;  -- Turn on voltage
           ihold  : current := 0.0;  -- Holding current
           iss    : REAL := 1.0e-12); -- Saturation current
  port (terminal anode, cathode, gate: electrical);
end entity Scr;
```

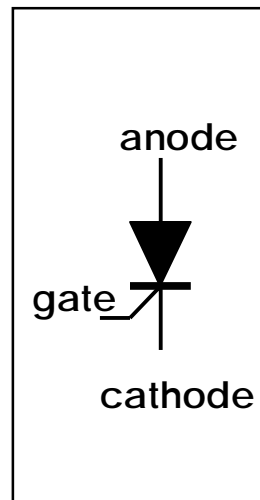- ◆ SCR turns on if voltage across SCR is positive and control voltage is larger than the on voltage `von`
- ◆ SCR turns off if control voltage is below the on voltage `von` and current falls below the holding current `ihold`



Silicon Controlled Rectifier

VHDL-AMS Architecture Body

```
architecture Ideal of Scr is
  quantity vscr across iscr through anode to cathode;
  quantity vcntl across gate to cathode;
  signal ison: BOOLEAN;
  constant vt: REAL := 0.0258;  -- thermal voltage
begin
  process
    variable off: BOOLEAN := true;
  begin
    ison <= not off;
    case off is
      when true =>
        wait until vcntl'Above(von) and vscr'Above(0.0);
        off := false;
      when false =>
        wait until not (vcntl'Above(von) or iscr'Above(ihold));
        off := true;
    end case;
  end process;

  if ison use
    iscr == iss * (exp(vscr/vt) - 1.0);
  else
    iscr == 0.0;
  end use;
  break on ison;
end architecture Ideal;
```



Break Statement

- ◆ New concurrent statement
- ◆ Announces a discontinuity in the solution of the DAEs
 - In the example `iscr` changes discontinuously
- ◆ Analog solver must re-initialize for next continuous interval
- ◆ Break on event may include condition
- ◆ New initial conditions may be specified on quantities
- ◆ A VHDL-AMS model that causes a discontinuity on a quantity at some time T and does not execute a break statement at T is erroneous
 - Exception: discontinuities caused by using `S'Ramp`, `S'Slew`, `Q'Slew`, `Q'ZOH`, `Q'Ztf`

Voltage Limiter Revisited


```
architecture Good of VoltageLimiter is
  quantity vin across ip to im;
  quantity vout across iout through op to om;
begin
  if vin'Above(vlim) use
    vout == vlim;
  elsif not vin'Above(-vlim) use
    vout == -vlim;
  else
    vout == vin;
  end use;
  break on vin'Above(vlim), vin'Above(-vlim);
end architecture Good;
```

- ◆ Compare with implementation on slide 40
 - Relational expressions have been replaced by names of implicit signals detecting change of state
 - Break statement announces discontinuity in derivative

Bouncing Ball

```
library Disciplines;
use Disciplines.mechanical_system.all;
entity BounceBall is
end entity BounceBall;


architecture Ideal of BounceBall is
  quantity v: velocity;           -- m/s
  quantity s: displacement;       -- m
  constant G: REAL := 9.81;       -- m/s**2
  constant Air_Res: REAL := 0.1;  -- 1/m
begin
  -- Specify initial conditions
  break v => 0.0, s => 10.0;
  -- announce discontinuity and reset velocity value
  break v => -v when not s'above(0.0);
  s'dot == v;
  if v > 0.0 use
    v'dot == -G - v**2*Air_Res;
  else
    v'dot == -G + v**2*Air_Res;
  end use;
end architecture Ideal;
```

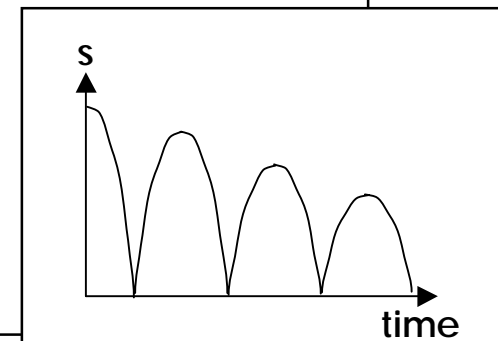



Outline

- ◆ Introduction
- ◆ Brief Overview of VHDL-AMS
- ◆ Basic Concepts: DAEs
- ◆ Systems with Conservation Semantics: Diode
- ◆ Mixed Technology: Diode with Self Heating
- ◆ Piecewise Defined Behavior: Compressor, Voltage Limiter
- ◆ Procedural Modeling: Weighted Summer
- ◆ Signal-Flow Modeling: Adder-Integrator, Conversions
- ◆ Solvability: Voltage Source, Signal Flow Amplifier
- ◆ Initial Conditions: Capacitor
- ◆ Implicit Quantities
- ◆ Mixed-Signal Modeling: Comparators, D/A Converter
- ◆ VHDL-AMS Model Execution
- ◆ Discontinuities: SCR, Voltage Limiter, Bouncing Ball
- ◆ Time-Dependent Modeling: Sinusoid Voltage Source
- ◆ Frequency Domain Modeling: Current Source, Filter
- ◆ Noise Modeling: Resistor, Diode
- ◆ Conclusion

 

Time-dependent Modeling Sinusoid Voltage Source

```
library Disciplines, IEEE;  
use Disciplines.electrical_system.all;  
use IEEE.math_real.all;  
entity Vsine is  
    generic (ampl, freq: REAL);  
    port (terminal p, m: electrical);  
end entity Vsine;
```

```
architecture Sine of Vsine is  
    quantity v across i through p to m;  
    limit v: electrical'across with 1.0/(20.0*freq);  
begin  
    v == ampl * sin(math_2_pi*freq*NOW);  
end architecture Sine;
```




Time-Dependent Modeling

- ◆ Predefined function NOW has been overloaded
 - NOW returning type TIME
 - NOW returning type REAL
- ◆ Analog solver computes the solution at certain times only
 - Time steps usually depend on tolerances
- ◆ For independent sources and free-running oscillators tolerances may not be sufficient to yield smooth waveform
- ◆ Step limit specification forces re-evaluation of listed quantities within interval specified by expression
 - Expression is evaluated after each analog solution point
 - Expression may depend on quantities and signals



Outline

- ◆ Introduction
- ◆ Brief Overview of VHDL-AMS
- ◆ Basic Concepts: DAEs
- ◆ Systems with Conservation Semantics: Diode
- ◆ Mixed Technology: Diode with Self Heating
- ◆ Piecewise Defined Behavior: Compressor, Voltage Limiter
- ◆ Procedural Modeling: Weighted Summer
- ◆ Signal-Flow Modeling: Adder-Integrator, Conversions
- ◆ Solvability: Voltage Source, Signal Flow Amplifier
- ◆ Initial Conditions: Capacitor
- ◆ Implicit Quantities
- ◆ Mixed-Signal Modeling: Comparators, D/A Converter
- ◆ VHDL-AMS Model Execution
- ◆ Discontinuities: SCR, Voltage Limiter, Bouncing Ball
- ◆ Time-Dependent Modeling: Sinusoid Voltage Source
- ◆ Frequency Domain Modeling: Current Source, Filter
- ◆ Noise Modeling: Resistor, Diode
- ◆ Conclusion

 



Frequency Domain Modeling

- ◆ Frequency domain simulation based on small-signal model
 - Obtained by linearizing equations about quiescent point
- ◆ Spectral source quantities allow a user to specify stimulus in the frequency domain
 - Magnitude and phase
 - Can be frequency dependent
 - Predefined function `FREQUENCY` can be called in the declaration of source quantities only
 - Value of spectral source quantity is 0.0 except during frequency domain simulation
- ◆ Laplace and z-domain transfer functions can be used to describe the behavior of abstract filters
- ◆ No support for more general frequency domain modeling because language scope is restricted to lumped systems

Current Source With AC Spectrum

```
library Disciplines, IEEE;
use Disciplines.electrical_system.all;
use IEEE.math_real.all;
entity Isine is
    generic (ampl, freq: REAL;
            mag, phase: REAL := 0.0);
    port (terminal p, m: electrical);
end entity Isine;
```

```
architecture Sine of Isine is
    quantity i through p to m;
    quantity ac: REAL spectrum mag, phase;
    limit i: electrical'through with 1.0/(20.0*freq);
begin
    i == ampl * sin(math_2_pi*freq*NOW) + ac;
end architecture Sine;
```

Second Order Lowpass Filter

- ◆ Behavior specified by pole frequency, pole Q and gain

```
library Disciplines, IEEE;
use Disciplines.electrical_system.all;
use IEEE.math_real.all;
entity Lowpass2 is
  generic (fp, qp: REAL;
           gain: REAL := 1.0);
  port (terminal input, output, ref: electrical);
end entity Lowpass2;
```


```
architecture One of Lowpass2 is
  quantity vin across input to ref;
  quantity vout across iout through output to ref;
  constant wp : REAL := math_2_pi*fp;
  constant num: REAL_VECTOR := (0 => gain*wp*wp);
  constant den: REAL_VECTOR := (wp*wp, wp/qp, 1.0);
begin
  vout == vin'Ltf(num, den);
end architecture One;
```





Outline

- ◆ Introduction
- ◆ Brief Overview of VHDL-AMS
- ◆ Basic Concepts: DAEs
- ◆ Systems with Conservation Semantics: Diode
- ◆ Mixed Technology: Diode with Self Heating
- ◆ Piecewise Defined Behavior: Compressor, Voltage Limiter
- ◆ Procedural Modeling: Weighted Summer
- ◆ Signal-Flow Modeling: Adder-Integrator, Conversions
- ◆ Solvability: Voltage Source, Signal Flow Amplifier
- ◆ Initial Conditions: Capacitor
- ◆ Implicit Quantities
- ◆ Mixed-Signal Modeling: Comparators, D/A Converter
- ◆ VHDL-AMS Model Execution
- ◆ Discontinuities: SCR, Voltage Limiter, Bouncing Ball
- ◆ Time-Dependent Modeling: Sinusoid Voltage Source
- ◆ Frequency Domain Modeling: Current Source, Filter
- ◆ Noise Modeling: Resistor, Diode
- ◆ Conclusion

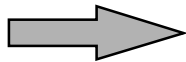



Noise Modeling


- ◆ Support for noise modeling in the frequency domain
- ◆ Noise source quantities allow a user to specify a noise spectrum
 - Power spectrum
 - Can depend on frequency by calling predefined function `FREQUENCY` in the definition of the noise spectrum
 - Can depend on operating point by including quantity names in the definition of the noise spectrum
 - Value of noise source quantity is 0.0 except during noise simulation

Resistor Model with Thermal Noise

```

library Disciplines;
use Disciplines.electrical_system.all;
use Disciplines.environment.all;
entity Resistor is
    generic (r: REAL);
    port (terminal p, m: electrical);
end entity Resistor;

```

 

```

architecture Noisy of Resistor is
    quantity v across i through p to m;
    quantity thns : REAL noise 4.0*ambient_temp*boltzmann/r;
begin
    assert r /= 0.0;
    i == v / r + thns;
end architecture Noisy;

```

- ◆ Resistor current is sum of ohmic current and thermal noise current represented by noise source quantity `thns`

Diode with Flicker Noise


```
architecture Noisy of Diode is
  quantity vd across id, ic through p to m;
  quantity qc: REAL;
  quantity flns: REAL noise kf * id**af / FREQUENCY;
  constant vt: REAL := 0.0258; -- thermal voltage
begin
  id == iss * (exp((vd-rs*id)/(n*vt)) - 1.0) + flns;
  qc == tt*id - 2.0*cj0 * sqrt(vj**2 - vj*vd);
  ic == qc'dot;
end architecture Noisy;
```

- ◆ Flicker noise current represented by noise source quantity `flns` depends on quiescent state diode current and is inversely proportional to the simulation frequency



Outline

- ◆ Introduction
- ◆ Brief Overview of VHDL-AMS
- ◆ Basic Concepts: DAEs
- ◆ Systems with Conservation Semantics: Diode
- ◆ Mixed Technology: Diode with Self Heating
- ◆ Piecewise Defined Behavior: Compressor, Voltage Limiter
- ◆ Procedural Modeling: Weighted Summer
- ◆ Signal-Flow Modeling: Adder-Integrator, Conversions
- ◆ Solvability: Voltage Source, Signal Flow Amplifier
- ◆ Initial Conditions: Capacitor
- ◆ Implicit Quantities
- ◆ Mixed-Signal Modeling: Comparators, D/A Converter
- ◆ VHDL-AMS Model Execution
- ◆ Discontinuities: SCR, Voltage Limiter, Bouncing Ball
- ◆ Time-Dependent Modeling: Sinusoid Voltage Source
- ◆ Frequency Domain Modeling: Current Source, Filter
- ◆ Noise Modeling: Resistor, Diode
- ◆ Conclusion

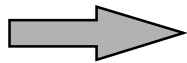



Conclusion

- ◆ VHDL 1076.1 extends VHDL 1076 to the continuous domain
 - Keeps VHDL 1076 fundamental philosophy
 - Adds support for continuous and mixed continuous/discrete behavior
 - Builds on solid mathematical foundations
- ◆ VHDL-AMS is equally applicable to electrical and non-electrical domains
 - Mixed discipline
 - Control systems
- ◆ Two separate but related standards
 - IEEE Std. 1076-1993 for digital (event-driven) applications
 - IEEE Std. 1076.1-1999 for digital AND mixed-signal applications



Additional Information

- ◆ 1076.1 Working Group
 - Reporting to Design Automation Standards Committee (DASC) of IEEE Computer Society
- ◆ Email reflector vhdl-ams@eda.org
 - All requests to owner-vhdl-ams-request@eda.org
- ◆ Web site at <http://www.eda.org/vhdl-ams/>




Part II:

**VHDL-AMS
in Practical Applications**



Outline

 

- ◆ VHDL-AMS Modeling Guidelines
- ◆ VHDL-AMS Modeling Techniques
 - IC Applications
- ◆ Modeling at Different Levels of Abstraction
 - Telecom Applications
- ◆ Modeling of Multi-Disciplinary Systems
 - Automotive Applications
- ◆ MEMS Modeling Using the VHDL-AMS Language



Overview of VHDL-AMS Modeling Guidelines

- ◆ Package Architecture
- ◆ Types and Subtypes
- ◆ Natures and Subnatures
- ◆ Physical and Mathematical Constants
- ◆ Simulation Control



VHDL-AMS Modeling Utilities

- ◆ VHDL-AMS modeling requires common set of utilities and styles
 - Avoid needless duplication
 - Promote interoperation
 - Establish coordinated family of dialects for specialized modeling applications


- ◆ Initial group effort has concentrated on data modeling
 - Behavioral modeling will follow

- ◆ Common Modeling Utilities
 - Packages
 - Types/Subtypes
 - Natures/Subnatures
 - Physical/Mathematical Constants
 - Simulation Control



Packages

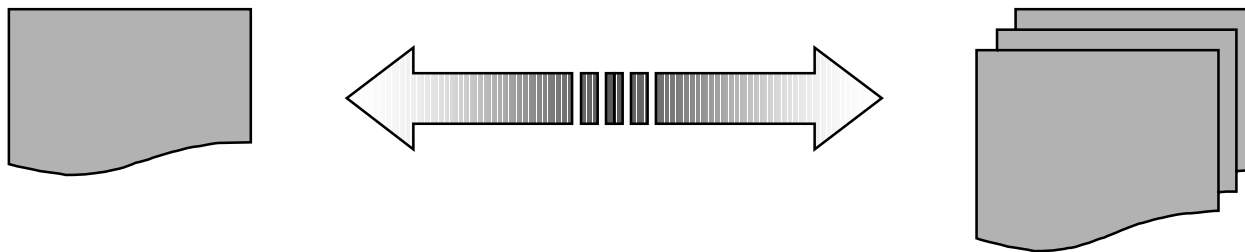
- ◆ Domain abstractions implemented as package(s)
- ◆ Packages provide convenient set of abstractions and operations to compose models
 - Quickly
 - Consistently
 - Limited domain expertise
- ◆ Issue: What level of package aggregation/segmentation?





Package Architecture

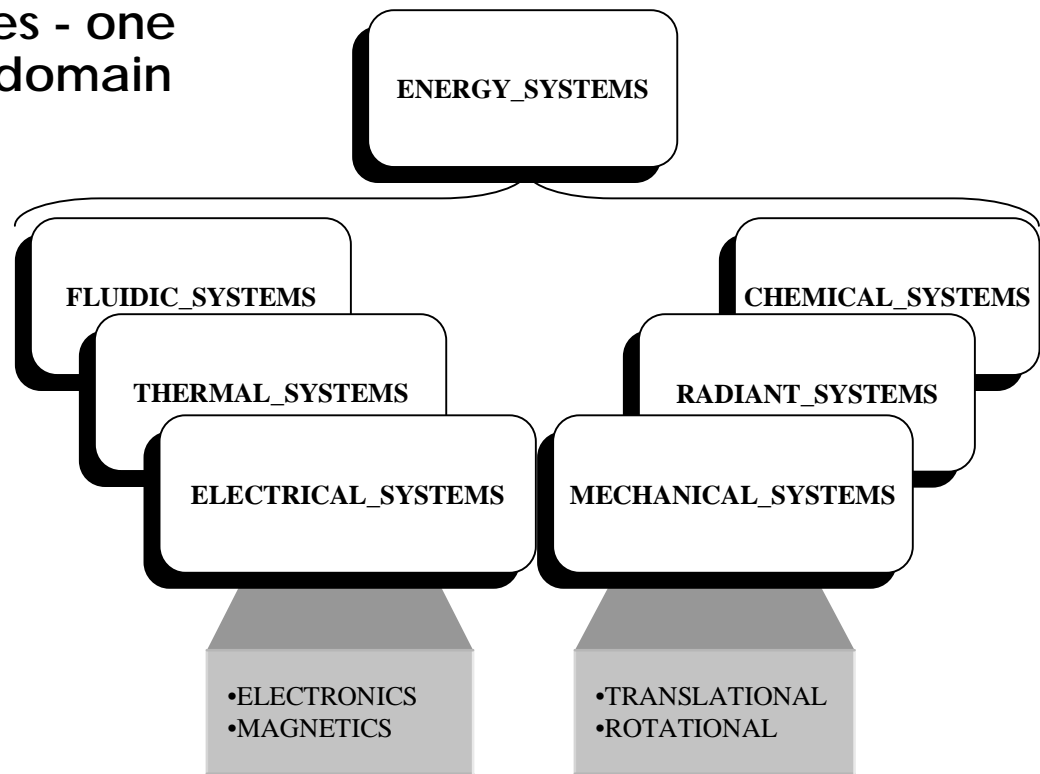- ◆ **Proposal: Two-tier package hierarchy**
 - Single package containing declarations common across energy domains
 - Collection of packages - one package per energy domain
- ◆ **Segmentation**
 - Allows separate communities of interest per discipline
- ◆ **Aggregation**
 - Allows variety of composite system modeling by "mixing-and-matching"





MEMS VHDL-AMS Modeling

```
library IEEE;  
use IEEE.MATH_REAL.all;  
use IEEE.ELECTRICAL_SYSTEMS.all;  
use IEEE.MECHANICAL_SYSTEMS.all;  
entity LOUDSPEAKER is  
    .....
```

port (
 terminal PLUS, MINUS : ELECTRICAL;
 terminal CONE : TRANSLATIONAL);
end entity LOUDSPEAKER;

Add mathematical constants/functions

- MATH_2_PI = 2π

Add electrical domain

- ELECTRICAL
- FLUX_DENSITY

Add mechanical domain

- TRANSLATIONAL
- MASS
- STIFFNESS
- DAMPING



Across/Through Quantities

Energy Domain	Across Quantity	Through Quantity
Electrical	Voltage	Current
Magnetic	MMF	Magnetic Flux
Translational	Displacement	Force
Rotational	Angle	Torque
Fluidic	Pressure	Flow Rate
Thermal	Temperature	Heat Flux

```

nature ELECTRICAL is
  VOLTAGE across
  CURRENT through
  ELECTRICAL_REF reference;

```

```

nature ROTATIONAL is
  ANGLE across
  TORQUE through
  ROTATIONAL_ref reference;

```

```

nature MAGNETIC is
  MMF across
  FLUX through
  MAGNETIC_REF reference;

```

```

nature FLUIDIC is
  PRESSURE across
  FLOW_RATE through
  FLUIDIC_REF reference;

```

```

nature TRANSLATIONAL is
  DISPLACEMENT across
  FORCE through
  TRANSLATIONAL_REF reference;

```

```

nature THERMAL is
  TEMPERATURE across
  HEAT_FLUX through
  THERMAL_REF reference;

```




VHDL-AMS Types and Subtypes

- ◆ Natures define types for across and through branch quantities
 - **VOLTAGE, CURRENT, DISPLACEMENT, VELOCITY, FORCE, and ANGLE** - examples of types
- ◆ Strong data typing is common aspect of complex software programming and digital system modeling
- ◆ Strong data typing (predefined and user defined) is a major aspect of VHDL
- ◆ VHDL-AMS limits use of strong data typing - emphasizes floating point types
 - Model analytic continuous functions of time
 - Support practical implementation issues of analog solver



VHDL-AMS Types and Subtypes

 - ◆ Quantities must be of a floating point type
 - Across and Through types in nature declarations must be of a floating point type
- ◆ Issue: What level of floating point types/subtype aggregation and/or segmentation?



- ◆ Proposal: Do not impose strong data typing
 - Floating point types are declared as subtypes of single parent type **REAL**



VHDL-AMS Types and Subtypes

Sample common declarations

```
-- electrical_systems
```

```
subtype VOLTAGE is REAL tolerance "DEFAULT_VOLTAGE";
```

```
subtype CURRENT is REAL tolerance "DEFAULT_CURRENT";
```

```
subtype CHARGE is REAL tolerance "DEFAULT_CHARGE";
```

```
-- mechanical_systems
```

```
subtype DISPLACEMENT is REAL tolerance "DEFAULT_DISPLACEMENT";
```

```
subtype FORCE is REAL tolerance "DEFAULT_FORCE";
```

```
subtype VELOCITY is REAL tolerance "DEFAULT_VELOCITY";
```

```
subtype MASS is REAL tolerance "DEFAULT_MASS";
```

```
subtype STIFFNESS is REAL tolerance "DEFAULT_STIFFNESS";
```

```
subtype DAMPING is REAL tolerance "DEFAULT_DAMPING";
```

```
-- fluidic_systems
```

```
subtype PRESSURE is REAL tolerance "DEFAULT_PRESSURE";
```

Package: ENERGY_SYSTEMS

- ◆ Physical and mathematical constants often used in modeling coupled-energy systems are defined in package **ENERGY_SYSTEMS**

```
package ENERGY_SYSTEMS is
-- common scaling factors
constant PICO  : REAL := 1.0e-12;
constant NANO  : REAL := 1.0e-9;
constant MICRO : REAL := 1.0e-6;
constant MILLI : REAL := 1.0e-3;
      ●●●
constant KILO  : REAL := 1.0e+3;
constant MEGA  : REAL := 1.0e+6;
constant GIGA  : REAL := 1.0e+9;

-- permittivity of vacuum <FARADS/METER>
constant EPS0 : REAL := 8.8542*PICO;

-- permeability of vacuum <HENRIES/METER>
constant MU0  : REAL := 4.0e-6 * MATH_PI;

-- electron charge <COULOMB>
constant Q    : REAL := 1.60218e-19;

-- acceleration due to gravity <METERS/SQ_SEC>
constant GRAV : REAL := 9.81;
end package ENERGY_SYSTEMS;
```



Package: - ELECTRICAL_SYSTEMS

- ◆ Defines commonly used quantity types and defining nature for electrical domain

```
library IEEE;
use IEEE.ENERGY_SYSTEMS.all;
package ELECTRICAL_SYSTEMS is
  -- subtype declarations
  subtype VOLTAGE is REAL tolerance "DEFAULT_VOLTAGE";
  subtype CURRENT is REAL tolerance "DEFAULT_CURRENT";
  subtype CHARGE is REAL tolerance "DEFAULT_CHARGE";
  subtype RESISTANCE is REAL tolerance "DEFAULT_RESISTANCE";
  subtype CAPACITANCE is REAL tolerance "DEFAULT_CAPACITANCE";

  -- nature declarations
  nature ELECTRICAL is VOLTAGE across CURRENT through
                      ELECTRICAL_REF reference;

  -- alias declarations
  alias GROUND is ELECTRICAL_REF;
end package ELECTRICAL_SYSTEMS;
```



Package: MECHANICAL_SYSTEMS

- ◆ Defines commonly used quantity types and defining nature for mechanical domain

```
library IEEE;
use IEEE.ENERGY_SYSTEMS.all;
package MECHANICAL_SYSTEMS is
  -- subtype declarations
  subtype DISPLACEMENT is REAL tolerance "DEFAULT_DISPLACEMENT";
  subtype FORCE is REAL tolerance "DEFAULT_FORCE";
  subtype VELOCITY is REAL tolerance "DEFAULT_VELOCITY";
  subtype ACCELERATION is REAL tolerance "DEFAULT_ACCELERATION";
  subtype MASS is REAL tolerance "DEFAULT_MASS";
  subtype STIFFNESS is REAL tolerance "DEFAULT_STIFFNESS";
  subtype DAMPING is REAL tolerance "DEFAULT_DAMPING";

  -- nature declarations
  nature TRANSLATIONAL is DISPLACEMENT across FORCE through
                        TRANSLATIONAL_REF reference;

  -- alias declarations
  alias ANCHOR is TRANSLATIONAL_REF;
end package MECHANICAL_SYSTEMS;
```



Outline

- ◆ VHDL-AMS Modeling Guidelines
- ➔ ◆ VHDL-AMS Modeling Techniques
 - IC Applications
- ◆ Modeling at Different Levels of Abstraction
 - Telecom Applications
- ◆ Modeling of Multi-Disciplinary Systems
 - Automotive Applications
- ◆ MEMS Modeling Using the VHDL-AMS Language



Overview

- ◆ Technology and geometry parameters
 - Sharing of technology parameters
- ◆ Ambient temperature
 - Propagation through design hierarchy
- ◆ Global nets
 - Power distribution
 - Chassis ground



Technology and Geometry Parameters

- ◆ Semiconductors on a chip vary in geometry, but share technology parameters
- ◆ Want to share technology parameters among different instances of a device

- ◆ In SPICE:

* technology parameters specified with .MODEL card

```
.MODEL d d1234 is 1e-13 rs 10
```


...

```
d1 34 57 d1234
```

```
d2 23 45 d1234 1.5
```



 two instances, one with default area, the other with explicit area



same technology parameters for both instances



Sharing of Technology Parameters

- ◆ Represent the technology parameters as a generic of a record type
- ◆ For the diode we had:

```
generic (iss: REAL := 1.0e-14;  
        n, af: REAL := 1.0;  
        tt, cj0, vj, rs, kf: REAL := 0.0);
```


- ◆ Equivalent record type declaration

```
type DiodeModel is record  
    iss, n, rs, tt, cj0, vj, af, kf: REAL;  
end record;
```

- Declared in package `diode_pkg` for re-use

Revised Diode Architecture

```
architecture Noisy of Diode2 is
  quantity vd across id, ic through p to m;
  quantity qc: REAL;
  quantity flns: REAL noise model.kf*id**model.af / FREQUENCY;
  constant vt: REAL := boltzmann * ambient_temp / elec_charge;
begin
  id == area * model.iss * (exp((vd-model.rs*id)/(model.n*vt))
    - 1.0) + flns;
  qc == model.tt*id - 2.0*model.cj0 *
    sqrt(model.vj**2 - model.vj*vd);
  ic == qc'dot;
end architecture Noisy;
```

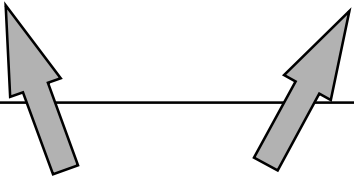

Handling of Defaults


- ◆ Declare a constructor function for an object of the record type
 - Function parameters are technology parameters with defaults
 - Return value has record type

```
function DiodeModelValue(  
    iss: REAL := 1.0e-14;  
    n, af: REAL := 1.0;  
    tt, cj0, vj, rs, kf: REAL := 0.0) return DiodeModel is  
begin  
    return DiodeModel'(iss, n, rs, tt, cj0, vj, af, kf);  
end function DiodeModelValue;
```

parameters ordered according to record type

Revised Diode Entity

```
library IEEE, Disciplines;
use Disciplines.electrical_system.all;
use Disciplines.environment.all;
use IEEE.math_real.all;
use work.diode_pkg.all;
entity Diode2 is
    generic (model: DiodeModel := DiodeModelValue;
            area: REAL := 1.0);
    port (terminal anode, cathode: electrical);
end entity Diode2;
```



- ◆ Generic `model` now has record type with default


```
use work.diode_pkg.all;
...
terminal n23, n34, n45, n57, ... : electrical;
constant d1234: DiodeModel :=
    DiodeModelValue(iss => 1.0e-13, rs => 10.0);
...
d1: entity Diode2 generic map (model => d1234)
    port map (anode => n34, cathode => n57);
d2: entity Diode2 generic map (model => d1234, area => 1.5)
    port map (anode => n23, cathode => n45);
...
d12: entity Diode2 generic map
    (model => DiodeModelValue(iss => 1.0e-15))
    port map (anode => ..., cathode => ...);
```

new functionality



Ambient Temperature: The Problem

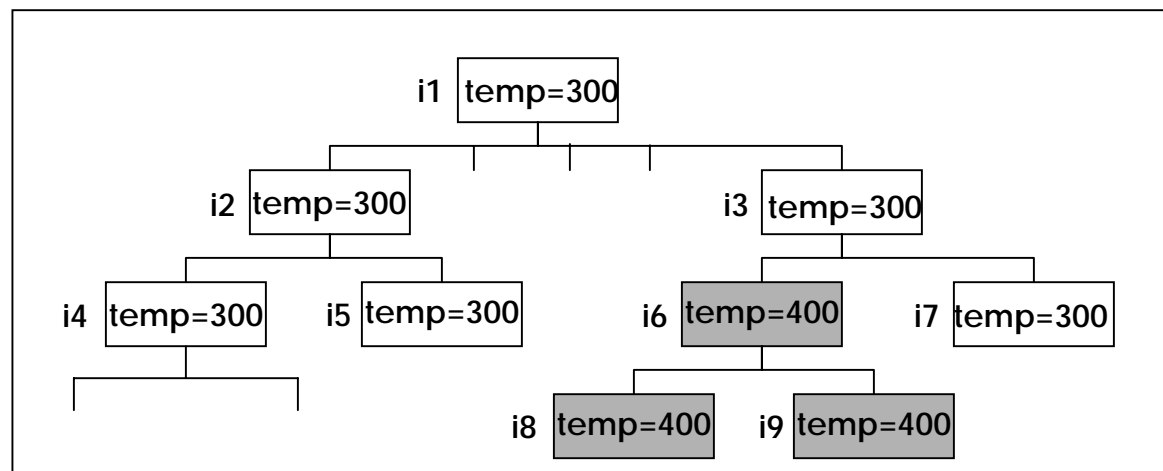- ◆ Most physics based models are temperature dependent
- ◆ For many applications dependency on ambient temperature is sufficient (no self heating) needed)
- ◆ Ambient temperature is the same in all or most instances of a design hierarchy






Ambient Temperature: The Solution


- ◆ Each entity has a generic named `temp` of type `REAL`
 - Its initial value is the ambient temperature from package environment
- ◆ Ambient temperature for a subtree of the design hierarchy is defined at the root of the subtree
- ◆ Temperature is passed through subtree by associating the generic `temp` of an instance as an actual with the formal `temp` of each subinstance

Ambient Temperature: Example

```
library Disciplines;
use Disciplines.environment.all;
entity e3 is
    generic (...;
        temp: REAL := ambient_temp);
    port (...);
end entity e3;
```


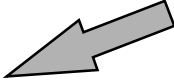
```
architecture one of e3 is
    component e6 is
        generic (...; temp: REAL); port (...);
    end component e6;
    component e7 is
        generic (...; temp: REAL); port (...);
    end component e7;
begin
    i6: e6 generic map (... , temp => 400.0) port map (...);
    i7: e7 generic map (... , temp => temp) port map (...);
end architecture one;
```



Defines temperature in
subtree rooted at i6
Propagates temperature
to subtree rooted at i7




Global Nets

- ◆ Power distribution and ground nets are typically not drawn in a schematic
 - These nets are global nets
- ◆ A global nets can be represented in VHDL-AMS as a terminal declared in a package
- ◆ A VHDL-AMS model that makes this terminal visible does not need a port for power or ground
 - VHDL-AMS model corresponds exactly to schematic
- ◆ Properties of global net must be defined exactly once, typically in the root instance of a design hierarchy
 - Voltage/impedance for power distribution nets
 - Impedance to electrical reference for ground nets



Global Nets: Example

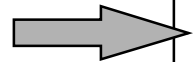

```
library Disciplines;  
use Disciplines.electrical_system.all;  
package PowerDistribution is  
    terminal vcc, vee, chassis: electrical;  
end package PowerDistribution;
```

```
library Disciplines;  
use Disciplines.electrical_system.all;  
use work.PowerDistribution.all;  
entity Inverter is  
    port (terminal inp, outp: electrical);  
end entity Inverter;
```


only functional
terminals declared




```
architecture one of Inverter is  
    constant qnpn: BjtModel := BjtModelValue(kind => npn);  
begin  
    r1: entity resistor generic map (r => 1.0e3)  
        port map (p => vcc, m => outp);  
    t1: entity bjt generic map (model => qnpn)  
        port map (collector => outp, base => inp,  
                emitter => chassis);  
end architecture one;
```




Global Nets: Test Bench



```
library Disciplines;  
use Disciplines.electrical_system.all;  
use work.PowerDistribution.all;  
entity testbench is  
end entity testbench;
```




```
architecture example of testbench is  
    ...  
begin  
    -- define properties of global nets  
    vvcc: entity Vdc generic map (dc => 5.0)  
        port map (p => vcc, m => ground);  
    vvee: entity Vdc generic map (dc => 3.0)  
        port map (p => vee, m => ground);  
    rgnd: entity Resistor generic map (r => 10.0)  
        port map (p => chassis, m => ground);  
    cgnd: entity Capacitor generic map (c => 30.0e-12)  
        port map (p => chassis, m => ground);  
    ...  
    inv1: entity Inverter port map (inp => ..., outp => ...);  
end architecture example;
```

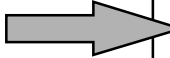




Outline

- ◆ VHDL-AMS Modeling Guidelines
- ◆ VHDL-AMS Modeling Techniques
 - IC Applications
-  ◆ Modeling at Different Levels of Abstraction
 - Telecom Applications
- ◆ Modeling of Multi-Disciplinary Systems
 - Automotive Applications
- ◆ MEMS Modeling Using the VHDL-AMS Language


A VCO from a Telecom Library

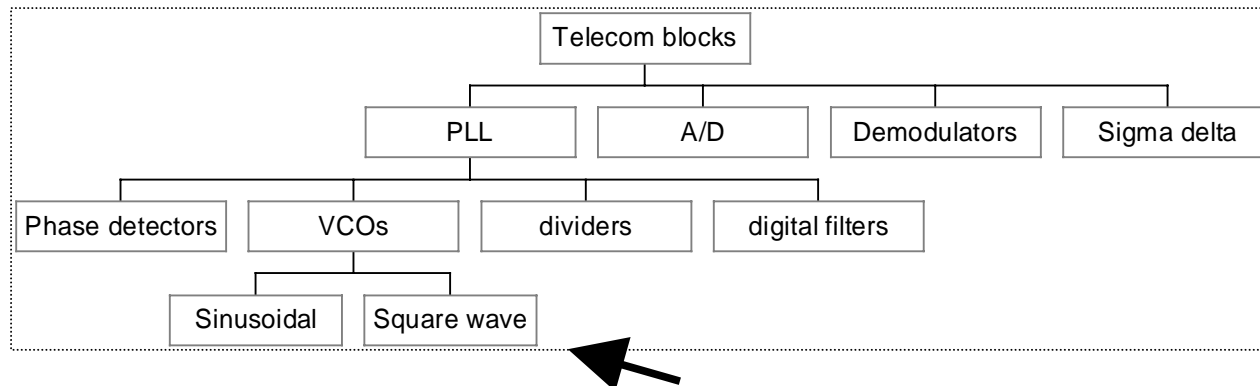- ◆ Why does the world need analog behavioral libraries?
 - Behavioral simulation reduces design cycle time
 - Creating verified, flexible, reusable models is time consuming
 - "Black box" models are not good enough
- ◆ Standard analog HDLs are the enabling technology
- ◆ The VCO is designed to be a member of a large, coordinated model set





The VCO in its Native Element


 


FM Demodulator using the PLL Model Set



Parameters of the VCO
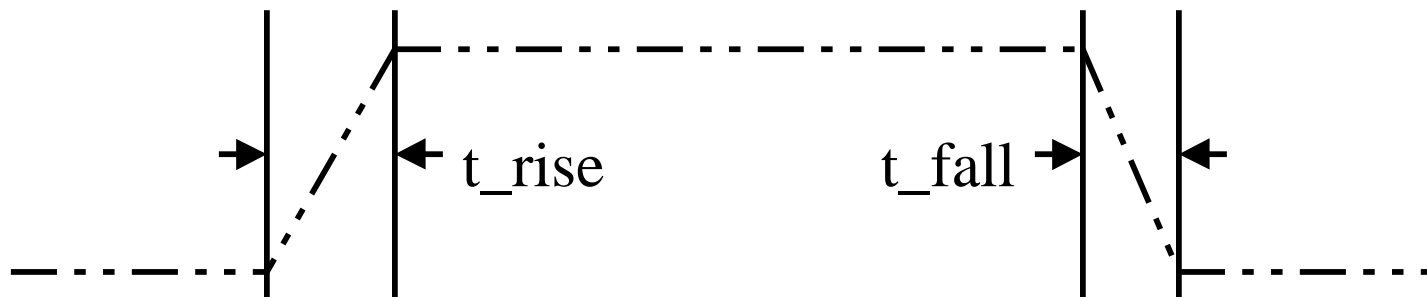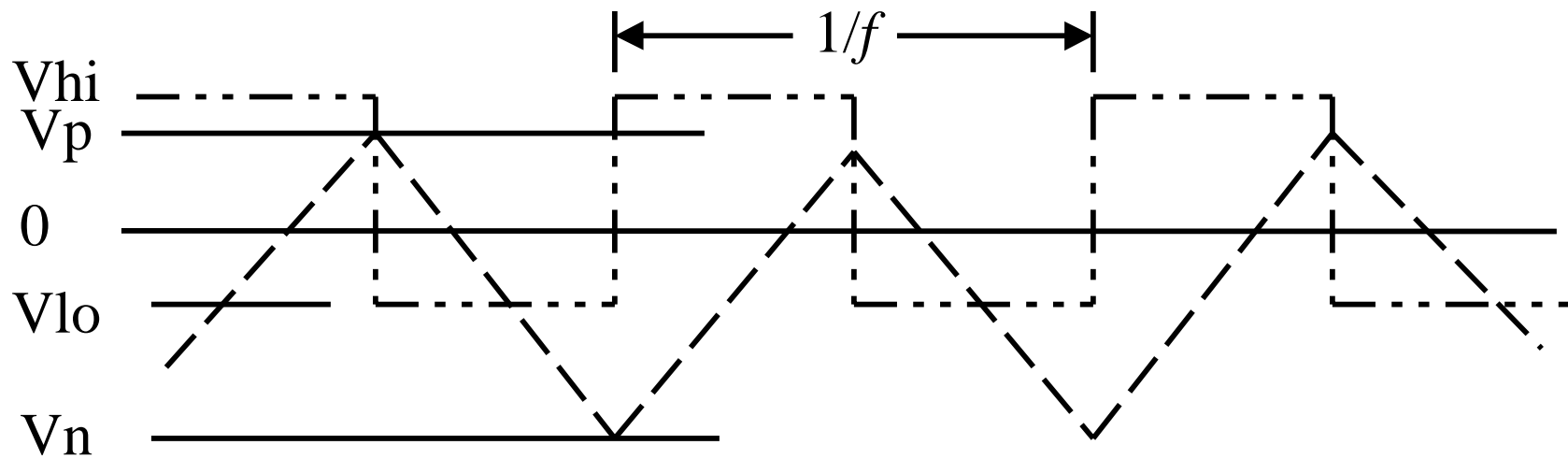
$$f = f_0 + K_v(v_{in} - V_{f0})/2\pi + K_{vv}(v_{in}^2 - V_{f0}^2)/2\pi$$





Theory of Operation

$$v_{out2} = \int_0^t A_{tot} dt \quad \text{the triangular wave}$$

Where:

$$A_{tot} = \quad \text{the instantaneous slope of the triangular wave}$$

When $v_{out1} = V_{hi}$:

$$k_1(v_{in} - V_{fo}) + k_{11}(v_{in}^2 - V_{fo}^2) + 2f_o(V_p - V_n)$$

When $v_{out1} = V_{lo}$:

$$- \left[k_1(v_{in} - V_{fo}) + k_{11}(v_{in}^2 - V_{fo}^2) + 2f_o(V_p - V_n) \right]$$

and:

$$k_1 = K_v(V_p - V_n) / \pi, \quad k_{11} = K_{vv}(V_p - V_n) / \pi$$



The Model

```
library IEEE, Disciplines;
use Disciplines.ElectroMagnetic_system.all, IEEE.math_real.all;

entity vco_sqr_tri_1_1 is
  generic (
    Vp      : real := 1.0;           -- High level of triangular waveform
    Vn      : real := -1.0;          -- Low level of triangular wavefor
    Vhi     : real := 5.0;           -- Output high level
    Vlo     : real := 0.0;           -- Output low
    V_f0    : real := 1.0;           -- Input voltage corresponding to f0
    f0      : real := 100.0e3;       -- Output center frequency
    fmin    : real := 10.0e3;        -- Minimum allowable output frequency
    fmax    : real := 200.0e3;       -- Maximum allowable output frequency
    kv      : real := 100.0e3;       -- VCO linear gain rad/s/V
    kvv     : real := 100.0e1;       -- VCO gain quadratic rad/s/V^2 (arch. a2 only)
    PHI     : real := 0.0;           -- Initial phase shift of the output
    t_rise  : real := 1.0e-9;        -- Rise time of the output
    t_fall  : real := 1.0e-9;        -- Fall time of the output
    R_ip    : real := 100.0e3;        -- Shunt input resistance
    C_ip    : real := 0.1e-12;       -- Shunt input capacitance (arch. a2 only)
    R_op    : real := 1.0e3;         -- Series output resistance
    C_op    : real := 0.1e-12 );     -- Shunt output capacitance (arch. a2 only)
  port (
    terminal p1, p2, p3, gnd : electrical );
  .
  .
  .
```



Check the Generics!

```


      .
      .
begin
  assert Vp>Vn          report "Vp must be > Vn.";
  assert Vhi>Vlo       report "Vhi must be > Vlo.";
  assert f0>0.0        report "f0 must be > zero.";
  assert Kv>0.0        report "Kv must be > zero.";
  assert Kvv>0.0       report "KVV must be > zero.";
  assert fmax>fmin     report "fmax must be > fmin.";
  assert fmax>=f0      report "fmax must be >= f0.";
  assert fmin<=f0      report "fmin must be <= f0.";
  assert PHI<=180.0 and PHI>=-180.0
                      report "PHI must > -180 and < 180 degrees.";
  assert t_rise>1.0e-12 report "t_rise should be > 1 ps." severity warning;
  assert t_fall>1.0e-12 report "t_fall should be > 1 ps." severity warning;
  assert R_ip>0.0      report "R_ip must be > zero.";
  assert R_op>0.0      report "R_op must be > zero.";
  assert C_ip>=0.0     report "C_ip should be >= zero." severity warning;
  assert C_op>=0.0     report "C_op should be >= zero." severity warning;
end entity vco_sqr_tri_1_1;
```



1st Architecture: Constants and Quantities

```
architecture a1 of vco_sqr_tri_1_1 is
  function ifelse (a: boolean; b,c:real) return real is begin
    if a then return b; else return c; end if;
  end;
  constant k1      : real := Kv*(Vp-Vn)/math_pi;           -- contrib to slope for 1 v in
  constant V1      : real := V_f0 + 2.0*math_pi*(fmax-f0)/Kv; -- Input corresponding to fmax
  constant V2      : real := V_f0 - 2.0*math_pi*(f0-fmin)/Kv; -- Input corresponding to fmin
  constant v_init2: real := Vp - (abs(PHI)/180.0)*(Vp-Vn);   -- initial value of vout2
  constant v_init1: real := ifelse(phi>=0.0 and phi<180.0, vlo, vhi);-- initial val of vout1
  constant dc      : real := (vhi+vlo)/2.0;                 -- dc of square wave

  quantity vin across iin through p1 to gnd; -- input branch
  quantity vin_lim: real; -- limited version of input
  quantity T_vout1 across i_out1 through p2; -- true output branch
  quantity T_vout3 across i_out3 through p3; -- triangel wave output
  quantity vout1: real := v_init1; -- square wave output
  signal svout1: real := v_init1; -- discrete form of vout1
  quantity vout2 : real := v_init2; -- tri output
  quantity Atot : real; -- integrand of tri generator
begin
  .
  .
  .
```

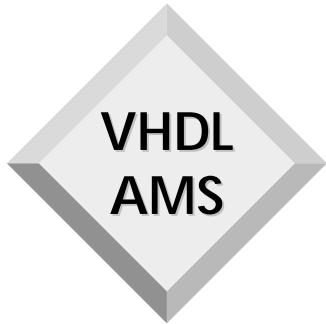

The Schmitt Trigger

```

      .
      .
begin
  schmitt: process
    variable low: boolean := v_init1 < dc;
  begin
    if low then
      wait until not vout2'above(Vn);
      svout1 <= vhi;
    else
      wait until vout2'above(Vp);
      svout1 <= vlo;
    end if;
    low := not low;
  end process;
  .
  .
  .
```



The Equations

```
.
.
.
-- input load
iin == vin / R_ip;
-- input limiter
If vin'above(V1) then
    Vin_lim == V1;
elsif vin'above(V2) then
    Vin_lim == vin;
else
    Vin_lim == V2;
end if;
-- limiter induced discontinuities
break on vin'above(V1), vin'above(V2);

vout1 == svout1'ramp(t_rise, t_fall);
Atot == sign(vout1-dc)* (k1*(Vin_lim-V_f0) + 2.0*f0*(Vp-Vn));
vout2 == Atot'integ + v_init2;
i_out1 == (T_vout1 - vout1) / R_op;
i_out3 == (T_vout3 - vout2) / R_op;
end architecture a1;
```



Adding Second Order Effects

```
library IEEE, Disciplines;
use Disciplines.ElectroMagnetic_system.all, IEEE.math_real.all;

entity vco_sqr_tri_1_1 is
  generic (
    Vp      : real := 1.0;           -- High level of triangular waveform
    Vn      : real := -1.0;          -- Low level of triangular wavefor
    Vhi     : real := 5.0;           -- Output high level
    Vlo     : real := 0.0;           -- Output low
    V_f0    : real := 1.0;           -- Input voltage corresponding to f0
    f0      : real := 100.0e3;       -- Output center frequency
    fmin    : real := 10.0e3;        -- Minimum allowable output frequency
    fmax    : real := 200.0e3;       -- Maximum allowable output frequency
    kv      : real := 100.0e3;       -- VCO linear gain rad/s/V
    kvv     : real := 100.0e1;        -- VCO gain quadratic rad/s/V^2 (arch a2 only)
    PHI     : real := 0.0;           -- Initial phase shift of the output
    t_rise  : real := 1.0e-9;        -- Rise time of the output
    t_fall  : real := 1.0e-9;        -- Fall time of the output
    R_ip    : real := 100.0e3;       -- Shunt input resistance
    C_ip    : real := 0.1e-12;        -- Shunt input capacitance (arch a2 only)
    R_op    : real := 1.0e3;         -- Series output resistance
    C_op    : real := 0.1e-12 );     -- Shunt output capacitance (arch a2 only)
  port (
    terminal p1, p2, p3, gnd : electrical );
  .
  .
  .
```



Check the Generics!

```

:
:
begin
  assert Vp>Vn          report "Vp must be > Vn.";
  assert Vhi>Vlo       report "Vhi must be > Vlo.";
  assert f0>0.0        report "f0 must be > zero.";
  assert Kv>0.0        report "Kv must be > zero.";
  assert Kvv>0.0       report "KVV must be > zero.";
  assert fmax>fmin     report "fmax must be > fmin.";
  assert fmax>=f0      report "fmax must be >= f0.";
  assert fmin<=f0      report "fmin must be <= f0.";
  assert PHI<=180.0 and PHI>=-180.0
    report "PHI must > -180 and < 180 degrees.";
  assert t_rise>1.0e-12 report "t_rise should be > 1 ps." severity warning;
  assert t_fall>1.0e-12 report "t_fall should be > 1 ps." severity warning;
  assert R_ip>0.0      report "R_ip must be > zero.";
  assert R_op>0.0      report "R_op must be > zero.";
  assert C_ip>=0.0     report "C_ip should be >= zero." severity warning;
  assert C_op>=0.0     report "C_op should be >= zero." severity warning;
end entity vco_sqr_tri_1_1;
```



2nd Architecture: Constants

```
architecture a2 of vco_sqr_tri_1_1 is
  function ifelse (a: boolean; b,c:real) return real is begin
    if a then return b; else return c; end if;
  end;
  function f2v (f: real) return real is
    constant fr: real := f-f0;
    constant tk: real := Kv + 2.0*Kvv*V_f0;
    constant kr: real := 8.0*math_pi*Kvv*fr;
  begin
    if kvv = 0.0 and kv/=0.0 then
      return V_f0 + 2.0*math_pi*fr/Kv;
    elsif tk**2 + kr >= 0.0 then
      return V_f0 + (-tk+SQRT(tk**2+kr))/(2.0*Kvv);
    else
      report "Please check values of Kv, Kvv, fmin and fmax. ";
    end if;
  end function f2v;

  constant k1      : real := Kv*(Vp-Vn)/math_pi;      -- contrib to slope for 1 v in
  constant k11     : real := Kvv*(Vp-Vn)/math_pi;
  constant V1      : real := f2v(fmax);              -- Input corresponding to fmax
  constant V2      : real := f2v(fmin);              -- Input corresponding to fmin

  :
```




Quantities

```

:
:
quantity vin across iin through p1 to gnd; -- input branch
quantity vin_lim: real; -- limited version of input
quantity T_vout1 across p2 to gnd;
quantity i_Rout, i_Cout through p2;
quantity i_Cgnd through gnd;
quantity T_vout3 across i_out3 through p3; -- triangle wave output
quantity vout1: real := v_init1; -- square wave output
signal svout1: real := v_init1; -- discrete form of vout1
quantity vout2 : real := v_init2; -- tri output
quantity Atot : real; -- integrand of tri generator
begin
:
:
:
```



The Schmitt Trigger is Unaltered

```
      .  
      .  
begin  
  schmitt: process  
    variable low: boolean := v_init1 < dc;  
  begin  
    if low then  
      wait until not vout2'above(Vn);  
      svout1 <= vhi;  
    else  
      wait until vout2'above(Vp);  
      svout1 <= vlo;  
    end if;  
    low := not low;  
  end process;  
  .  
  .  
  .
```




The Equations Change

```
.
.
-- input load
iin == vin / R_ip;
-- input limiter
If vin'above(V1) then
    Vin_lim == V1;
elsif vin'above(V2) then
    Vin_lim == vin;
else
    Vin_lim == V2;
end if;
-- limiter induced discontinuities
break on vin'above(V1), vin'above(V2);

vout1 == svout1'ramp(t_rise, t_fall);
Atot == sign(vout1-dc)* (k1*(Vin_lim-V_f0) + 2.0*f0*(Vp-Vn))
      + k11*(Vin_lim**2 - V_f0**2);
vout2 == Atot'integ + v_init2;
i_Rout == (T_vout1 - vout1) / R_op;
i_Cout == C_op * T_vout1'dot;
i_Cgnd == -i_Cout;
i_out3 == (T_vout3 - vout2) / R_op;
end architecture a2;
```



Outline

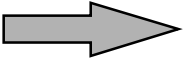- ◆ VHDL-AMS Modeling Guidelines
- ◆ VHDL-AMS Modeling Techniques
 - IC Applications
- ◆ Modeling at Different Levels of Abstraction
 - Telecom Applications
-  ◆ Modeling of Multi-Disciplinary Systems
 - Automotive Applications
- ◆ MEMS Modeling Using the VHDL-AMS Language



Overview

- ◆ Introduction
- ◆ Use of Mixed Domain - Mixed Level Models
- ◆ Control Design for Revolving Load
- ◆ Plant Model for Component Design
- ◆ Approach Towards Unified Modeling, Practical Implications
- ◆ Conclusion



Modeling of Multi-Disciplinary Systems

- ◆ **Mixed domain-modeling**
 - Combining different engineering disciplines (e.g., control, mechanics, hydraulics)

- ◆ **Mixed level-modeling**
 - Combining different levels of abstraction (e.g., behavioral model of plant, behavioral model of controller and detailed model of amplifier)




Component Library Using VHDL-AMS

- ◆ **Documentation**
 - VHDL-AMS allows precise behavioral description including discontinuous behavior
- ◆ **Modeling**
 - Single-source
 - Detailed vs. abstract model can be verified
- ◆ **Simulation**
 - All simulators are optimized towards a special-purpose (e.g., electronic, hydraulic, control, real-time)
 - Unique semantic allows conversion into many foreign (non-native) simulators



Use of Mixed-Domain/Mixed-Level (1)

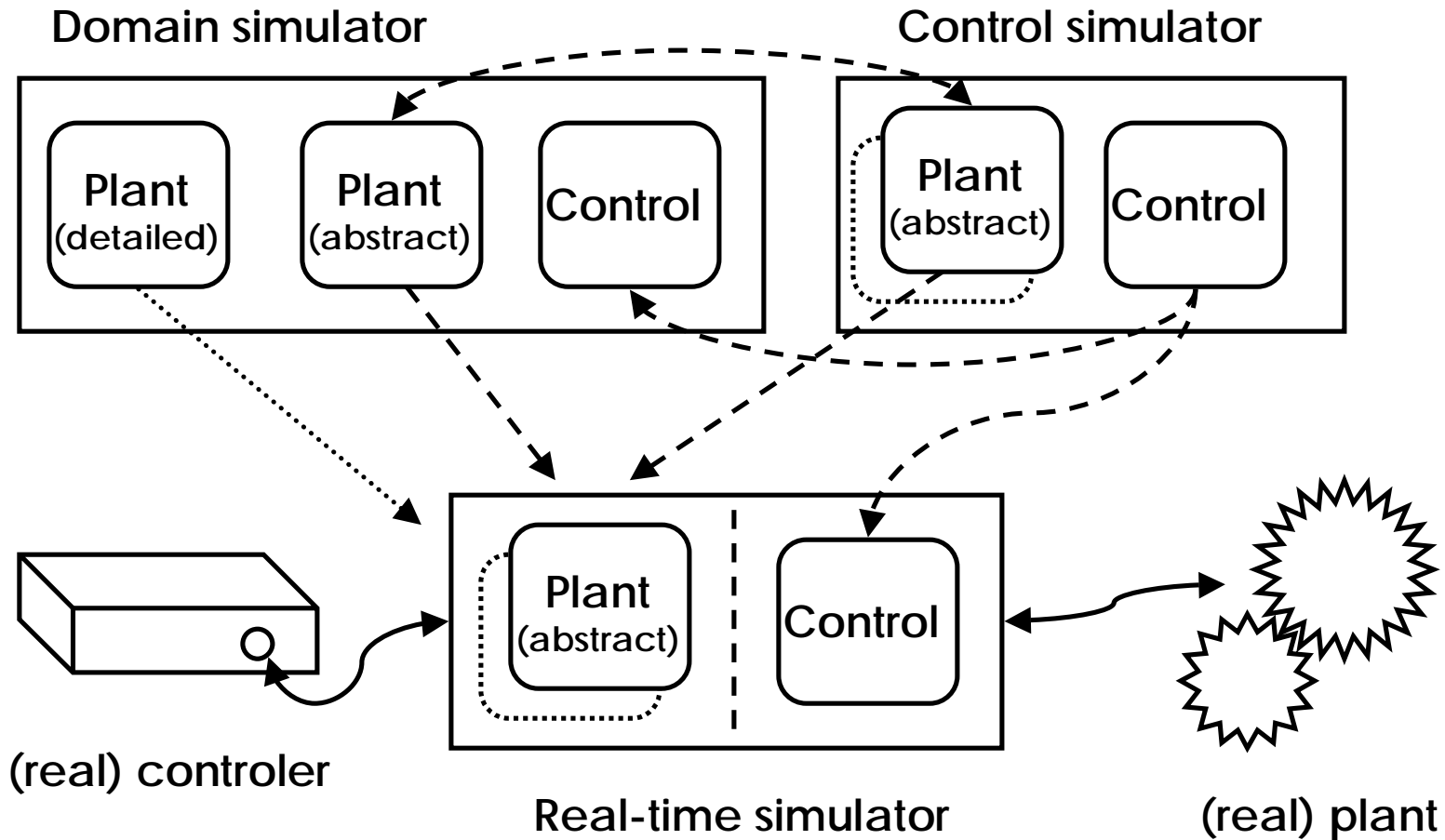
Controler and plant design and validation






Use of Mixed-Domain/Mixed-Level (2)

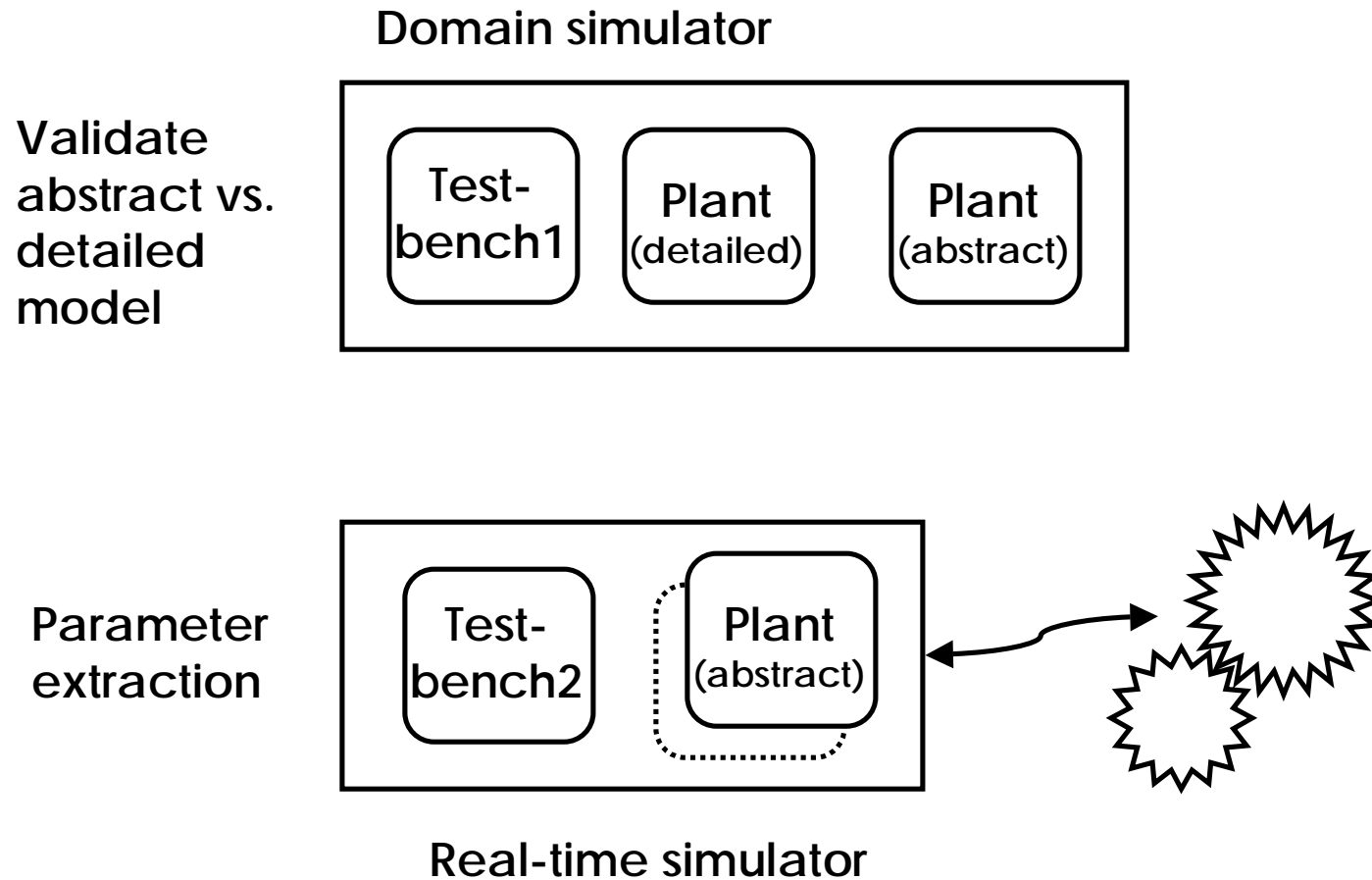
Model validation and parameter extraction




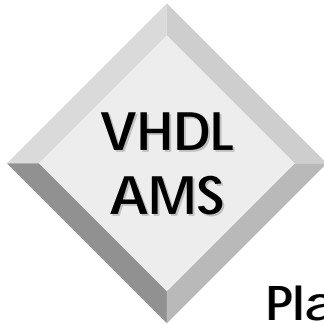

Controler Design for Revolving Load

 
Plant model as vehicle for controler design and verification
(reuse of detailed mechanical component model)



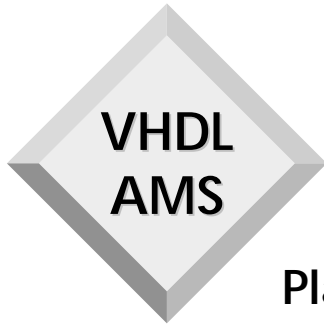

Controler Design for Revolving Load

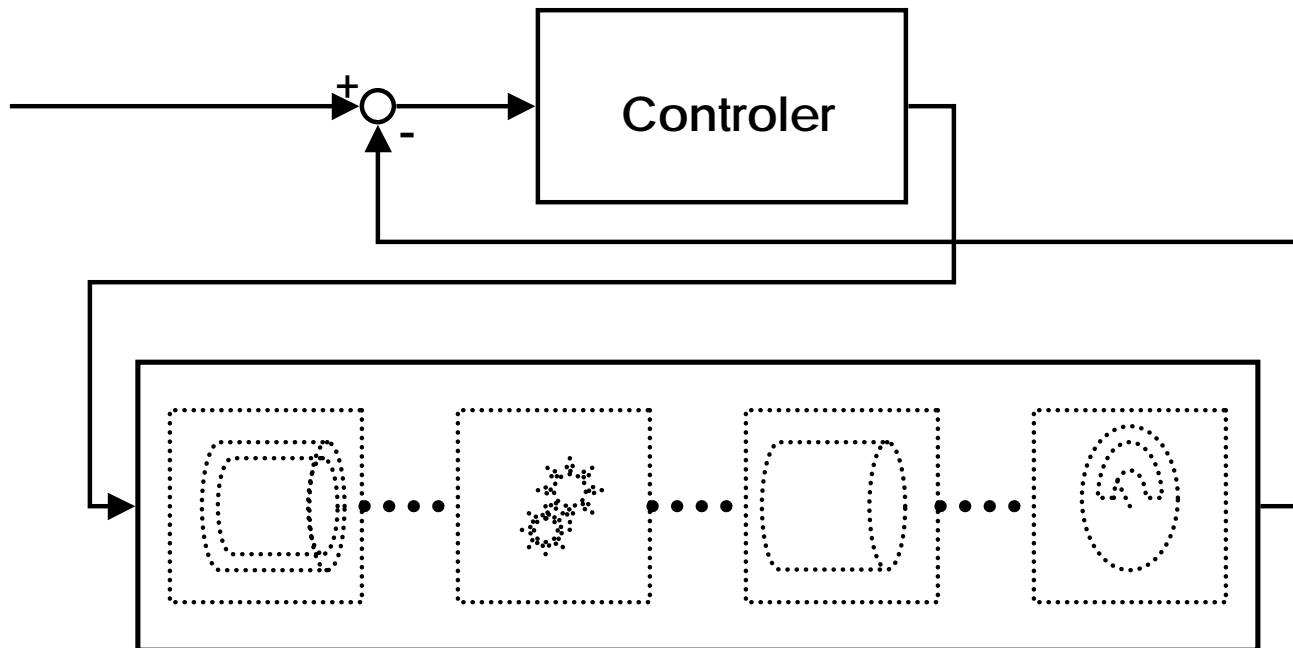Plant model as vehicle for controler design and verification
(abstract plant model, verified vs. detailed model)




**abstract (behavioral) model of revolving load
including backlash and stick/slip friction**
(VHDL-AMS source code see Appendix)



Revolving Load: Stick/Slip-Friction

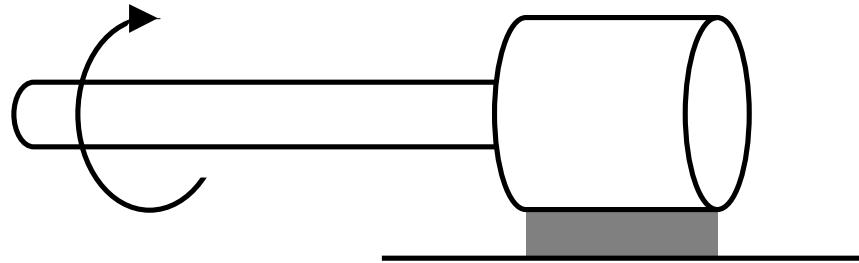m: Momentum
p: Angular position
w: Angular velocity
dw: Angular acceleration




$$p = \int w \, dt$$

IF motion_mode = slip USE

$$w = \int ((m - m_{\text{slip}} \bullet \text{sign}(w)) / j) \, dt$$

if motion_mode = stick USE

$$w = 0.0$$

 


Revolving Load: Stick/Slip-Friction

Process which determines the motion mode of the load
(toggles between stick and slip motion)

```
motion_ctrl: process
begin
    motion_mode <= stick;      -- load sticks
    wait until m_load`Above(m_stick)  -- wait until abs(m)<m_stick
    or not m_load`Above(-m_stick);

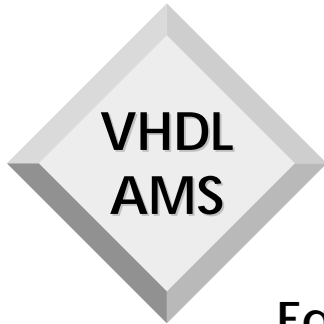    motion_mode <= slip;      -- load slips
    wait on w_load`Above(0.0)  -- wait until w=0 and abs(m)<m_slip
    until not m_load`Above(m_slip) and m_load`Above(-m_slip);
end process motion_ctrl;
```



Revolving Load: Stick/Slip-Friction

Equations of motion depending on the motion mode

```
p_load'DOT == w_load;           -- p = integral of w


if motion_mode = slip use
  -- w = integral of ((m - sign(w) * m_slip) / j)
  w_load'Dot == calc_internal_momentum(m_load,
                                       w_load'Above(0.0), m_slip) / j_load;
else
  w_load == 0.0;
end use;

break on motion_mode;         -- restart analog kernel
```



Simulation Results of Stick/Slip-Friction

 The simulation results feature only the stick/slip friction position on the load (2.) with sinusoidal momentum (1.)







Revolving Load: Backlash in Gear-Box

Process features only one side of the gap
(for details see appendix)
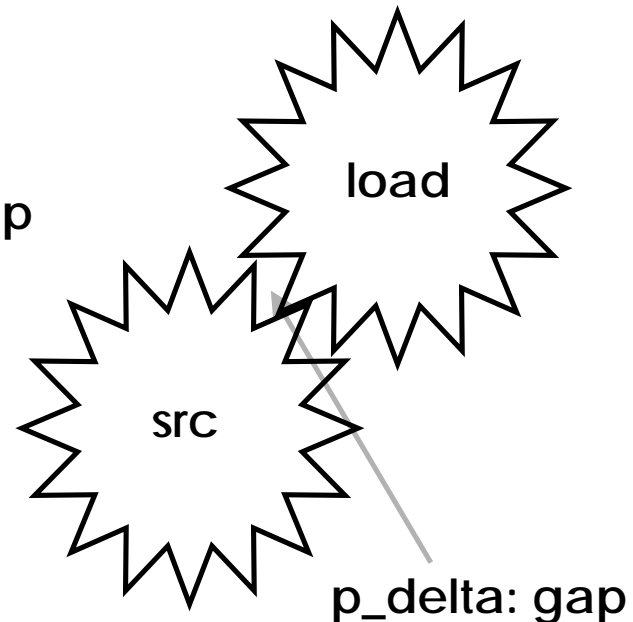
```
connection_ctrl: process
begin
    connection_mode <= loose;
    wait until p_src'Above(p_load)
    connection_mode <= coupled;
    break w_src => ... ,
        w_load => ... ;
    wait dw_load'Above(dw_src));
end process connection_ctrl;
```




src: electrical motor

 


Simulation Results of Backlash

 Results feature the position of load (1.), electrical rotor (2.) and status of backlash (3.) [loose = 0, connected otherwise]




Plant Modeling for Component Design

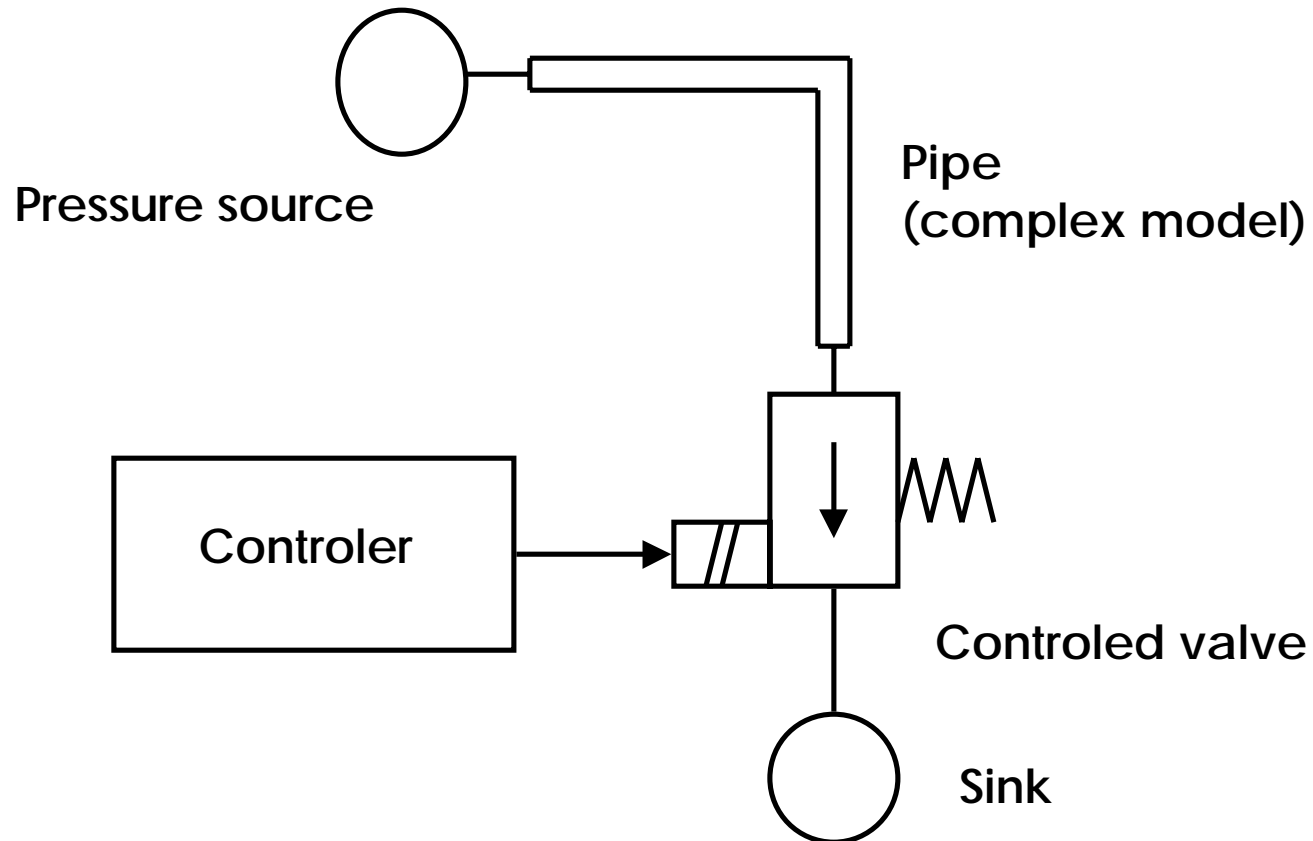Analysis of plant should reveal destroying effects on valve and pipe due to cavitation (domains: Hydraulics, mechanics and control)



Including Multi Body Systems

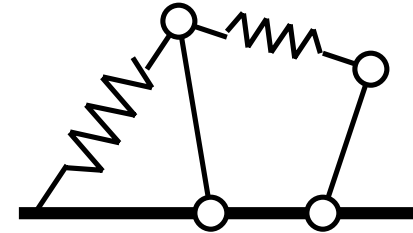


- ◆ Natural description is topology and geometrical information
 - consisting of joints, masses, links, springs, etc.
- ◆ Most simulators never derive a fixed system of differential algebraic equations (DAE) but determine the equations on the fly (during runtime)
- ◆ Integration of this models via procedural interface. Simulator vendor distributes library for
 - setting up the system (initialization)
 - derive residual of DAE, or derivative of state variables
 - derive output values (from state variables)



Scenario for Model Exchange

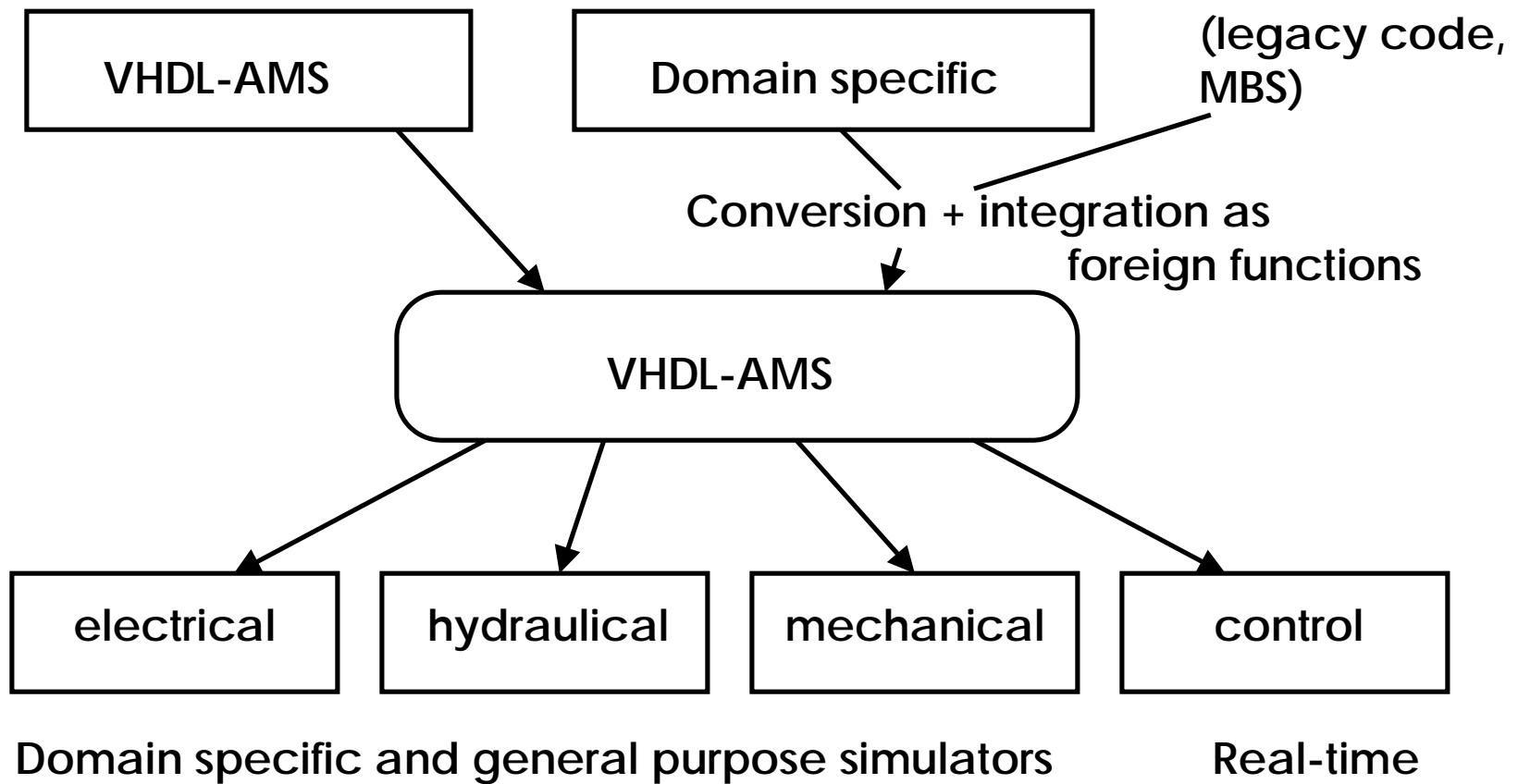This scenario is supported by European car makers and supplies, partially funded by the EC (BRITE-EURAM-Projects TOOLSYS and ODECOMS)





Approach Towards Unified Modeling (1)

- ◆ VHDL-AMS is a powerful and large language
- ◆ For most mixed-domain modeling only few concepts from (event-driven) VHDL are necessary
- ◆ Most continuous simulators have little or no support of the complex event-driven features
- ◆ Its usage with other than native VHDL-AMS simulators needs conversion
 - these conversion is simple, if only the basic concepts of event-driven modeling are permitted, and
 - a tiny kernel for these basic features is provided



Approach Towards Unified Modeling (2)

- ◆ **VHDL-AMS subset (proposal)**
 - (event-driven) VHDL is pretty much restricted to “synthesis-able” VHDL (e.g. IEEE PAR 1076.6)
 - no history information or delays on signals
 - no memory allocation
 - no global variables

- ◆ **Further restrictions for real-time simulation**
(and simulators only supporting ordinary differential equations)
 - no conservative communication (no nodes, terminals)
 - only equations of type
 - $q_i = f(q_1, \dots)$
 - $q_k' = g(q_1, \dots)$
 - equations of type 1 must be sortable



Approach Towards Unified Modeling (3)

- ◆ Modeling discontinuous behavior needs careful design
 - otherwise portability is difficult to achieve

- ◆ Style guide must be developed
 - standard natures, global parameters
 - standard concepts (slip/stick, bouncing ball)
 - never use discontinuous functions (e.g., $\text{sign}(x)$)
but
 - if x above(0.0) use ...
 - Coupling elements and defined communication
mechanism between domains
 - ...



Conclusion

- ◆ Automotive industry is using mixed-domain/mixed-level modeling for design and validation
- ◆ The language is an important step towards unified modeling
- ◆ Further steps are necessary (modeling techniques)
- ◆ VHDL-AMS subset is needed for many applications (e.g., real-time)
- ◆ Experiments demonstrate the suitability for many applications



Appendix: VHDL-AMS Source Code of Revolving Load

- ◆ Example features an abstract (behavioral) model of the revolving load (see above)
- ◆ Inputs: Momentum on armature of motor (m_src)
 Momentum on load (m_load)
- ◆ Output: Position of load (p_load)
- ◆ Processes: motion control (stick/slip),
 coupling control (loose, coupled ...)
- ◆ Equations: Equations of motion



Plant Model: Revolving Load

VHDL-AMS Source Code No. 1

```
ENTITY revolving_load IS
  GENERIC (
    j_src: REAL := 1.0;      -- inertia of electrical motor
    j_load: REAL := 1.0;    -- inertia of load
    m_slip: REAL := 0.01;   -- friction (on load) during slip mode
    m_stick: REAL := 0.1;   -- friction (on load) during stick mode
    delta_p: REAL := 0.034  -- gap between electrical motor and load (angle)
  );
  PORT (
    QUANTITY m_src : IN REAL; -- momentum generated by electrical motor
    QUANTITY m_load : IN REAL; -- outer momentum (not from electrical motor)
                                -- on load
    QUANTITY p_load : OUT REAL -- rotational position of load
  );
END ENTITY revolving_load;
```



Plant Model: Revolving Load

VHDL-AMS Source Code No 2

```
ARCHITECTURE behavioral OF revolving_load IS
  QUANTITY p_src: REAL; -- rotational position of electrical motor
  QUANTITY w_src: REAL; -- rotational velocity of electrical motor
  QUANTITY dw_src: REAL; -- rotational acceleration of electrical motor
  QUANTITY w_load: REAL; -- rotational velocity of load
  QUANTITY dw_load: REAL; -- rotational acceleration of load (always
    -- calculated as if connection_mode = loose)
  -- slip_type defines, if the load sticks or slips
  TYPE slip_type IS ( stick, slip );
  SIGNAL motion_mode: slip_type; -- handles slip/stick friction status
  -- connection_type defines the status of the connection between the
  -- electrical motor and load due to the backlash:
  -- loose : no connection
  -- coupled_low: connected and p_src = p_load
  -- coupled_high: connected and p_src + delta_p = p_load
  TYPE connection_type IS ( loose, coupled_low, coupled_high );
  SIGNAL connection_mode: connection_type; -- handles connection status

  -- further quantities are for internal use
  QUANTITY m_load_ext: REAL; -- external momentum on load
  QUANTITY dw_connected: REAL; -- rotational acceleration connected inertia
    -- ( always calculated as if connection_mode = coupled)
```



Plant Model: Revolving Load

VHDL-AMS Source Code No 3

```
-- calc_internal_momentum derives internal momentum
-- given the external momentum (m) subtracting slip friction m_slip
-- or returning 0.0 if motion_mode = stick
FUNCTION calc_internal_momentum(motion_mode: slip_type; m: REAL;
    direction: BOOLEAN; m_slip: REAL)
    RETURN REAL IS
BEGIN
    IF ( motion_mode = slip ) THEN
        IF direction THEN RETURN m - m_slip;
        ELSE RETURN m + m_slip; END IF;
    ELSE
        RETURN 0.0;
    END IF;
END;
```



Plant Model: Revolving Load

VHDL-AMS Source Code No. 4

```
BEGIN
```

```
-- motion_ctrl determines the motion_mode between slip and stick mode
-- (toggles between stick and slip motion)
motion_ctrl: PROCESS
BEGIN
    motion_mode <= stick;           -- load sticks
                                   -- wait until abs(m) < m_stick
    WAIT UNTIL m_load_ext'ABOVE(m_stick) OR NOT m_load_ext'ABOVE(-m_stick);
    motion_mode <= slip;           -- load slips
    WAIT ON w_load'ABOVE(0.0)      -- wait until w = 0 and abs(m) < m_slip
        UNTIL NOT m_load_ext'ABOVE(m_slip) AND m_load_ext'ABOVE(-m_slip);
END PROCESS motion_ctrl;

BREAK ON motion_mode;            -- notice discontinuity
```



Plant Model: Revolving Load

VHDL-AMS Source Code No. 5

```
-- connection_ctrl determines the connection_mode due to backlash,  
-- toggles between loose and connected (on low or high bound)  
connection_ctrl: PROCESS  
BEGIN  
    connection_mode <= loose;  
    WAIT UNTIL p_src'ABOVE(p_load) OR NOT p_src'ABOVE(p_load - delta_p);  
    IF p_src'ABOVE(p_load) THEN          -- p_src touches p_load  
        connection_mode <= coupled_low; -- connected on low bound  
    ELSE                                  -- p_src touches p_load - delta_p  
        connection_mode <= coupled_high; -- connected on high bound  
    END IF;  
    -- calculate new common velocities w_src = w_load (reset state variables)  
    BREAK w_src => ((j_src * w_src + j_load * w_load) / (j_src + j_load)),  
           w_load => ((j_src * w_src + j_load * w_load) / (j_src + j_load));  
    -- if acceleration of (individual) objects fulfill condition below  
    -- change connection_mode to loose  
    WAIT ON dw_load'ABOVE(dw_src), dw_src'ABOVE(dw_load)  
           UNTIL (connection_mode = coupled_low AND dw_load'ABOVE(dw_src)) OR  
                (connection_mode = coupled_high AND dw_src'ABOVE(dw_load));  
    BREAK; -- notice discontinuity  
END PROCESS connection_ctrl;
```



Plant Model: Revolving Load

VHDL-AMS Source Code No. 6

```
- initial setting of position and velocity of electrical motor and load
BREAK
  p_src => 0.0,
  w_src => 0.0,
  p_load => 0.0,
  w_load => 0.0;

-- state equations
p_src'DOT == w_src;           -- p_src := integral of w
p_load'DOT == w_load;        -- p_load := integral of w

IF connection_mode = loose USE -- if loose
  w_src'DOT == dw_src;       -- w_src := integral of dw_src
  w_load'DOT == dw_load;     -- w_load := integral of dw_load
ELSE                           -- if connected
  w_src'DOT == dw_connected; -- w_src := integral of dw_connected
  w_load'DOT == dw_connected; -- w_load := integral of dw_connected
END USE;
```



Plant Model: Revolving Load

VHDL-AMS Source Code No. 7


```
-- internal quantities
dw_src ==      m_src / j_load;      -- dw_src (as if not connected)
-- dw_load (as if not connected, with friction)
dw_load ==      calc_internal_momentum(motion_mode, m_load,
      w_load'ABOVE(0.0), m_slip) / j_load;
-- dw_connected (as if connected, with friction)
dw_connected == calc_internal_momentum(motion_mode, m_load + m_src,
      w_src'ABOVE(0.0), m_slip) / (j_src + j_load);

-- m_load_ext is used for determining motion_mode (motion_ctrl)
IF connection_mode = loose USE
  m_load_ext == m_load;
ELSE
  m_load_ext == m_load + m_src;
END USE;

END ARCHITECTURE behavioral;
```




Outline

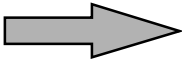- ◆ VHDL-AMS Modeling Guidelines
- ◆ VHDL-AMS Modeling Techniques
 - IC Applications
- ◆ Modeling at Different Levels of Abstraction
 - Telecom Applications
- ◆ Modeling of Multi-Disciplinary Systems
 - Automotive Applications
-  ◆ MEMS Modeling Using the VHDL-AMS Language



MEMS Accelerometers

- ◆ **Open-Loop Accelerometers**
 - Acceleration is sensed by measuring displacement of a seismic (proof/shuttle) mass
 - Advantages: low cost and small size
 - Disadvantages: nonlinearity/hysteresis effects and fatigue

- ◆ **Closed-Loop Accelerometers**
 - Acceleration is sensed by measuring force required to maintain position of seismic (proof/shuttle) mass
 - Advantages: reduced transverse sensitivity
 - Disadvantages: more circuitry and higher costs




Accelerometer Performance Characteristics

- ◆ Dynamic range of acceleration
 - Displacement limits
- ◆ Frequency response
 - Mechanical and electrical time constants
- ◆ Linearity
 - Parasitics
- ◆ Transverse (out-of-plane) sensitivity
 - Seismic mass suspension
- ◆ Temperature sensitivity
- ◆ Noise floor



Accelerometer Applications

 


◆ B. Boser, UC Berkeley



MEMS Accelerometers

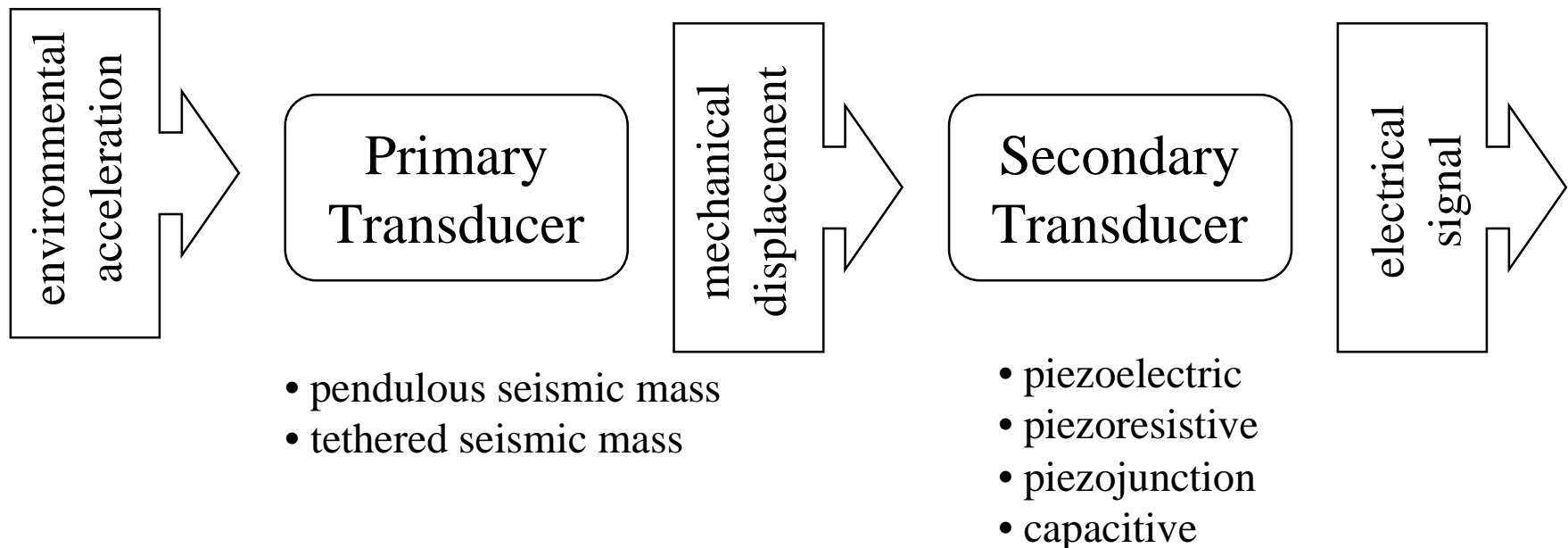
- ◆ Sensing is typically performed in two steps
 - Transform acceleration to mechanical displacement
 - Transform mechanical displacement to electrical signal






MEMS Accelerometers

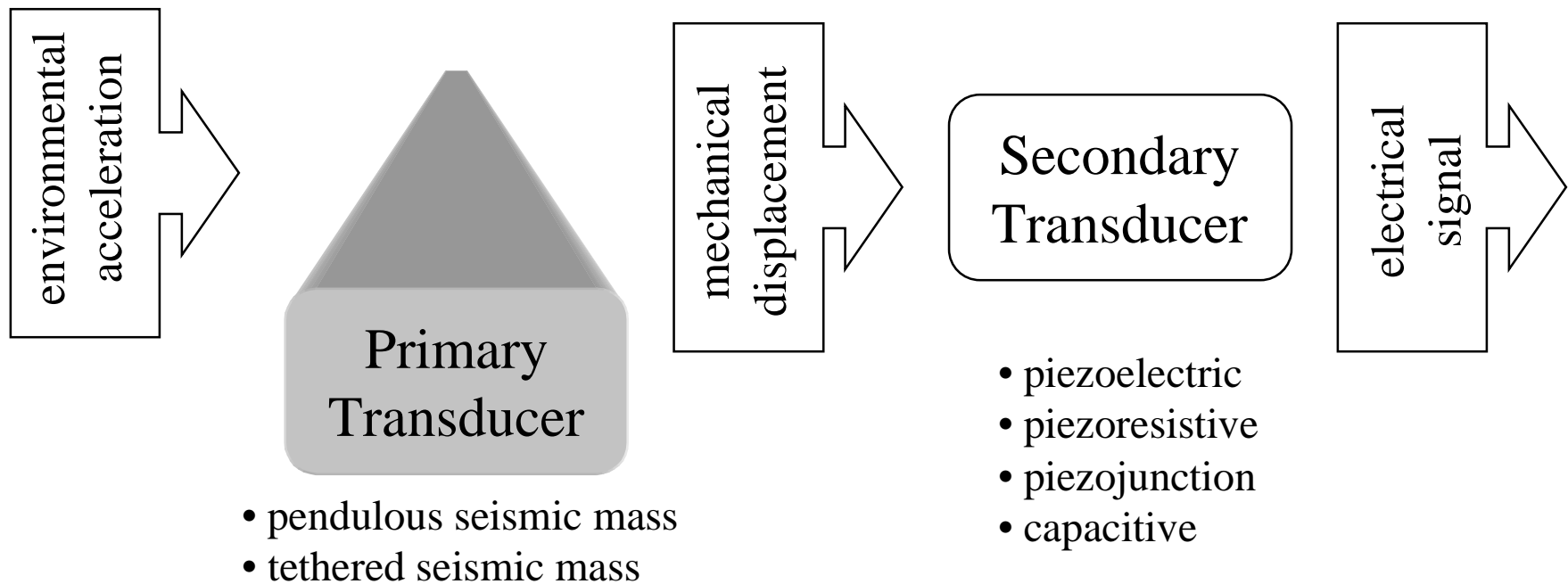- ◆ Sensing is typically performed in two steps
 - Transform acceleration to mechanical displacement
 - Transform mechanical displacement to electrical signal







Microflexural Structures

 


single cantilever

 

hammock flexure

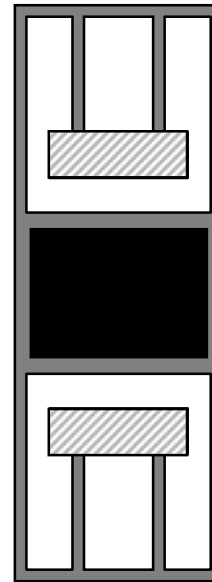


folded flexure

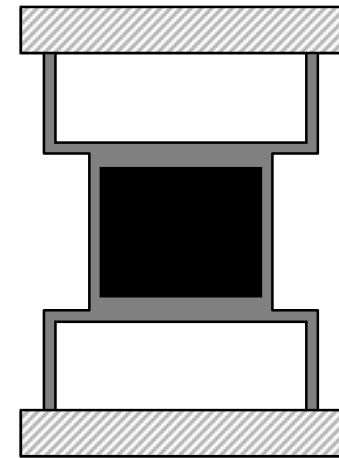

crab-leg flexure

damped harmonic oscillator

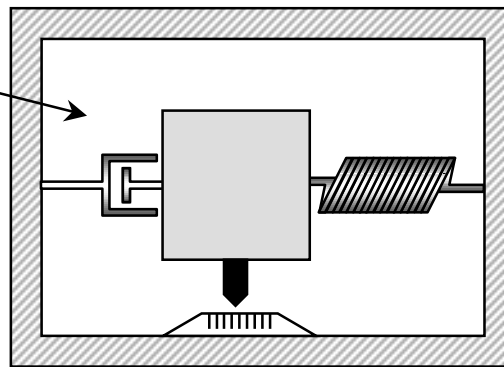


2nd order differential equation



Damped Harmonic Oscillator

$$F_{applied} = F_{mass} + F_{damping} + F_{spring}$$
 
$$F(t) = M \frac{d^2x}{dt^2} + D \frac{dx}{dt} + Kx$$



Model frictional resistance as damping force proportional to rate of movement (velocity)


Model inertia as force proportional to rate of velocity (acceleration)

Model structural elasticity as spring force proportional to movement



2nd Order Differential Equation

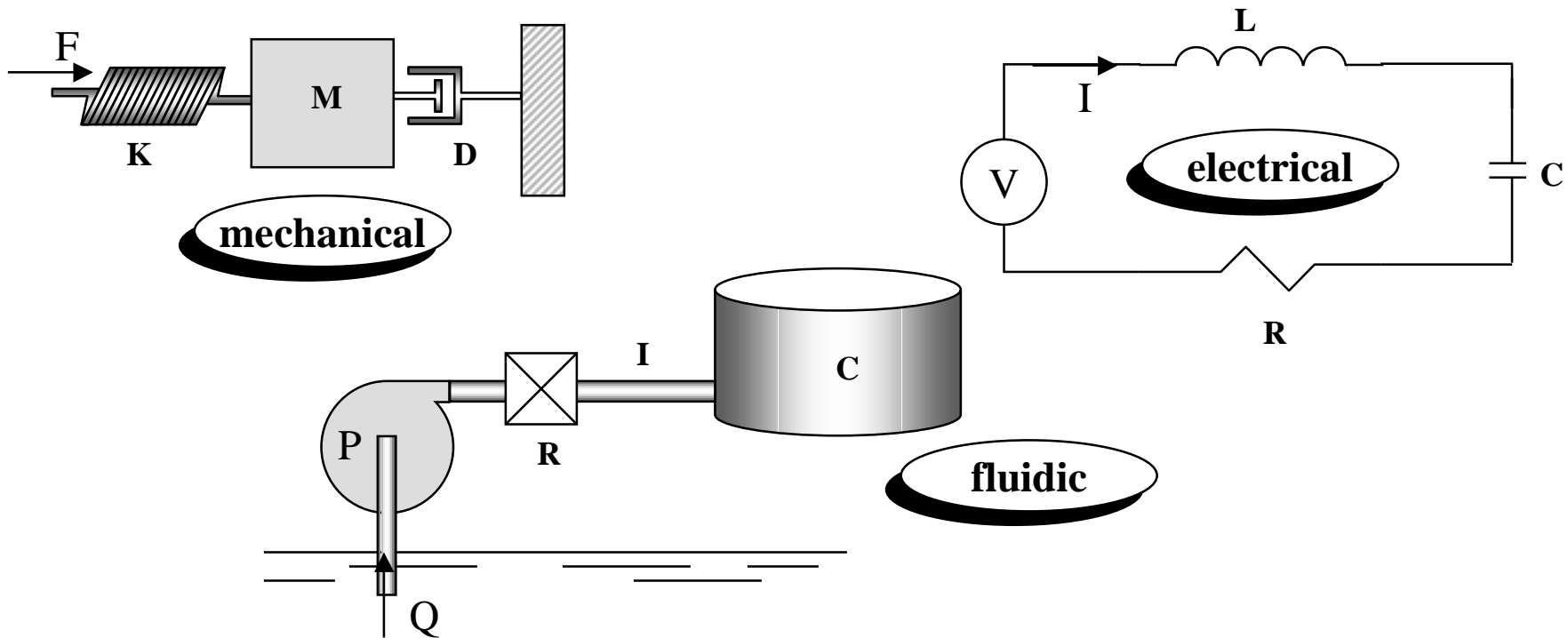- ◆ 2nd order ordinary differential equations (ODEs) naturally arise as mathematical models of physical systems - one per each degree of freedom.





Canonical Response

- ◆ Inertia, dissipative, elasticity characteristics determine transient (time domain) and bandwidth (frequency domain) response.

$$\frac{F(t)}{M} = G(t) = \frac{d^2x}{dt^2} + 2\xi\omega_0 \frac{dx}{dt} + \omega_0^2 x$$

$$\omega_0 = \sqrt{\frac{K}{M}}$$

- natural resonant frequency - oscillation with no damping/forcing

$$\xi = \frac{D}{2\sqrt{KM}}$$

- damping factor - actual damping/critical damping

$$\omega = \omega_0 \sqrt{1 - \xi^2}$$

- damped resonant frequency


$$\frac{x}{a} = \frac{1}{\omega_0^2}$$

- primary transducer transfer function - displacement/unit acceleration



MEMS Accelerometers

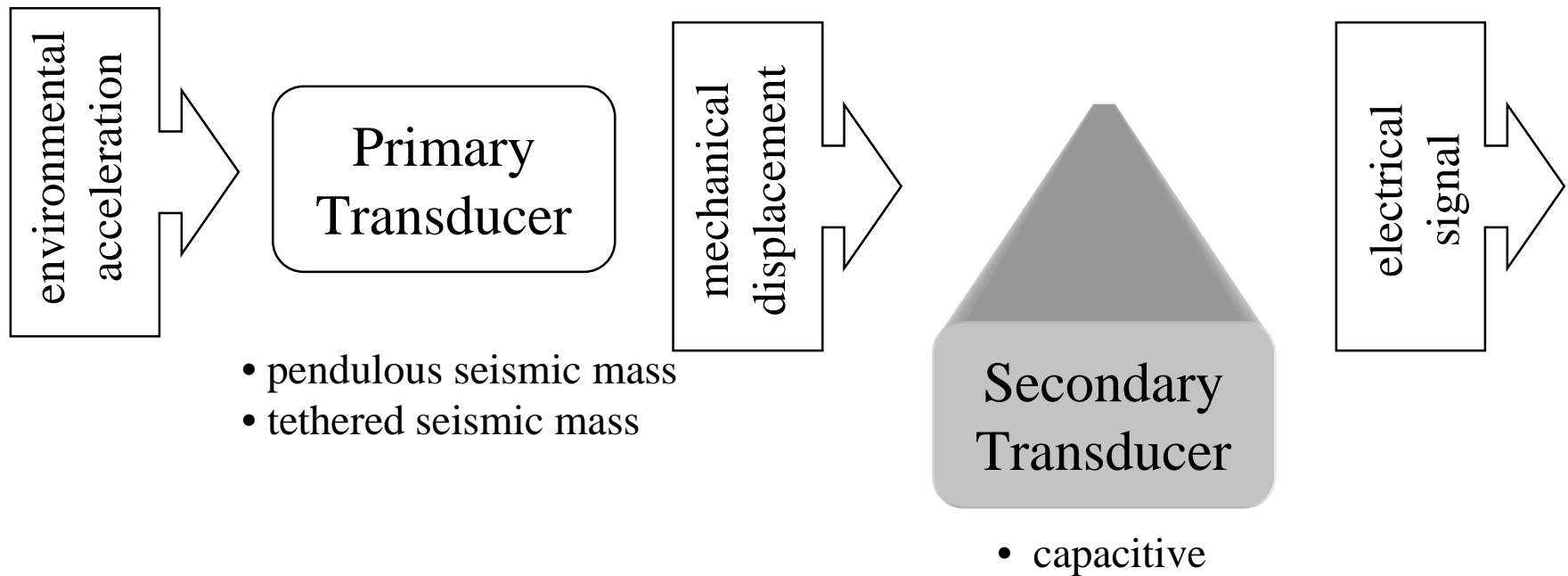- ◆ Sensing is typically performed in two steps
 - Transform acceleration to mechanical displacement
 - Transform mechanical displacement to electrical signal





Capacitive Sensing

- ◆ Seismic mass forms one plate of a parallel plate capacitance. Movement of mass changes area/gap between parallel plates and, consequently the capacitance.


- ◆ Advantages
 - low temperature sensitivity
 - noncontacting transduction
 - insensitivity to magnetic fields
 - operational reliability

- ◆ Disadvantages
 - parasitics
 - undesired electrostatic forces




Capacitive Sensing Configurations


◆ Parallel plate

 

◆ Transverse comb


 


◆ Lateral comb

 


Differential Capacitance Sensing

  - ◆ Easier to detect relative (differential) change rather than absolute change
- ◆ Differential configuration preferred over single-ended for linearity.







$$C_1 - C_{REF} \approx \frac{\epsilon A}{\delta} \left\{ \frac{\Delta x}{\delta} + \left(\frac{\Delta x}{\delta} \right)^2 \right\}$$
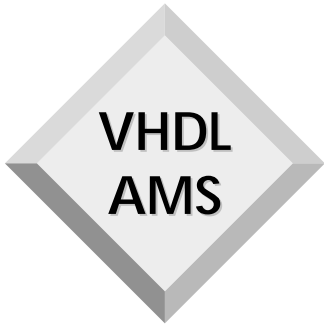
$$C_1 - C_2 \approx 2 \frac{\epsilon A}{\delta} \left\{ \frac{\Delta x}{\delta} - \left(\frac{\Delta x}{\delta} \right)^3 \right\}$$




Transverse Linear Comb Drive

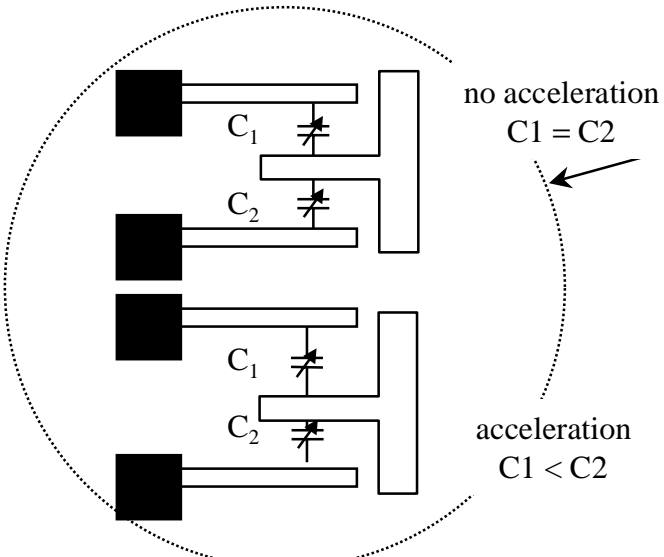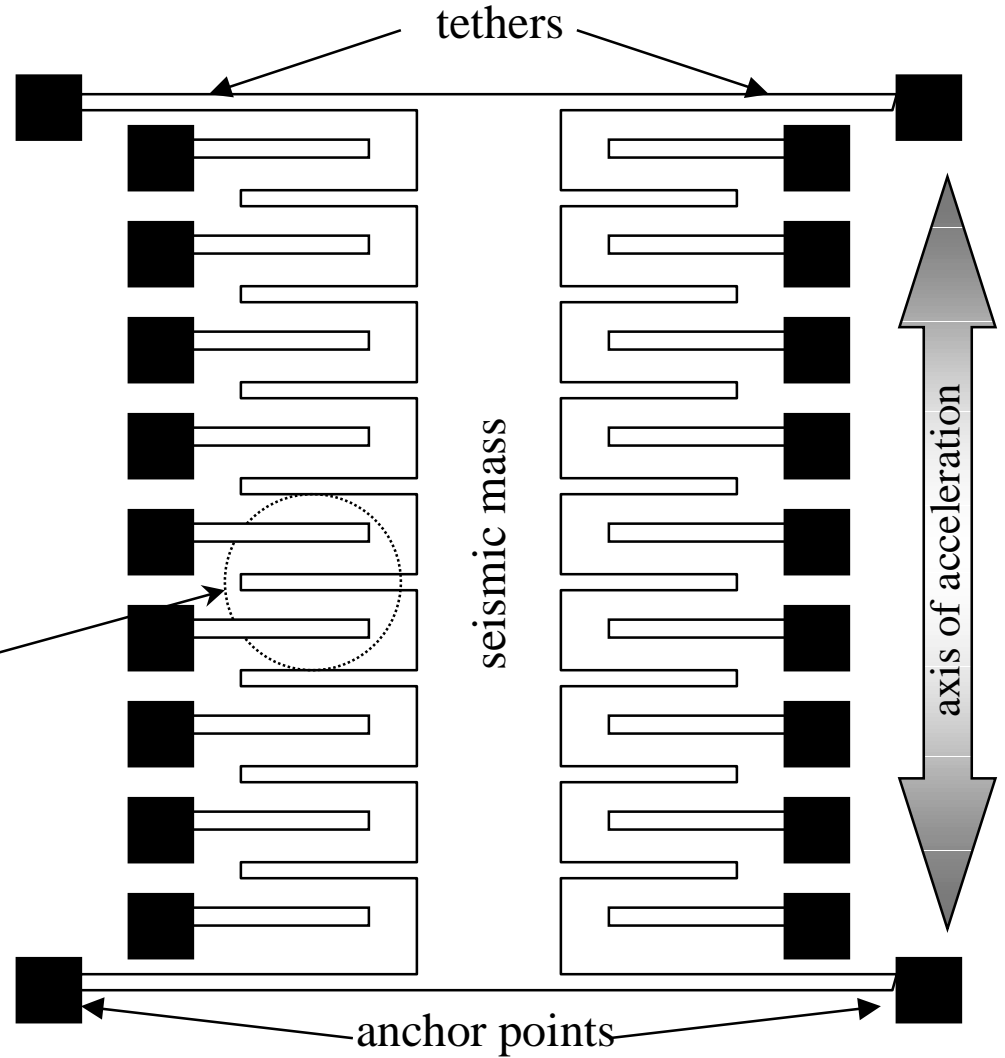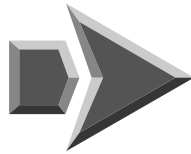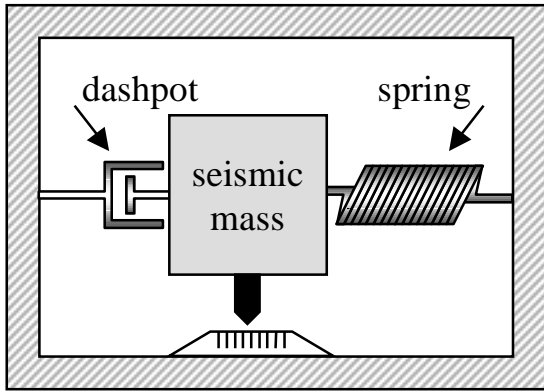



Capacitance Bridge (Analog Sampling)

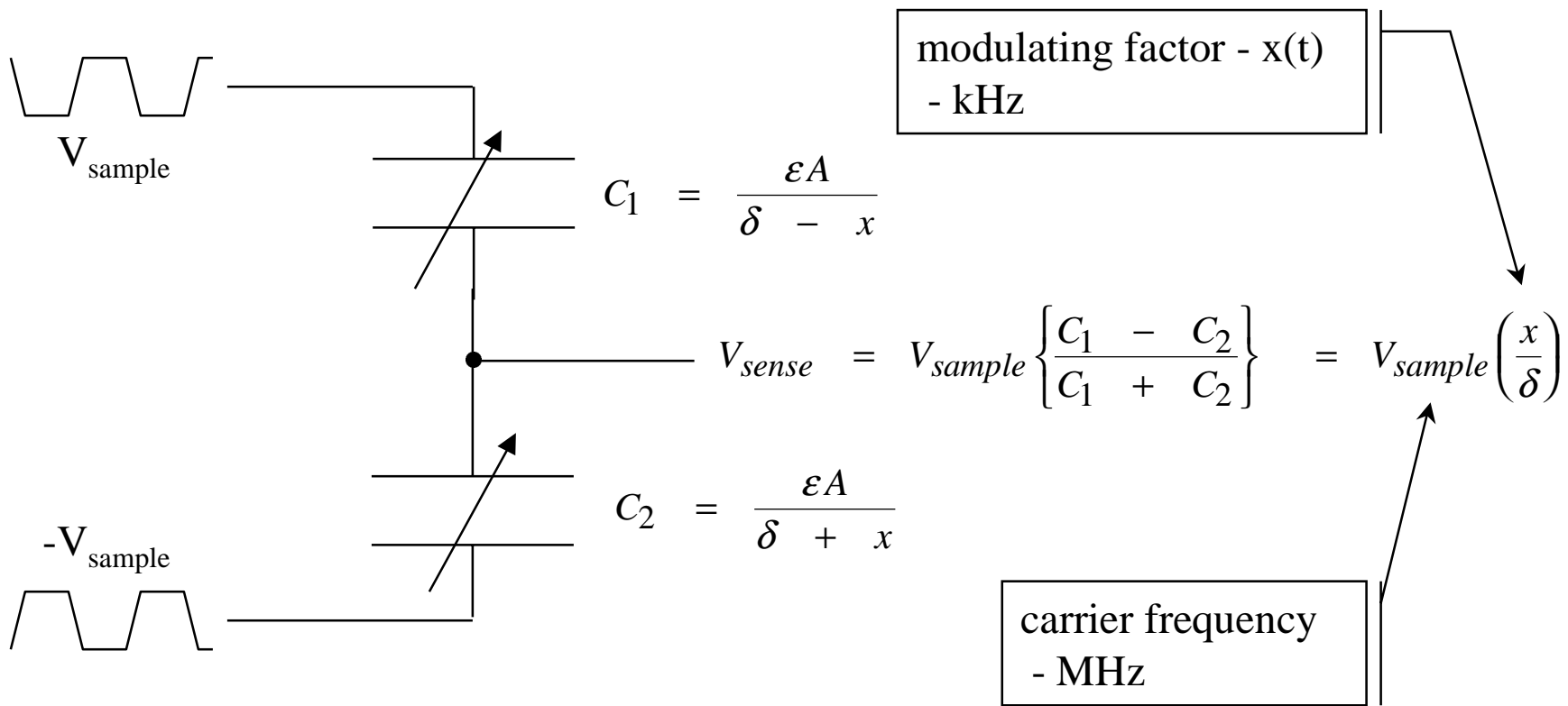
- ◆ Comb finger capacitances connected in parallel to add to form C_1 and C_2





MEMS Accelerometers

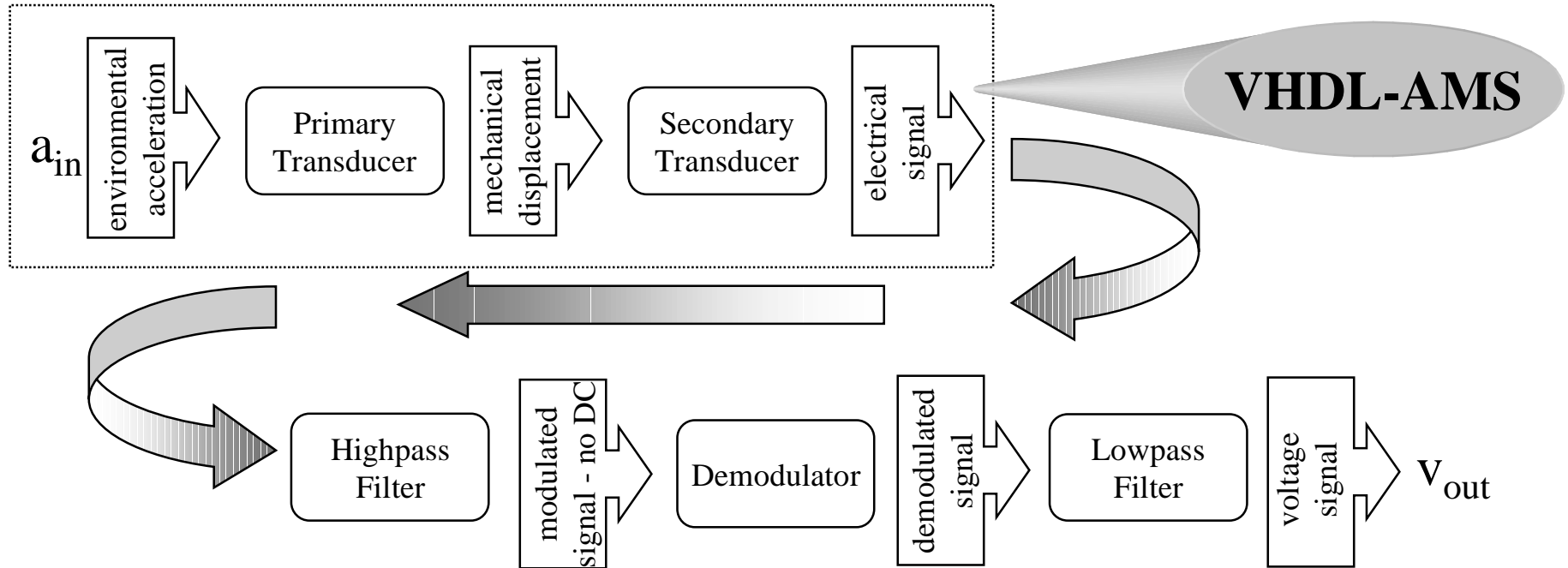
- ◆ Remaining processing conditions electrical signal
 - Extracts modulated acceleration information



$$\frac{V_{out}}{a_{in}} \propto \frac{V_{sample}}{\omega_0^2 \delta}$$



VHDL-AMS Model - Organization

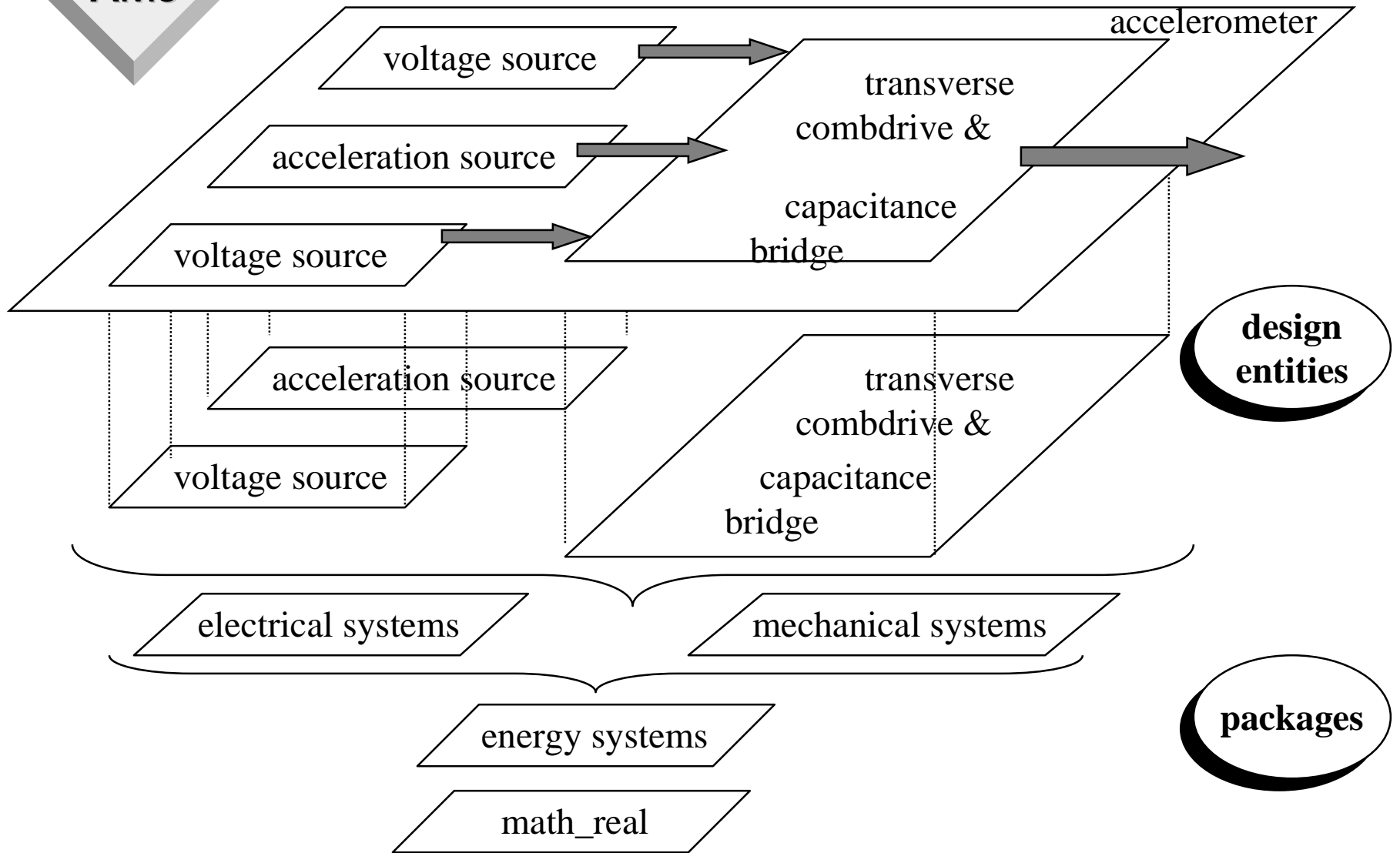



Design Entity: Acceleration Source

- ◆ Alternative forcing functions for ambient acceleration

```
library IEEE;  
use IEEE.MATH_REAL.all;  
use IEEE.MECHANICAL_SYSTEMS.all;  
entity ENV_FORCE is  
    generic (constant MAG_AC, MAG_DC : FORCE := 0.0;  
            constant FREQ : REAL := 0.0);  
    port (terminal PT1, PT2 : TRANSLATIONAL);  
end entity ENV_FORCE;
```

```
architecture DC of ENV_FORCE is  
    quantity FORCE through PT1 to PT2;  
begin  
    FORCE == MAG_DC;  
end architecture DC;
```

```
architecture SINE of ENV_FORCE is  
    quantity FORCE through PT1 to PT2;  
begin  
    FORCE == MAG_AC*sin(MATH_2_PI*FREQ*NOW);  
end architecture SINE;
```



Design Entity: Voltage Source

◆ Carrier frequency for analog sampling

```
library IEEE;
use IEEE.MATH_REAL.all;
use IEEE.ELECTRICAL_SYSTEMS.all;
entity VSOURCE is
    generic (constant MAG_AC, MAG_DC : VOLTAGE := 0.0;
             constant FREQ : REAL := 0.0);
    port (terminal P, M : ELECTRICAL);
end entity VSOURCE;

architecture SINE of VSOURCE is
    quantity V across I through P to M;
begin
    V == MAG_AC*sin(MATH_2_PI*FREQ*NOW) + MAG_DC;
end architecture SINE;
```



Design Entity: Transducer

- ◆ Design entity declaration couples energy domains
 - Electrical domain
 - Mechanical domain

```
library IEEE;  
use IEEE.ENERGY_SYSTEMS.all  
use IEEE.ELECTRICAL_SYSTEMS.all;  
use IEEE.MECHANICAL_SYSTEMS.all;  
entity COMB_DRIVE is  
  generic (M : MASS      := 0.16*NANO;  
           D : DAMPING   := 4.0e-6;  
           K : STIFFNESS := 2.6455;  
           A : REAL      := 2.0e-6*110.0e-6 ;  
           D0 : REAL     := 1.5e-6);  
  
  port (terminal PROOF_MASS, REF : TRANSLATIONAL;  
        terminal TOP_EL, MID_EL, BOT_EL : ELECTRICAL);  
end entity COMB_DRIVE;
```

mechanical
properties

geometric
properties



Design Entity: Transducer (Continued)

```
architecture BCR of COMB_DRIVE is
  -- free quantities
  quantity VEL      : VELOCITY;
  quantity QTM,QBM : CHARGE;

  quantity DTM,DBM : DISPLACEMENT;
  quantity CTM,CBM : CAPCITANCE;

  -- branch quantities
  quantity POS across FORCE through PROOF_MASS to REF;
  quantity VTM across ITM   through TOP_EL   to MID_EL;
  quantity VBM across IBM   through BOT_EL   to MID_EL;
begin
  -- compute displacement of comb drive
  VEL == POS'DOT;
  FORCE == K*POS + D*VEL + M*VEL'DOT;

  DTM == D0 + POS; DBM == D0 - POS;

  -- compute change in capacitance
  CTM == A*EPS0/DTM; CBM == A*EPS0/DBM;

  -- compute generated current
  QTM == CTM*VTM; QBM == CBM*VBM;
  ITM == QTM'DOT; IBM == QBM'DOT;
end architecture BCR;
```

mechanical dynamics

electrical dynamics



Design Entity: MEMS Accelerometer

```
library IEEE;  
use IEEE.ELECTRICAL_SYSTEMS.all;  
use IEEE.MECHANICAL_SYSTEMS.all;  
entity ACCELEROMETER is  
end entity ACCELEROMETER;
```

```
architecture TOP_LEVEL of ACCELEROMETER is
```

```
  terminal SMASS : TRANSLATIONAL;
```

```
  terminal TOP, MID, BOT : ELECTRICAL;
```

```
begin
```

```
  F1:entity WORK.ENV_FORCE(SINE)
```

```
    generic map (MAG_AC=>0.16e-9*5.0*GRAV, FREQ=>100.0)
```

```
    port map (PT1=>SMASS, PT2=>ANCHOR);
```

```
  V1:entity WORK.VSOURCE
```

```
    generic map (MAG_AC=>300.0e-3, FREQ=>1.0*MEGA, MAG_DC=>0.0)
```

```
    port map (P=>TOP, M=>GROUND);
```

```
  V2:entity WORK.VSOURCE
```

```
    generic map (MAG_AC=>-300.0e-3, FREQ=>1.0*MEGA, MAG_DC=>0.0)
```

```
    port map (P=>BOT, M=>GROUND);
```





Design Entity: MEMS Accelerometer (Continued)



```
A1:entity WORK.COMB_DRIVE
  generic map (M => 0.16e-9,
               K => 2.6455,
               D => 4.0e-6,
               A => 2.0e-6*110.0e-6,
               D0 => 1.5e-6)


  port map (   PROOF_MASS => SMASS,
               REF => ANCHOR,
               TOP_EL => TOP,
               MID_EL => MID,
               BOT_EL => BOT);

R1:entity WORK.RESISTOR
  generic map (RNOM => 3.0*MEGA)
  port map (P=>MID, M=>GROUND);


end architecture TOP_LEVEL;
```





Sample Simulation Results

 

Input Force

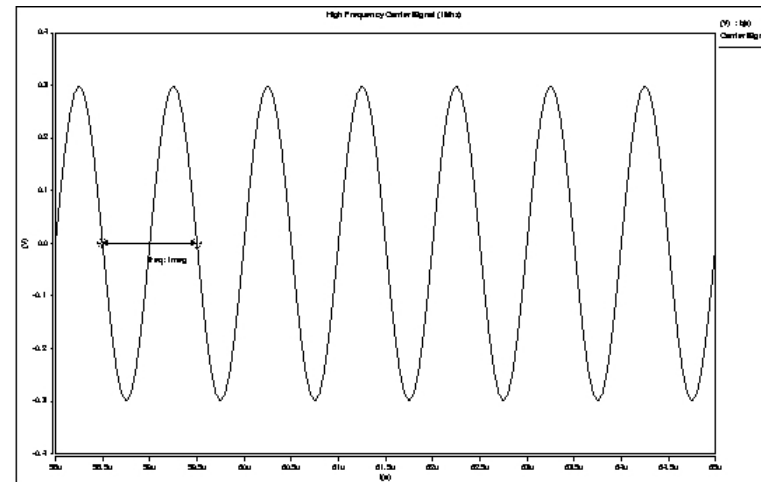 


Analog Voltage
Carrier Frequency




Sample Simulation Results


Seismic Mass Position

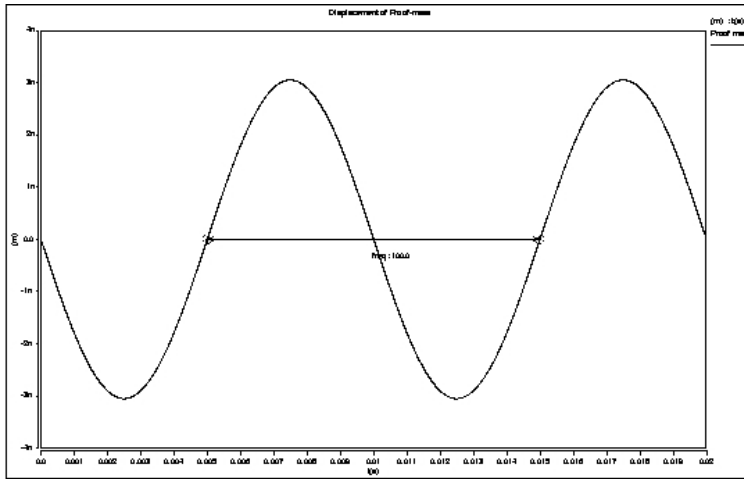

Modulated Signal

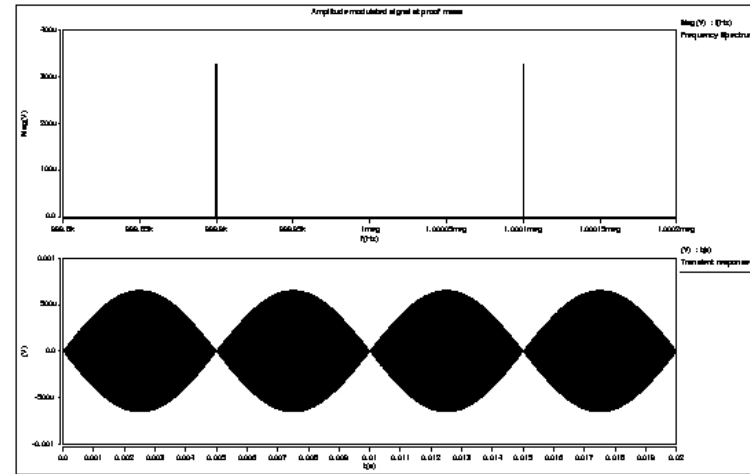

Demodulated and Lowpass Filtered Signal

 




Improved MEMS Accelerometer Model

- ◆ Model shows only first-order physics
 - Not adequate for practical design


- ◆ Model assumes constant values for mechanical elasticity and damping
 - Parametric values per microflexural structure
 - Interaction of electrostatic forces

 - ◆ Model assumes basic capacitance models
 - Parasitics
 - Nonparallel plates




Parasitic Capacitances

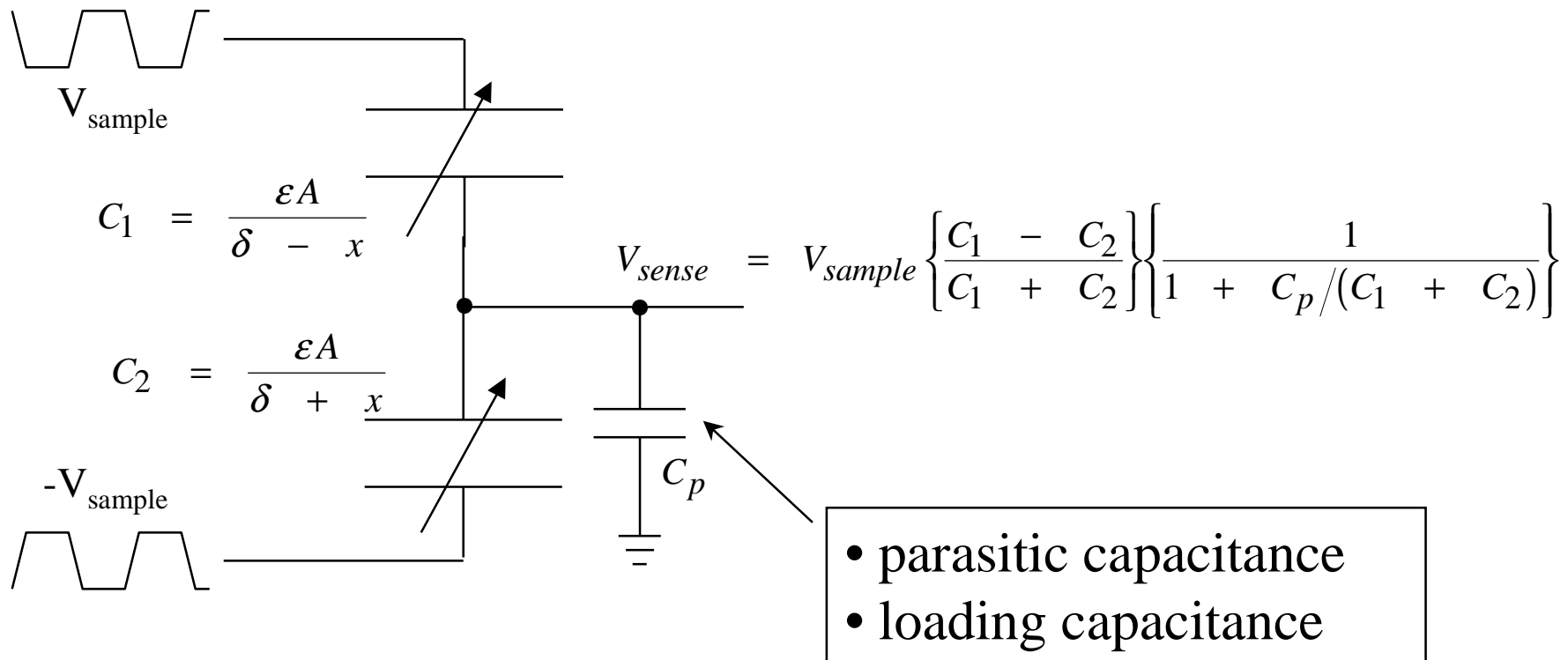- ◆ Stray and fringe field capacitances influence transduction properties
 - Introduces nonlinearity in modulation
 - Attenuates gain



Electrostatics


- ◆ Potential energy - $E = \int_Q V dQ = \int_Q \frac{Q}{C} dQ = \frac{1}{2} \frac{Q^2}{C} = \frac{1}{2} CV^2$
- ◆ Electrostatic force - $F = \frac{\partial E}{\partial x} = \frac{\partial}{\partial x} \left(\frac{1}{2} CV^2 \right) = \frac{1}{2} V^2 \frac{\partial C}{\partial x}$
- ◆ Electrostatic spring coefficient - $k_e = \frac{\partial F}{\partial x} = \frac{1}{2} V^2 \frac{\partial^2 C}{\partial x^2}$

 

$$C(x) = \frac{\epsilon A}{(\delta + x)} = C_0 \left(1 + \frac{x}{\delta} \right)^{-1}$$

$$F(x) = \frac{1}{2} V^2 \frac{C_0}{\delta} \left(1 + \frac{x}{\delta} \right)^{-2}$$
 
$$k_e(x) = \frac{\partial F}{\partial x} = V^2 \frac{C_0}{\delta^2} \left(1 + \frac{x}{\delta} \right)^{-3}$$



$$C(x) = 2 \frac{\epsilon h}{\delta} (L + x) = C_0 \left(1 + \frac{x}{L} \right)$$

$$F = \frac{1}{2} V^2 \frac{C_0}{L} = V^2 \frac{\epsilon h}{\delta}$$

$$k_e = \frac{\partial F}{\partial x} = 0$$



Electrostatic/Mechanical Elasticity

- ◆ Electrostatic force opposes structural restoring force
- ◆ Addition of electrostatic force “softens” the transducer
- ◆ Elasticity is combination of mechanical and electrical spring constants
 - Frequency-pulling


$$K_{electrical} = \frac{\partial}{\partial x}(F_1 - F_2)$$

$$K = K_{electrical} + K_{mechanical}$$

$$\omega_0 = \sqrt{\frac{K_{electrical} + K_{mechanical}}{M}}$$

VHDL
AMS

Construct Modeling Levels

 

- Noise
- Temperature
- High-order modal modeling

- Nonparallel plate capacitances
- Squeeze film damping
- Residual material stresses

- Electrostatic spring constants
- Parametric mechanical elasticity
- Parasitic capacitances

- Basic lumped-element model
- 2nd-order harmonic mechanical oscillator
- Constant coefficients