



Digital Design

Chapter 9: Hardware Description Languages

Slides to accompany the textbook *Digital Design*, First Edition,
by Frank Vahid, John Wiley and Sons Publishers, 2007.
<http://www.ddvahid.com>



Copyright © 2007 Frank Vahid

Instructors of courses requiring Vahid's *Digital Design* textbook (published by John Wiley and Sons) have permission to modify and use these slides for customary course-related activities, subject to keeping this copyright notice in place and unmodified. These slides may be posted as unanimated pdf versions on publicly-accessible course websites. PowerPoint source (or pdf with animations) may not be posted to publicly-accessible websites, but may be posted for students on internal protected sites or distributed directly to students by other electronic means. Instructors may make printouts of the slides available to students for a reasonable photocopying charge, without incurring royalties. Any other use requires explicit permission. Instructors may obtain PowerPoint source or obtain special use permissions from Wiley – see <http://www.ddvahid.com> for information.

  9.1

Introduction

- A drawing of a circuit, or *schematic*, contains graphical information about a design
 - Inverter is above the OR gate, AND gate is to the right, etc.
- Such graphical information may not be useful for large designs
- Can use textual language instead




Digital Design
Copyright © 2006
Frank Vahid

2

Note: Slides with animation are denoted with a small red "a" near the animated items

Textual Language – English

 - Can describe circuit using English text rather than using a drawing
 - Of course, English isn't a good language for a computer to read
 - Need a more precise, computer-oriented language



(b) We'll now describe a circuit whose name is DoorOpener. The external inputs are c, h and p, which are bits. The external output is f, which is a bit.

We assume you know the behavior of these components:
An inverter, which has a bit input x, and bit output F.
A 2-input OR gate, which has inputs x and y, and bit output F.
A 2-input AND gate, which has bit inputs x and y, and bit output F.

The circuit has internal wires n1 and n2, both bits.
The DoorOpener circuit internally consists of:
An inverter named Inv_1, whose input x connects to external input c, and whose output connects to n1.
A 2-input OR gate named OR2_1, whose inputs connect to external inputs h and p, and whose output connects to n2.
A 2-input AND gate named AND2_1, whose inputs connect to n1 and n2, and whose output connects to external output f.
That's all.



Digital Design
Copyright © 2006
Frank Vahid

3

Computer-Readable Textual Language for Describing Hardware Circuits: HDLs

- Hardware description language (HDL)
 - Intended to describe circuits textually, for a computer to read
 - Evolved starting in the 1970s and 1980s
- Popular languages today include:
 - VHDL – Defined in 1980s by U.S. military; Ada-like language
 - Verilog – Defined in 1980s by a company; C-like language
 - SystemC – Defined in 2000s by several companies; consists of libraries in C++



Digital Design
Copyright © 2006
Frank Vahid


4

Combinational Logic Description using Hardware Description Languages ^{9.2}

Description Languages

- **Structure**

 - Another word for "circuit"
- An interconnection of components
- Key use of HDLs is to describe structure




Note: The term "instantiate" will be used to indicate adding a new copy of a component to a circuit

The OR component



Three instances of the OR component

 


Digital Design
Copyright © 2006
Frank Vahid

5

Describing Structure in VHDL

 - Entity – Defines new item's name & ports (inputs/outputs)
 - std_logic means bit type, defined in ieee library
- Architecture – Describes internals, which we named "Circuit"
 - Declares 3 previously-defined components
 - Declares internal signals
 - Note "--" comment
 - Instantiates and connects those components



We'll now describe a circuit whose name is DoorOpener. The external inputs are c, h and p, which are bits. The external output is f, which is a bit.

We assume you know the behavior of these components:
 An inverter, which has a bit input x, and bit output F.
 A 2-input OR gate, which has inputs x and y, and bit output F.
 A 2-input AND gate, which has bit inputs x and y, and bit output F.

The circuit has internal wires n1 and n2, both bits.

The DoorOpener circuit internally consists of:
 An inverter named Inv_1, whose input x connects to external input c, and whose output connects to n1.
 A 2-input OR gate named OR2_1, whose inputs connect to external inputs h and p, and whose output connects to n2.
 A 2-input AND gate named AND2_1, whose inputs connect to n1 and n2, and whose output connects to external output f.
 That's all.

```

library ieee;
use ieee.std_logic_1164.all;
entity DoorOpener is
    port ( c, h, p: in std_logic;
          f: out std_logic
        );
end DoorOpener;

architecture Circuit of DoorOpener is
    component Inv
        port ( x: in std_logic;
              F: out std_logic );
    end component;
    component OR2
        port ( x,y: in std_logic;
              F: out std_logic );
    end component;
    component AND2
        port ( x,y: in std_logic;
              F: out std_logic );
    end component;
    signal n1,n2: std_logic; --internal wires
begin
    Inv_1: Inv port map (x=>c, F=>n1);
    OR2_1: OR2 port map (x=>h,y=>p,F=>n2);
    AND2_1: AND2 port map (x=>n1,y=>n2,F=>f);
end Circuit;
    
```

(b)

(c)


6



Digital Design
Copyright © 2006
Frank Vahid

Describing Structure in Verilog

 - Modules defined for Inv, OR2, and AND2 (details omitted)
 - Note "//" comment
- Module defined for DoorOpener
 - Lists inputs and outputs
 - Declares internal wires
 - Instantiates and connects three components



(a)

We'll now describe a circuit whose name is DoorOpener. The external inputs are c, h and p, which are bits. The external output is f, which is a bit.

We assume you know the behavior of these components:
 An inverter, which has a bit input x, and bit output F.
 A 2-input OR gate, which has inputs x and y, and bit output F.
 A 2-input AND gate, which has bit inputs x and y, and bit output F.

The circuit has internal wires n1 and n2, both bits.

The DoorOpener circuit internally consists of:
 An inverter named Inv_1, whose input x connects to external input c, and whose output connects to n1.
 A 2-input OR gate named OR2_1, whose inputs connect to external inputs h and p, and whose output connects to n2.
 A 2-input AND gate named AND2_1, whose inputs connect to n1 and n2, and whose output connects to external output f.
 That's all.

```

module Inv(x, F);
    input x;
    output F;
    // details not shown
endmodule

module OR2(x, y, F);
    input x, y;
    output F;
    // details not shown
endmodule

module AND2(x, y, F);
    input x, y;
    output F;
    // details not shown
endmodule


module DoorOpener(c, h, p, f);
    input c, h, p;
    output f;
    wire n1, n2;
    Inv Inv_1(c, n1);
    OR2 OR2_1(h, p, n2);
    AND2 AND2_1(n1, n2, f);
endmodule
    
```



Digital Design
 Copyright © 2006
 Frank Vahid

Describing Structure in SystemC

 - Module defined
 - Declares inputs and outputs
 - Declares internal wires
 - Note "//" comment
 - Declares three previously-defined components
 - Constructor function "CTOR"
 - Instantiates components
 - Connects components



(a)

We'll now describe a circuit whose name is DoorOpener. The external inputs are c, h and p, which are bits. The external output is f, which is a bit.

We assume you know the behavior of these components:
 An inverter, which has a bit input x, and bit output F.
 A 2-input OR gate, which has inputs x and y, and bit output F.
 A 2-input AND gate, which has bit inputs x and y, and bit output F.

The circuit has internal wires n1 and n2, both bits.

The DoorOpener circuit internally consists of:
 An inverter named Inv_1, whose input x connects to external input c, and whose output connects to n1.
 A 2-input OR gate named OR2_1, whose inputs connect to external inputs h and p, and whose output connects to n2.
 A 2-input AND gate named AND2_1, whose inputs connect to n1 and n2, and whose output connects to external output f.
 That's all.

```

#include "systemc.h"
#include "inv.h"
#include "or2.h"
#include "and2.h"

SC_MODULE (DoorOpener)
{
    sc_in<sc_logic> c, h, p;
    sc_out<sc_logic> f;
    // internal wires
    sc_signal<sc_logic> n1, n2;
    // component declarations
    Inv Inv1;
    OR2 OR2_1;
    AND AND2_1;
    // component instantiations
    SC_CTOR (DoorOpener) : Inv_1 ("Inv_1"),
        OR2_1 ("OR2_1"), AND2_1 ("AND2_1")
    {
        Inv_1.x(c);
        Inv_1.F(n1);
        OR2_1.x(h);
        OR2_1.y(p);
        OR2_1.F(n2);
        AND2_1.x(n1);
        AND2_1.y(n2);
        AND2_1.F(f);
    }
};
    
```



Digital Design
 Copyright © 2006
 Frank Vahid

Combinational Behavior

- **Combinational behavior**
 - Description of desired behavior of combinational circuit without creating circuit itself
 - e.g., $F = c' * (h + p)$ can be described as equation rather than circuit
 - HDLs support description of combinational behavior



Describing Combinational Behavior in VHDL

- Describing an OR gate's behavior
 - Entity defines input/output ports
 - Architecture
 - Process – Describes behavior
 - Process "sensitive" to x and y
 - » Means behavior only executes when x changes or y changes
 - Behavior assigns a new value to output port F, computed using built-in operator "or"

```
library ieee;
use ieee.std_logic_1164.all;

entity OR2 is
  port (x, y: in std_logic;
        F: out std_logic
        );
end OR2;

architecture behavior of OR2 is
begin
  process (x, y)
  begin
    F <= x or y;
  end process;
end behavior;
```



Describing Combinational Behavior in VHDL

- Describing a custom function's behavior
 - Desired function: $f = c \cdot (h + p)$
 - Entity defines input/output ports (not shown)
 - Architecture
 - Process
 - Sensitive to c, h, and p
 - Assigns a new value to output port f, computed using built-in operators "not", "and", and "or"

```
architecture beh of DoorOpener is
begin
  process(c, h, p)
  begin
    f <= not(c) and (h or p);
  end process;
end beh;
```



Describing Combinational Behavior in Verilog

- Describing an OR gate's behavior
 - Module declares input/output ports
 - Also indicates that F is "reg"
 - Means F stores value
 - By default, ports are wires, having no storage
 - "always" procedure executes statement block when change occurs on x or on y
 - "Sensitive" to x and y
 - Assigns value to F, computed using built-in OR operator "|"

```
module OR2(x, y, F);
input x, y;
output F;
reg F;

always @(x or y)
begin
  F <= x | y;
end
endmodule
```



Describing Combinational Behavior in Verilog

- Describing a custom function's behavior
 - Desired function: $f = c \cdot (h + p)$
 - Module defines input/output ports
 - Output f defined as "reg"
 - "always" procedure sensitive to inputs
 - Assigns value to f, computed using built-in operators for NOT (~), AND (&), and OR (|)

```
module DoorOpener(c,h,p,f);
  input c, h, p;
  output f;
  reg f;

  always @(c or h or p)
  begin
    f <= (~c) & (h | p);
  end
endmodule
```



Describing Combinational Behavior in SystemC

- Describing an OR gate's behavior
 - Module declares input/output ports
 - Constructor (CTOR)
 - Indicates module described by a method (procedure) "comblogic"
 - Sensitive to x and y
 - Method "comblogic" assigns F a new value using built-in OR operator "|"
 - Reading input port done using .read() function defined for input port type; likewise, writing done using .write() function

```
#include "systemc.h"
SC_MODULE(OR2)
{
  sc_in<sc_logic> x, y;
  sc_out<sc_logic> F;

  SC_CTOR(OR2)
  {
    SC_METHOD(comblogic);
    sensitive << x << y;
  }

  void comblogic()
  {
    F.write(x.read() | y.read());
  }
};
```



Describing Combinational Behavior in SystemC

- Describing a custom function's behavior
 - Desired function: $f = c \cdot (h+p)$
 - Module defines input/output ports
 - Constructor
 - Indicates module described by a method (procedure) "comblogic"
 - Sensitive to c, h, and p
 - "comblogic" method
 - Assigns value to f, computed using built-in operators for NOT (~), AND (&), and OR (|)

```
#include "systemc.h"
SC_MODULE(DoorOpener)
{
    sc_in<sc_logic> c, h, p;
    sc_out<sc_logic> f;


    SC_CTOR(DoorOpener)
    {
        SC_METHOD(comblogic);
        sensitive << c << h << p;
    }

    void comblogic()
    {
        f.write((~c.read()) & (h.read() |
            p.read()));
    }
};
```



Testbenches

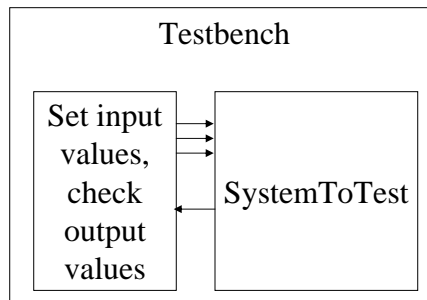- **Testbench**
 - Assigns values to a system's inputs, check that system outputs correct values
 - A key use of HDLs is to simulate system to ensure design is correct



Testbench in VHDL

- Entity
 - No inputs or outputs
- Architecture
 - Declares component to test, declares signals
 - Instantiates component, connects to signals
 - Process writes input signals, checks output signal
 - Waits a small amount of time after writing input signals
 - Checks for correct output value using "assert" statement

```

library ieee;
use ieee.std_logic_1164.all;


entity Testbench is
end Testbench;

architecture behavior of Testbench is
    component DoorOpener
        port ( c, h, p: in std_logic;
              f: out std_logic
            );
    end component;
    signal c, h, p, f: std_logic;
begin
    DoorOpener1: DoorOpener port map (c,h,p,f);

    process
    begin
        -- case 0
        c <= '0'; h <= '0'; p <= '0';
        wait for 1 ns;
        assert (f='0') report "Case 0 failed";

        -- case 1
        c <= '0'; h <= '0'; p <= '1';
        wait for 1 ns;
        assert (f='1') report "Case 1 failed";
        -- (cases 2-6 omitted from figure)
        -- case 7
        c <= '1'; h <= '1'; p <= '1';
        wait for 1 ns;
        assert (f='0') report "Case 7 failed";

         wait; -- process does not wake up again
    end process;
end behavior;
    
```



Digital Design
Copyright © 2006
Frank Vahid

17

Testbench in Verilog


- Module
 - Three register signals for inputs (values must be written and stored)
 - One wire signal for output (value is only read, need not be stored)
 - Instantiates component, connects to signals
 - "initial" procedure executed only once at beginning
 - Sets input values
 - Displays output value

```

module Testbench;
    reg c, h, p;
    wire f;

    DoorOpener DoorOpener1(c, h, p, f);

     initial
    begin
        // case 0
        c <= 0; h <= 0; p <= 0;
        #1 $display("f = %b", f);
        // case 1
        c <= 0; h <= 0; p <= 1;
        #1 $display("f = %b", f);
        // (cases 2-6 omitted from figure)
        // case 7
        c <= 1; h <= 1; p <= 1;
        #1 $display("f = %b", f);
    end
endmodule
    
```




Digital Design
Copyright © 2006
Frank Vahid

18

Testbench in SystemC

 - Module
 - Testbench is its own module
 - Three outputs, one for each input of system to test
 - One input, for the one output of the system to test
 - Constructor defined as THREAD
 - Like MODULE, but allows use of "wait" to control timing
 - testbench procedure writes outputs, waits for small amount of time, checks for correct output
 - assert function prints error if condition is not true



```

#include "systemc.h"
SC_MODULE(Testbench)
{
    sc_out<sc_logic> c_t, h_t, p_t;
    sc_in<sc_logic> f_t;

    SC_CTOR(Testbench)
    {
        SC_THREAD(testbench_proc);
    }

    void testbench_proc()
    {
        // case 0
        c_t.write(SC_LOGIC_0);
        h_t.write(SC_LOGIC_0);
        p_t.write(SC_LOGIC_0);
        wait(1, SC_NS);
        assert( f_t.read() == SC_LOGIC_0 );

        // case 1
        c_t.write(SC_LOGIC_0);
        h_t.write(SC_LOGIC_0);
        p_t.write(SC_LOGIC_1);
        wait(1, SC_NS);
        assert( f_t.read() == SC_LOGIC_1 );

        // (cases 2-6 omitted from figure)
        // case 7
        c_t.write(SC_LOGIC_1);
        h_t.write(SC_LOGIC_1);
        p_t.write(SC_LOGIC_1);
        wait(1, SC_NS);
        assert( f_t.read() == SC_LOGIC_0 );

        sc_stop();
    }
};
    
```



Digital Design
Copyright © 2006
Frank Vahid

19

Sequential Logic Description using Hardware Description Languages

9.3

- Will consider description of three sequential components
 - Registers
 - Oscillators
 - Controllers



Digital Design
Copyright © 2006
Frank Vahid

20

Describing a 4-bit Register in VHDL

- Entity
 - 4 data inputs, 4 data outputs, and a clock input
 - Use `std_logic_vector` for 4-bit data
 - I: `in std_logic_vector(3 downto 0)`
 - I <= "1000" would assign I(3)=1, I(2)=0, I(1)=0, I(0)=0
- Architecture
 - Process sensitive to clock input
 - First statement detects if change on clock was a rising edge
 - If clock change was rising edge, sets output Q to input I
 - Ports are signals, and signals store values – thus, output retains new value until set to another value

```
library ieee;
use ieee.std_logic_1164.all;

entity Reg4 is
  port ( I: in std_logic_vector(3 downto 0);
        Q: out std_logic_vector(3 downto 0);
        clk: in std_logic
        );
end Reg4;

architecture behavior of Reg4 is
begin
  process (clk)
  begin
    if (clk='1' and clk'event) then
      Q <= I;
    end if;
  end process;
end behavior;
```



Describing a 4-bit Register in Verilog

- Module
 - 4 data inputs, 4 data outputs, and a clock input
 - Define data inputs/outputs as vectors
 - input [3:0] I
 - I <= 4'b1000 assigns I[3]=1, I[2]=0, I[1]=0, I[0]=0
 - Output defined as register to store value
 - "always" procedure sensitive to positive (rising) edge of clock
 - Sets output Q to input I

```
module Reg4(I, Q, clk);
  input [3:0] I;
  input clk;
  output [3:0] Q;
  reg [3:0] Q;

  always @(posedge clk)
  begin
    Q <= I;
  end
endmodule
```



Describing a 4-bit Register in SystemC

- Module
 - 4 data inputs, 4 data outputs, and a clock input
 - Define data inputs/outputs as vectors
 - `sc_in<sc_lv<4>> I;`
 - `I<="1000"` assigns `I[3]=1, I[2]=0, I[1]=0, I[0]=0`
 - Constructor calls `seq_logic` method, sensitive to positive (rising) edge of clock
 - `seq_logic` writes output Q with input I
 - Output port is signal, and signal has storage, thus output retains value

```
#include "systemc.h"

SC_MODULE(Reg4)
{
    sc_in<sc_lv<4>> I;
    sc_out<sc_lv<4>> Q;
    sc_in<sc_logic> clk;

    SC_CTOR(Reg4)
    {
        SC_METHOD(seq_logic);
        sensitive_pos << clk;
    }

    void seq_logic()
    {
        Q.write(I.read());
    }
};
```



Describing an Oscillator in VHDL

- Entity
 - Defines clock output
- Architecture
 - Process
 - Has no sensitivity list, so executes non-stop as infinite loop
 - Sets clock to 0, waits 10 ns, sets clock to 1, waits 10 ns, repeats

```
library ieee;
use ieee.std_logic_1164.all;

entity Osc is
    port ( clk: out std_logic );
end Osc;

architecture behavior of Osc is
begin
    process
    begin
        clk <= '0';
        wait for 10 ns;
        clk <= '1';
        wait for 10 ns;
    end process;
end behavior;
```



Describing an Oscillator in Verilog

- Module
 - Has one output, clk
 - Declare as "reg" to hold value
 - "always" procedure
 - Has no sensitivity list, so executes non-stop as infinite loop
 - Sets clock to 0, waits for 10 ns, sets clock to 1, waits for 10 ns, repeats

```
module Osc(clk);
  output clk;
  reg clk;

  always
  begin
    clk <= 0;
    #10;
    clk <= 1;
    #10;
  end
endmodule
```



Describing an Oscillator in SystemC

- Module
 - Has one output, clk
 - Constructor creates single thread
 - Thread consists of infinite loop
 - while (true) {
 - Sets clock to 0, waits 10 ns, sets clock to 1, waits 10 ns, repeats

```
#include "systemc.h"


SC_MODULE(Osc)
{
  sc_out<sc_logic> clk;

  SC_CTOR(Osc)
  {
    SC_THREAD(seq_logic);
  }

  void seq_logic()
  {
    while(true) {
      clk.write(SC_LOGIC_0);
      wait(10, SC_NS);
      clk.write(SC_LOGIC_1);
      wait(10, SC_NS);
    }
  }
};
```



Describing a Controller in VHDL

 

- FSM behavior captured using architecture with 2 processes
 - First process models state register
 - Asynchronous reset sets state to "S_Off"
 - Rising clock edge sets currentstate to nextstate
 - Second process models combinational logic
 - Sensitive to currentstate and FSM inputs
 - Sets FSM outputs based on currentstate
 - Sets nextstate based on currentstate and present FSM input values
 - Note declaration of new type, statetype



Digital Design
Copyright © 2006
Frank Vahid

```

library ieee;
use ieee.std_logic_1164.all


entity LaserTimer is
port (b: in std_logic;
      x: out std_logic;
      clk, rst: in std_logic
);
end LaserTimer;

architecture behavior of LaserTimer is
type statetype is
(S_Off, S_On1, S_On2, S_On3);
signal currentstate, nextstate:
statetype;
begin
statereg: process (clk, rst)
begin
if (rst='1') then -- initial state
currentstate <= S_Off;
elsif (clk='1' and clk'event) then
currentstate <= nextstate;
end if;
end process;

comblogic: process (currentstate, b)
begin
case currentstate is
when S_Off =>
x <= '0'; -- laser off
if (b='0') then
nextstate <= S_Off;
else
nextstate <= S_On1;
end if;
when S_On1 =>
x <= '1'; -- laser on
nextstate <= S_On2;
when S_On2 =>
x <= '1'; -- laser still on
nextstate <= S_On3;
when S_On3 =>
x <= '1'; -- laser still on
nextstate <= S_Off;
end case;
end process;
end behavior;
    
```

27

Describing a Controller in Verilog

 

- FSM behavior captured using 2 "always" procedures
 - First procedure models state register
 - Asynchronous reset sets state to "S_Off"
 - Rising clock edge sets currentstate to nextstate
 - Second process models combinational logic
 - Sensitive to currentstate and FSM inputs
 - Sets FSM outputs based on currentstate
 - Sets nextstate based on currentstate and present FSM input values
 - Note state register size must be explicit – 2 bits, reg [1:0] currentstate



Digital Design
Copyright © 2006
Frank Vahid

```


module LaserTimer(b, x, clk, rst);
input b, clk, rst;
output x;
reg x;

parameter S_Off = 2'b00,
          S_On1 = 2'b01,
          S_On2 = 2'b10,
          S_On3 = 2'b11;

reg [1:0] currentstate;
reg [1:0] nextstate;
// state register procedure
always @(posedge rst or posedge clk)
begin
if (rst==1) // initial state
currentstate <= S_Off;
else
currentstate <= nextstate;
end
// combinational logic procedure
always @(currentstate or b)
begin
case (currentstate)
S_Off: begin
x <= 0; // laser off
if (b=0)
nextstate <= S_Off;
else
nextstate <= S_On1;
end
S_On1: begin
x <= 1; // laser on
nextstate <= S_On2;
end
S_On2: begin
x <= 1; // laser still on
nextstate <= S_On3;
end
S_On3: begin
x <= 1; // laser still on
nextstate <= S_Off;
end
endcase
end
endmodule
    
```

28

Describing a Controller in SystemC

 

- FSM behavior captured using 2 methods
 - First method models state register
 - Asynchronous reset sets state to "S_Off"
 - Rising clock edge sets currentstate to nextstate
 - Second process models combinational logic
 - Sensitive to currentstate and FSM inputs
 - Sets FSM outputs based on currentstate
 - Sets nextstate based on currentstate and present FSM input values
 - Note use of new type, statetype

```
#include "systemc.h"
enum statetype { S_Off, S_On1, S_On2, S_On3 };
SC_MODULE(LaserTimer)
{
    sc_in<sc_logic> b, clk, rst;
    sc_out<sc_logic> x;
    sc_signal<statetype> currentstate, nextstate;

    SC_CTOR(LaserTimer) {
        SC_METHOD(statereg);
        sensitive_pos << rst << clk;
        SC_METHOD(comblogic);
        sensitive << currentstate << b;
    }

    void statereg() {
        if (rst.read() == SC_LOGIC_1)
            currentstate = S_Off; // initial state
        else
            currentstate = nextstate;
    }

    void comblogic() {
        switch (currentstate) {
            case S_Off:
                x.write(SC_LOGIC_0); // laser off
                if (b.read() == SC_LOGIC_0)
                    nextstate = S_Off;
                else
                    nextstate = S_On1;
                break;
            case S_On1:
                x.write(SC_LOGIC_1); // laser on
                nextstate = S_On2;
                break;
            case S_On2:
                x.write(SC_LOGIC_1); // laser still on
                nextstate = S_On3;
                break;
            case S_On3:
                x.write(SC_LOGIC_1); // laser still on
                nextstate = S_Off;
                break;
        }
    }
};
```



Digital Design
Copyright © 2006
Frank Vahid

Datapath Component Description using Hardware Description Languages

9.4

- Will consider description of three datapath components
 - Full-adders
 - Carry-ripple adders
 - Up-counter



Digital Design
Copyright © 2006
Frank Vahid


30

Describing a Full-Adder in VHDL

- Entity
 - Declares inputs/outputs
- Architecture
 - Described behaviorally (could have been described structurally)
 - Process sensitive to inputs
 - Computes expressions, sets outputs

$$s = a \text{ xor } b \text{ xor } ci$$

$$co = bc + ac + ab$$

 

```

library ieee;
use ieee.std_logic_1164.all;

entity FullAdder is
    port ( a, b, ci: in std_logic;
          s, co: out std_logic
        );
end FullAdder;

architecture behavior of FullAdder is
begin
    process (a, b, ci)
    begin
        s <= a xor b xor ci;
        co <= (b and ci) or (a and ci) or (a and b);
    end process;
end behavior;
    
```



Digital Design
Copyright © 2006
Frank Vahid


31

Describing a Full-Adder in Verilog

- Module
 - Declares inputs/outputs
 - Described behaviorally (could have been described structurally)
 - "always" procedure
 - Sensitive to inputs
 - Computes expressions, sets outputs

$$s = a \text{ xor } b \text{ xor } ci$$

$$co = bc + ac + ab$$

 

```

module FullAdder(a, b, ci, s, co);
    input a, b, ci;
    output s, co;
    reg s, co;

    always @(a or b or ci)
    begin
        s <= a ^ b ^ ci;
        co <= (b & ci) | (a & ci) | (a & b);
    end
endmodule
    
```



Digital Design
Copyright © 2006
Frank Vahid


32

Describing a Full-Adder in SystemC

- Module
 - Declares inputs/outputs
 - Described behaviorally (could have been described structurally)
 - comblogic method
 - Computes expressions, sets outputs

$$s = a \text{ xor } b \text{ xor } ci$$

$$co = bc + ac + ab$$

 

```
#include "systemc.h"
SC_MODULE(FullAdder)
{
    sc_in<sc_logic> a, b, ci;
    sc_out<sc_logic> s, co;

    SC_CTOR(FullAdder)
    {
        SC_METHOD(comblogic);
        sensitive << a << b << ci;
    }

    void comblogic()
    {
        s.write(a.read() ^ b.read() ^ ci.read());
        co.write((b.read() & ci.read()) |
                (a.read() & ci.read()) |
                (a.read() & b.read()));
    }
};
```




Digital Design
Copyright © 2006
Frank Vahid

33

Describing a Carry-Ripple Adder in VHDL

 - Entity
 - Declares inputs/outputs
 - Uses std_logic_vector for 4-bit inputs/outputs
- Architecture
 - Described structurally by composing four full-adders (could have been described behaviorally instead)
 - Declares full-adder component, instantiates four full-adders, connects
 - Note use of three internal signal names for connecting carry-out of one stage to carry-in of next stage



```
library ieee;
use ieee.std_logic_1164.all;

entity CarryRippleAdder4 is
    port ( a : in std_logic_vector(3 downto 0);
          b : in std_logic_vector(3 downto 0);
          ci : in std_logic;
          s : out std_logic_vector(3 downto 0);
          co : out std_logic
    );
end CarryRippleAdder4;

architecture structure of CarryRippleAdder4 is
    component FullAdder
        port ( a, b, ci : in std_logic;
              s, co : out std_logic
        );
    end component;
    signal co1, co2, co3 : std_logic;
begin
    FullAdder1: FullAdder
        port map (a(0), b(0), ci, s(0), co1);
    FullAdder2: FullAdder
        port map (a(1), b(1), co1, s(1), co2);
    FullAdder3: FullAdder
        port map (a(2), b(2), co2, s(2), co3);
    FullAdder4: FullAdder
        port map (a(3), b(3), co3, s(3), co);
end structure;
```




Digital Design
Copyright © 2006
Frank Vahid

34

Describing a Carry-Ripple Adder in Verilog

 - Module
 - Declares inputs/outputs
 - Uses vectors for 4-bit inputs/outputs
 - Described structurally by composing four full-adders (could have been described behaviorally instead)
 - Instantiates four full-adders, connects
 - Note use of three internal wires for connecting carry-out of one stage to carry-in of next stage



```

module CarryRippleAdder4(a, b, ci, s, co);
    input [3:0] a;
    input [3:0] b;
    input ci;
    output [3:0] s;
    output co;

    wire co1, co2, co3;

    FullAdder FullAdder1(a[0], b[0], ci,
                        s[0], co1);
    FullAdder FullAdder2(a[1], b[1], co1,
                        s[1], co2);
    FullAdder FullAdder3(a[2], b[2], co2,
                        s[2], co3);
    FullAdder FullAdder4(a[3], b[3], co3,
                        s[3], co);
endmodule
    
```



Digital Design
Copyright © 2006
Frank Vahid

35

Describing a Carry-Ripple Adder in SystemC

- Module
 - Declares inputs/outputs
 - Uses vectors for 4-bit inputs/outputs
 - Described structurally by composing four full-adders (could have been described behaviorally instead)
 - Instantiates four full-adders, connects
 - Note use of three internal wires for connecting carry-out of one stage to carry-in of next stage

```

#include "systemc.h"
#include "fulladder.h"

SC_MODULE(CarryRippleAdder4)
{
    sc_in<sc_logic> a[4];
    sc_in<sc_logic> b[4];
    sc_in<sc_logic> ci;
    sc_out<sc_logic> s[4];
    sc_out<sc_logic> co;

    sc_signal<sc_logic> co1, co2, co3;

    FullAdder FullAdder_1;
    FullAdder FullAdder_2;
    FullAdder FullAdder_3;
    FullAdder FullAdder_4;

    SC_CTOR(CarryRipple4):
    {
        FullAdder_1("FullAdder_1"),
        FullAdder_2("FullAdder_2"),
        FullAdder_3("FullAdder_3"),
        FullAdder_4("FullAdder_4")
    {
        FullAdder_1.a(a[0]); FullAdder_1.b(b[0]);
        FullAdder_1.ci(ci); FullAdder_1.s(s[0]);
        FullAdder_1.co(co1);

        FullAdder_2.a(a[1]); FullAdder_2.b(b[1]);
        FullAdder_2.ci(co1); FullAdder_2.s(s[1]);
        FullAdder_2.co(co2);

        FullAdder_3.a(a[2]); FullAdder_3.b(b[2]);
        FullAdder_3.ci(co2); FullAdder_3.s(s[2]);
        FullAdder_3.co(co3);


        FullAdder_4.a(a[3]); FullAdder_4.b(b[3]);
        FullAdder_4.ci(co3); FullAdder_4.s(s[3]);
        FullAdder_4.co(co);
    }
};
    
```



Digital Design
Copyright © 2006
Frank Vahid

36

Describing an Up-Counter in VHDL

 

- Described structurally (could have been described behaviorally)
- Includes process that updates output port C whenever internal signal tempC changes
 - Need tempC signal because can't read C due to C being an output port

```

library ieee;
use ieee.std_logic_1164.all;

entity UpCounter is
    port ( clk: in std_logic;
          cnt: in std_logic;
          C: out std_logic_vector(3 downto 0);
          tc: out std_logic
    );
end UpCounter;

architecture structure of UpCounter is
    component Reg4
        port ( I: in std_logic_vector(3 downto 0);
              Q: out std_logic_vector(3 downto 0);
              clk, ld: in std_logic
        );
    end component;
    component Inc4
        port ( a: in std_logic_vector(3 downto 0);
              s: out std_logic_vector(3 downto 0)
        );
    end component;
    component AND4
        port ( w,x,y,z: in std_logic;
              F: out std_logic
        );
    end component;
    signal tempC: std_logic_vector(3 downto 0);
    signal incC: std_logic_vector(3 downto 0);
begin
    Reg4_1: Reg4 port map(incC, tempC, clk, cnt);
    Inc4_1: Inc4 port map(tempC, incC);
    AND4_1: AND4 port map(tempC(3), tempC(2),
                          tempC(1), tempC(0), tc);


    outputC: process(tempC)
    begin
        C <= tempC;
    end process;
end structure;
    
```



Digital Design
Copyright © 2006
Frank Vahid

37

Describing an Up-Counter in Verilog

 

- Described structurally (could have been described behaviorally)
- Includes always procedure that updates output C whenever internal wire tempC changes
 - Need tempC wire because can't use C in the connection statements

```

module Reg4(I, Q, clk, ld);
    input [3:0] I;
    input clk, ld;
    output [3:0] Q;
    // details not shown
endmodule

module Inc4(a, s);
    input [3:0] a;
    output [3:0] s;
    // details not shown
endmodule

module AND4(w,x,y,z,F);
    input w, x, y, z;
    output F;
    // details not shown
endmodule

module UpCounter(clk, cnt, C, tc);
    input clk, cnt;
    output [3:0] C;
    reg [3:0] C;
    output tc;

    wire [3:0] tempC;
    wire [3:0] incC;

    Reg4 Reg4_1(incC, tempC, clk, cnt);
    Inc4 Inc4_1(tempC, incC);
    AND4 AND4_1(tempC[3], tempC[2],
                tempC[1], tempC[0], tc);


    always @(tempC)
    begin
        C <= tempC;
    end
endmodule
    
```



Digital Design
Copyright © 2006
Frank Vahid

38

Describing an Up-Counter in SystemC

 

- Described structurally (could have been described behaviorally)
- Includes method that updates output C whenever internal signal tempC changes
 - Need tempC signal because can't use C in the connection statements
- Can't use logic vector bits individually for connections, so needed tempC_b array too



Digital Design
Copyright © 2006
Frank Vahid

```
#include "systemc.h"
#include "reg4.h"
#include "inc4.h"
#include "and4.h"

SC_MODULE(UpCounter)
{
    sc_in<sc_logic> clk, cnt;
    sc_out<sc_lv<4>> C;
    sc_out<sc_logic> tc;

    sc_signal<sc_lv<4>> tempC, incC;
    sc_signal<sc_logic> tempC_b[4];

    Reg4 Reg4_1;
    Inc4 Inc4_1;
    AND4 AND4_1;

    SC_CTOR(UpCounter) : Reg4_1("Reg4_1"),
                        Inc4_1("Inc4_1"),
                        AND4_1("AND4_1")
    {
        Reg4_1.I(incC); Reg4_1.Q(tempC);
        Reg4_1.clk(clk); Reg4_1.ld(cnt);

        Inc4_1.a(tempC); Inc4_1.s(incC);

        AND4_1.w(tempC_b[0]); AND4_1.x(tempC_b[1]);
        AND4_1.y(tempC_b[2]); AND4_1.z(tempC_b[3]);
        AND4_1.F(tc);

        SC_METHOD(comblgic);
        sensitive << tempC;
    }

    void complgic()
    {
        tempC_b[0] = tempC.read()[0];
        tempC_b[1] = tempC.read()[1];
        tempC_b[2] = tempC.read()[2];
        tempC_b[3] = tempC.read()[3];
        C.write(tempC);
    }
};
```

39

RTL Design using Hardware Description Languages

9.5

- Will consider two forms of RTL descriptions
 - High-level state machine
 - Controller and datapath



Digital Design
Copyright © 2006
Frank Vahid

40

High-Level State Machine of the Laser-Based Distance Measurer in VHDL

- Architecture similar to FSM, but single process
- Asynch reset forces to state S0
- For each rising clock
 - Perform state's computation
 - Prepare to go to next state based on state and inputs


```

library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_arith.all;

entity LaserDistMeasurer is
port ( clk, rst: in std_logic;
      B, S: in std_logic;
      L: out std_logic;
      D: out unsigned(15 downto 0)
);
end LaserDistMeasurer;

architecture behavior of LaserDistMeasurer is
type statetype is (S0, S1, S2, S3, S4);
signal state : statetype;
signal Dctr : unsigned(15 downto 0);

constant U_ZERO :
  unsigned(15 downto 0) := "0000000000000000";
constant U_ONE : unsigned(0 downto 0) := "1";
begin
statemachine: process (clk, rst)
begin
if (rst='1') then
L <= '0';
Dctr <= U_ZERO;
state <= S0; -- initial state
elsif (clk='1' and clk'event) then
case state is
when S0 =>
L <= '0'; -- laser off
Dctr <= U_ZERO; -- clear D
state <= S1;
when S1 =>
Dctr <= U_ZERO; -- reset count
if (B='1') then
state <= S2;
else
state <= S1;
end if;
when S2 =>
L <= '1'; -- laser on
state <= S3;
when S3 =>
L <= '0'; -- laser off
Dctr <= Dctr + 1;
if (S='1') then
state <= S4;
else
state <= S3;
end if;
when S4 =>
D <= SHR(Dctr, U_ONE); -- calculate D
state <= S1;
end case;
end if;
end process;
end behavior;
    
```

 

Digital Design
Copyright © 2006
Frank Vahid

High-Level State Machine of the Laser-Based Distance Measurer in Verilog

```


module LaserDistMeasurer(clk, rst, B, S, L, D);
input clk, rst, B, S;
output L;
output [15:0] D;
reg L;
reg [15:0] D;

parameter S0 = 3'b000,
          S1 = 3'b001,
          S2 = 3'b010,
          S3 = 3'b011,
          S4 = 3'b100;

reg [2:0] state;
reg [16:0] Dctr;

always @(posedge rst or posedge clk)
begin
if (rst==1) begin
L <= 0;
D <= 0;
Dctr <= 0;
state <= S0; // initial state
end
else begin
case (state)
S0: begin
L <= 0; // laser off
D <= 0; // clear D
state <= S1;
end
S1: begin
Dctr <= 0; // reset count
if (B==1)
state <= S2;
else
state <= S1;
end
S2: begin
L <= 1; // laser on
state <= S3;
end
S3: begin
L <= 0; // laser off
Dctr <= Dctr + 1;
if (S==1)
state <= S4;
else
state <= S3;
end
S4: begin
D <= Dctr >> 1; // calculate D
state <= S1;
end
endcase
end
endmodule
    
```

(continued in Figure 9.37)

 

Digital Design
Copyright © 2006
Frank Vahid

High-Level State Machine of the Laser-Based Distance Measurer in SystemC


- Module similar to FSM, but single method
- Asynch reset forces to state S0
- For each rising clock
 - Perform state's computation
 - Prepare to go to next state based on state and inputs

```
#include "systemc.h"
enum statetype { S0, S1, S2, S3, S4 };
SC_MODULE(LaserDistMeasurer)
{
    sc_in<sc_logic> clk, rst;
    sc_in<sc_logic> B, S;
    sc_out<sc_logic> L;
    sc_out<sc_lv<16>> D;

    sc_signal<statetype> state;
    sc_signal<sc_uint<16>> Dctr;

    SC_CTOR(LaserDistMeasurer)
    {
        SC_METHOD(statemachine);
        sensitive_pos << rst << clk;
    }


    void statemachine()
    {
        if (rst.read() == SC_LOGIC_1) {
            L.write(SC_LOGIC_0);
            D.write(0);
            Dctr = 0;
            state = S0; // initial state
        }
        else {
            switch (state) {
                case S0:
                    L.write(SC_LOGIC_0); // laser off
                    D.write(0); // clear D
                    state = S1;
                    break;
                case S1:
                    Dctr = 0; // clear count
                    if (B.read() == SC_LOGIC_1)
                        state = S2;
                    break;
                case S2:
                    L.write(SC_LOGIC_1); // laser on
                    Dctr = Dctr.read() + 1;
                    if (S.read() == SC_LOGIC_1)
                        state = S3;
                    else
                        state = S1;
                    break;
                case S3:
                    L.write(SC_LOGIC_0); // laser off
                    Dctr = Dctr.read() + 1;
                    if (S.read() == SC_LOGIC_1)
                        state = S4;
                    else
                        state = S3;
                    break;
                case S4:
                    D.write(Dctr.read() >> 1); // Calculate D
                    state = S1;
                    break;
            }
        }
    }
};
```

 

Digital Design
Copyright © 2006
Frank Vahid

Controller and Datpath of the Laser-Based Distance Measurer in VHDL

 - At highest level, just connection of controller and datapath components





```
library ieee;
use ieee.std_logic_1164.all;

entity LaserDistMeasurer is
    port ( clk, rst: in std_logic;
          B, S: in std_logic;
          L: out std_logic;
          D: out std_logic_vector(15 downto 0)
    );
end LaserDistMeasurer;

architecture structure of LaserDistMeasurer is
    component LDM_Controller
        port ( clk, rst: in std_logic;
              B, S: in std_logic;
              L: out std_logic;
              Dreg_clr, Dreg_ld: out std_logic;
              Dctr_clr, Dctr_cnt: out std_logic
        );
    end component;
    component LDM_Datpath
        port ( clk: in std_logic;
              Dreg_clr, Dreg_ld: in std_logic;
              Dctr_clr, Dctr_cnt: in std_logic;
              D: out std_logic_vector(15 downto 0)
        );
    end component;
    signal Dreg_clr, Dreg_ld: std_logic;
    signal Dctr_clr, Dctr_cnt: std_logic;
begin
    LDM_Controller_1: LDM_Controller
        port map (clk, rst, B, S, L,
                 Dreg_clr, Dreg_ld, Dctr_clr,
                 Dctr_cnt);
    LDM_Datpath_1: LDM_Datpath
        port map (clk, Dreg_clr, Dreg_ld,
                 Dctr_clr, Dctr_cnt, D);
end structure;
```

Digital Design
Copyright © 2006
Frank Vahid

  Datapath of the Laser-Based Distance Measurer in VHDL



- Datapath just another connection of components
 - Assume up-counter, register, and shift-right components are already designed (similar to earlier-designed items)


```

library ieee;
use ieee.std_logic_1164.all;

entity LDM_Datapath is
    port ( clk: in std_logic;
          Dreg_clr, Dreg_ld: in std_logic;
          Dctr_clr, Dctr_cnt: in std_logic;
          D: out std_logic_vector(15 downto 0)
    );
end LDM_Datapath;

architecture structure of LDM_Datapath is
    component UpCounter16
        port ( clk: in std_logic;
              clr, cnt: in std_logic;
              C: out std_logic_vector(15 downto 0)
        );
    end component;
    component Reg16
        port ( I: in std_logic_vector(15 downto 0);
              Q: out std_logic_vector(15 downto 0);
              clk, clr, ld: in std_logic
        );
    end component;
    component ShiftRightOne16
        port ( I: in std_logic_vector(15 downto 0);
              S: out std_logic_vector(15 downto 0)
        );
    end component;
    signal tempC: std_logic_vector(15 downto 0);
    signal shiftC: std_logic_vector(15 downto 0);
begin
    Dctr: UpCounter16
        port map ( clk, Dctr_clr, Dctr_cnt, tempC);
    ShiftRight: ShiftRightOne16
        port map ( tempC, shiftC);
    Dreg: Reg16
        port map ( shiftC, D, clk, Dreg_clr, Dreg_ld);
end structure;
    
```

 Controller of the Laser-Based Distance Measurer in VHDL



- FSM similar to high-level state machine
 - But high-level operations replaced by low-level datapath signals
 - Use two-process FSM description approach

```

(continued from Figure 9.42)
when S2 =>
    L <= '1'; -- laser on
    nextstate <= S3;
when S3 =>
    L <= '0'; -- laser off
    Dctr_cnt <= '1'; -- count up
    if (S='1') then
        nextstate <= S4;
    else
        nextstate <= S3;
    end if;
when S4 =>
    Dreg_ld <= '1'; -- load Dreg
    Dctr_cnt <= '0'; -- stop counting
    nextstate <= S1;
end case;
end process;
end behavior;
    
```

```

library ieee;
use ieee.std_logic_1164.all;


entity LDM_Controller is
    port ( clk, rst: in std_logic;
          B, S: in std_logic;
          L: out std_logic;
          Dreg_clr, Dreg_ld: out std_logic;
          Dctr_clr, Dctr_cnt: out std_logic
    );
end LDM_Controller;

architecture behavior of LDM_Controller is
    type statetype is (S0, S1, S2, S3, S4);
    signal currentstate, nextstate: statetype;
begin
    statereg: process (clk, rst)
    begin
        if (rst='1') then
            currentstate <= S0; -- initial state
        elsif (clk='1' and clk'event) then
            currentstate <= nextstate;
        end if;
    end process;

    comblogic: process (currentstate, B, S)
    begin
        L <= '0';
        Dreg_clr <= '0';
        Dreg_ld <= '0';
        Dctr_clr <= '0';
        Dctr_cnt <= '0';
        case currentstate is
            when S0 =>
                L <= '0'; -- laser off
                Dreg_clr <= '1'; -- clear Dreg
                nextstate <= S1;
            when S1 =>
                Dctr_clr <= '1' -- clear count
                if (B='1') then
                    nextstate <= S2;
                else
                    nextstate <= S1;
                end if;
            when S2 =>
                L <= '1'; -- laser on
                nextstate <= S3;
            when S3 =>
                Dctr_cnt <= '1'; -- count up
                if (S='1') then
                    nextstate <= S4;
                else
                    nextstate <= S3;
                end if;
            when S4 =>
                Dreg_ld <= '1'; -- load Dreg
                Dctr_cnt <= '0'; -- stop counting
                nextstate <= S1;
            when S0 to S4 =>
                nextstate <= currentstate;
        end case;
    end process;
end behavior;
(continued in Figure 9.43)
    
```

Controller and Datapath of the Laser-Based Distance Measurer in Verilog

 - At highest level, just connection of controller and datapath components



```

module LaserDistMeasurer(clk, rst, B, S, L, D);
    input clk, rst, B, S;
    output L;
    output [15:0] D;

    wire Dreg_clr, Dreg_ld;
    wire Dctr_clr, Dctr_cnt;

    LDM_Controller
        LDM_Controller_1(clk, rst, B, S, L,
            Dreg_clr, Dreg_ld,
            Dctr_clr, Dctr_cnt);



    LDM_Datapath
        LDM_Datapath_1(clk, Dreg_clr, Dreg_ld,
            Dctr_clr, Dctr_cnt, D);
endmodule
    
```



Digital Design
Copyright © 2006
Frank Vahid

47

  Datapath of the Laser-Based Distance Measurer in Verilog



- Datapath just another connection of components
 - Assume up-counter, register, and shift-right components are already designed (similar to earlier-designed items)

```

module UpCounter16(clk, clr, cnt, C);
    input clk, clr, cnt;
    output [15:0] C;
    // details not shown
endmodule

module Reg16(I, Q, clk, clr, ld);
    input [15:0] I;
    input clk, clr, ld;
    output [15:0] Q;
    // details not shown
endmodule

module ShiftRightOne16(I, S);
    input [15:0] I;
    output [15:0] S;
    // details not shown
endmodule

module LDM_Datapath(clk, Dreg_clr, Dreg_ld,
    Dctr_clr, Dctr_cnt, D);
    input clk;
    input Dreg_clr, Dreg_ld;
    input Dctr_clr, Dctr_cnt;
    output [15:0] D;

    wire [15:0] tempC, shiftC;


    UpCounter16 Dctr(clk, Dctr_clr, Dctr_cnt,
        tempC);
    ShiftRightOne16 ShiftRight(tempC, shiftC);
    Reg16 Dreg(shiftC, D, clk, Dreg_clr, Dreg_ld);
endmodule
    
```



Digital Design
Copyright © 2006
Frank Vahid

48

 Controller of the Laser-Based Distance Measurer in Verilog



- FSM similar to high-level state machine
 - But high-level operations replaced by low-level datapath signals
 - Use two-procedure FSM description approach

```
(continued from Figure 9.46)
S1: begin
    Dctr_clr <= 1; // clear count
    if (B=1)
        nextstate <= S2;
    else
        nextstate <= S1;
end
S2: begin
    L <= 1; // laser on
    nextstate <= S3;
end
S3: begin
    L <= 0; // laser off
    Dctr_cnt <= 1; // count up
    if (S=1)
        nextstate <= S4;
    else
        nextstate <= S3;
end
S4: begin
    Dreg_ld <= 1; // load Dreg
    Dctr_cnt <= 0; // stop counting
    nextstate <= S1;
end
endcase
end
endmodule
```

```
module LDM_Controller(clk, rst, B, S, L, Dreg_clk,
                    Dreg_ld, Dctr_clr,
                    Dctr_cnt);
    input clk, rst, B, S;
    output L;
    output Dreg_clk, Dreg_ld;
    output Dctr_clr, Dctr_cnt;
    reg L;
    reg Dreg_clr, Dreg_ld;
    reg Dctr_clr, Dctr_cnt;

    parameter S0 = 3'b000,
              S1 = 3'b001,
              S2 = 3'b010,
              S3 = 3'b011,
              S4 = 3'b100;

    reg [2:0] currentstate;
    reg [2:0] nextstate;

    always @(posedge rst or posedge clk)
    begin
        if (rst==1)
            currentstate <= S0; // initial state
        else
            currentstate <= nextstate;
        end


    always @(currentstate or B or S)
    begin
        L <= 0;
        Dreg_clr <= 0;
        Dreg_ld <= 0;
        Dctr_clr <= 0;
        Dctr_cnt <= 0;
        case (currentstate)
            S0: begin
                L <= 0; // laser off
                Dreg_clr <= 1; // clear Dreg
                nextstate <= S1;
            end
        endcase
    end
end
```



Digital Design
Copyright © 2006
Frank Vahid

Controller and Datpath of the Laser-Based Distance Measurer in SystemC

 - At highest level, just connection of controller and datapath components



```
#include "systemc.h"
#include "LDM_Controller.h"
#include "LDM_Datpath.h"

SC_MODULE(LaserDistMeasurer)
{
    sc_in<sc_logic> clk, rst;
    sc_in<sc_logic> B, S;
    sc_out<sc_logic> L;
    sc_out<sc_lv<16>> D;

    sc_signal<sc_logic> Dreg_clr, Dreg_ld;
    sc_signal<sc_logic> Dctr_clr, Dctr_cnt;

    LDM_Controller LDM_Controller_1;
    LDM_Datpath LDM_Datpath_1;



    SC_CTOR(LaserDistMeasurer) :
    LDM_Controller_1("LDM_Controller_1"),
    LDM_Datpath_1("LDM_Datpath_1")
    {
        LDM_Controller_1.clk(clk);
        LDM_Controller_1.rst(rst);
        LDM_Controller_1.B(B);
        LDM_Controller_1.S(S);
        LDM_Controller_1.Dreg_clr(Dreg_clr);
        LDM_Controller_1.Dreg_ld(Dreg_ld);
        LDM_Controller_1.Dctr_clr(Dctr_clr);
        LDM_Controller_1.Dctr_cnt(Dctr_cnt);

        LDM_Datpath_1.clk(clk);
        LDM_Datpath_1.Dreg_clr(Dreg_clr);
        LDM_Datpath_1.Dreg_ld(Dreg_ld);
        LDM_Datpath_1.Dctr_clr(Dctr_clr);
        LDM_Datpath_1.Dctr_cnt(Dctr_cnt);
        LDM_Datpath_1.D(D);
    }
};
```



Digital Design
Copyright © 2006
Frank Vahid

  Datapath of the Laser-Based Distance Measurer in SystemC



- Datapath just another connection of components
 - Assume up-counter, register, and shift-right components are already designed (similar to earlier-designed items)

```
#include "systemc.h"
#include "upcounter16.h"
#include "reg16.h"
#include "shiftrightone16.h"

SC_MODULE(LDM_Datapath)
{
    sc_in<sc_logic> clk;
    sc_in<sc_logic> Dreg_clr, Dreg_ld;
    sc_in<sc_logic> Dctr_clr, Dctr_cnt;
    sc_out<sc_lv<16>> D;

    sc_signal<sc_lv<16>> tempC;
    sc_signal<sc_lv<16>> shiftC;


    UpCounter16 Dctr;
    Reg16 Dreg;
    ShiftRightOne16 ShiftRight;

    SC_CTOR(LDM_Datapath) :
        Dctr("Dctr"), Dreg("Dreg"),
        ShiftRight("ShiftRight")
    {
        Dctr.clk(clk);
        Dctr.clr(Dctr_clr);
        Dctr.cnt(Dctr_cnt);
        Dctr.C(tempC);

        ShiftRight.I(tempC);
        ShiftRight.S(shiftC);

        Dreg.I(shiftC);
        Dreg.Q(D);
        Dreg.clk(clk);
        Dreg.clr(Dreg_clr);
        Dreg.ld(Dreg_ld);
    }
};
```

 Controller of the Laser-Based Distance Measurer in SystemC



- FSM similar to high-level state machine
 - But high-level operations replaced by low-level datapath signals
 - Use two-procedure FSM description approach

```
(continued from Figure 9.50)
case S1:
    Dctr_clr.write(SC_LOGIC_1); // clear count
    if (B.read() == SC_LOGIC_1)
        nextstate = S2;
    else
        nextstate = S1;
    break;
case S2:
    L.write(SC_LOGIC_1); // laser on
    nextstate = S3;
    break;
case S3:
    L.write(SC_LOGIC_0); // laser off
    Dctr_cnt.write(SC_LOGIC_1); // count up
    if (S.read() == SC_LOGIC_1)
        nextstate = S4;
    else
        nextstate = S3;
    break;
case S4:
    Dreg_ld.write(SC_LOGIC_1); // load Dreg
    Dctr_cnt.write(SC_LOGIC_0); // stop counting
    nextstate = S1;
    break;
};
```

```
#include "system.h"
enum statetype { S0, S1, S2, S3, S4 };
SC_MODULE(LDM_Controller)
{
    sc_in<sc_logic> clk, rst, B, S;
    sc_out<sc_logic> L;
    sc_out<sc_logic> Dreg_clr, Dreg_ld;
    sc_out<sc_logic> Dctr_clr, Dctr_cnt;

    sc_signal<statetype> currentstate, nextstate;

    SC_CTOR(LDM_Controller)
    {
        SC_METHOD(statereg);
        sensitive pos << rst << clk;
        SC_METHOD(comblgic);
        sensitive << currentstate << B << S;
    }

    void statereg() {
        if (rst.read() == SC_LOGIC_1)
            currentstate = S0; // initial state
        else
            currentstate = nextstate;
    }

    void comblgic() {
        L.write(SC_LOGIC_0);
        Dreg_clr.write(SC_LOGIC_0);
        Dreg_ld.write(SC_LOGIC_0);
        Dctr_clr.write(SC_LOGIC_0);
        Dctr_cnt.write(SC_LOGIC_0);
    }

    switch (currentstate) {
        case S0:
            L.write(SC_LOGIC_0); // laser off
            Dreg_clr.write(SC_LOGIC_0); // clear Dreg
            nextstate = S1;
            break;
    }
};
```

Chapter Summary

- Hardware Description Languages (HDLs) are widely used in modern digital design
 - Textual rather than graphical language sufficient for many purposes
 - HDLs are computer-readable
 - Great for simulation
- VHDL, Verilog, and SystemC are popular
- Introduced languages mainly through examples
- Numerous HDL books exist to teach each language in more detail

