


# HIERARCHICAL DESIGN

# Outline

1. Introduction
2. Components
3. Generics
4. Configuration
5. Other supporting constructs
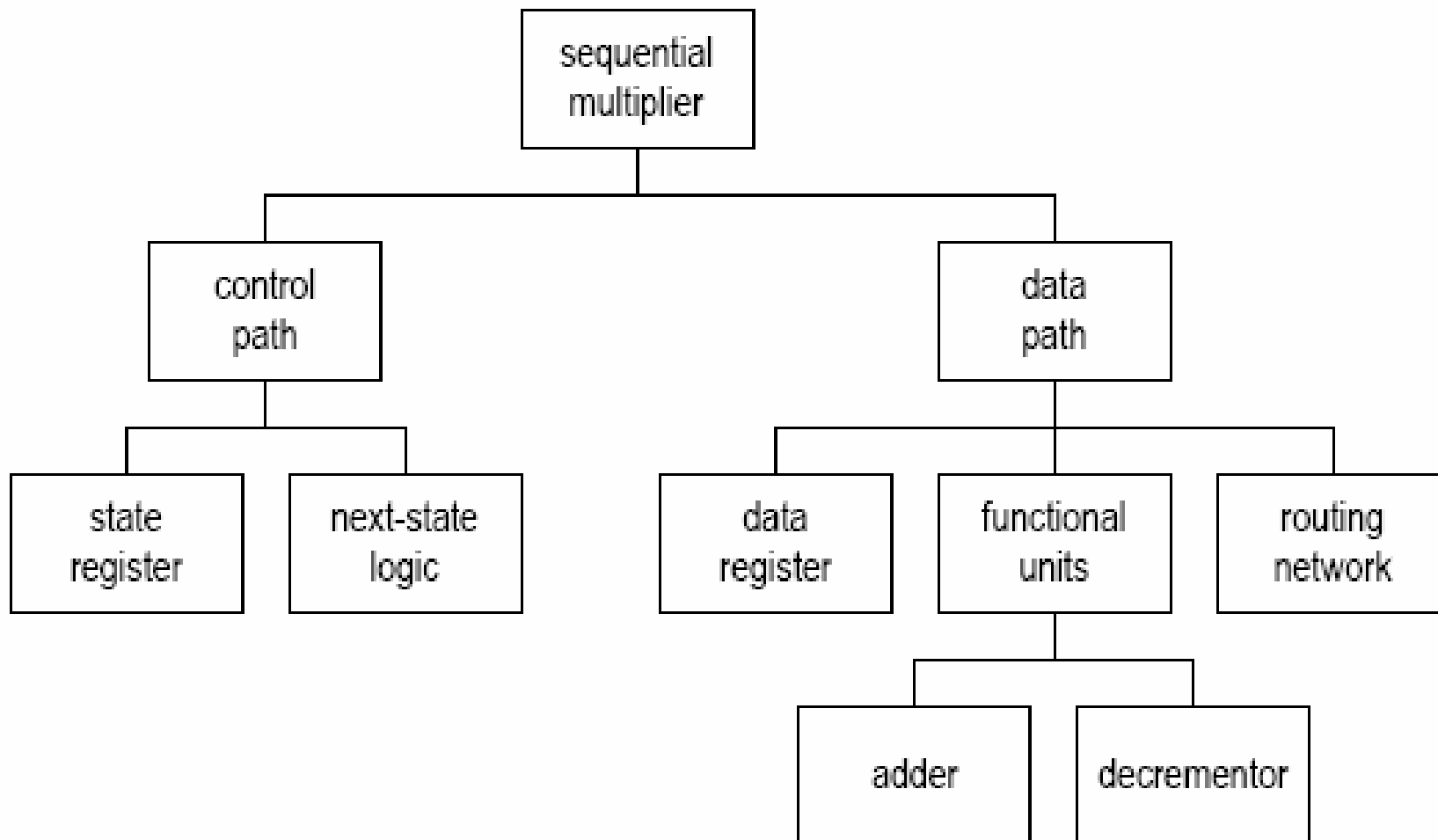
# 1. Introduction

- How to deal with 1M gates or more?
- Hierarchical design
  - Divided-and-conquer strategy
  - Divide a system into smaller parts



# Benefits of hierarchical design

- Complexity management
  - Focus on a manageable portion of the system, and analyze, design and verify each module in isolation.
  - Construct the system in stages by a designer or concurrently by a team of designers.
  - Help synthesis process

- Design reuse

- Use predesigned modules or third-party cores
- Use the same module in different design
- Isolate device-dependent components (e.g., SRAM)

# Relevant VHDL constructs

- Component
- Generic
- Configuration
- Library
- Package
- Subprogram

## 2. Components

- Hierarchical design usually shown as a block diagram (structural description)
- VHDL component is the mechanism to describe structural description in text
- To use a component
  - Component declaration (make known)
  - Component instantiation (create an instance)



# Component declaration

- In the declaration section of entity
- Info similar to entity declaration

- **Syntax:**

```
component component_name
    generic (
        generic_declaration;
        generic_declaration;
        . . .
    );
    port (
        port_declaration;
        port_declaration;
        . . .
    );
end component;
```

- E.g., a decade (mod-10) counter

```
entity dec_counter is
    port (
        clk, reset: in std_logic;
        en: in std_logic;
        q: out std_logic_vector(3 downto 0);
        pulse: out std_logic
    );
end dec_counter;
```


```

architecture up_arch of dec_counter is
    signal r_reg: unsigned(3 downto 0);
    signal r_next: unsigned(3 downto 0);
    constant TEN: integer:= 10;
begin
    -- register
    process (clk, reset)
    begin
        if (reset='1') then
            r_reg <= (others=>'0');
        elsif (clk'event and clk='1') then
            r_reg <= r_next;
        end if;
    end process;
    -- next-state logic
    process (en, r_reg)
    begin
        r_next <= r_reg;
        if (en='1') then
            if r_reg=(TEN-1) then
                r_next <= (others=>'0');
            else
                r_next <= r_reg + 1;
            end if;
        end if;
    end process;
    -- output logic
    q <= std_logic_vector(r_reg);
    pulse <= '1' when r_reg=(TEN-1) else
        '0';
end up_arch;

```

- Component declaration for dec\_counter
 
```
component dec_counter
  port (
    clk, reset: in std_logic;
    en: in std_logic;
    q: out std_logic_vector(3 downto 0);
    pulse: out std_logic
  );
end component;
```



# Component instantiation

- Instantiate an instance of a component
- Provide a generic value
- Map formal signals to actual signals


- **Syntax**

```
instance_label: component_name
  generic map(
    generic_association;
    generic_association;
    . . .
  )
  port map(
    port_association;
    port_association;
    . . .
  );
```

- **Port association (named association)**

```
port_name => signal_name
```

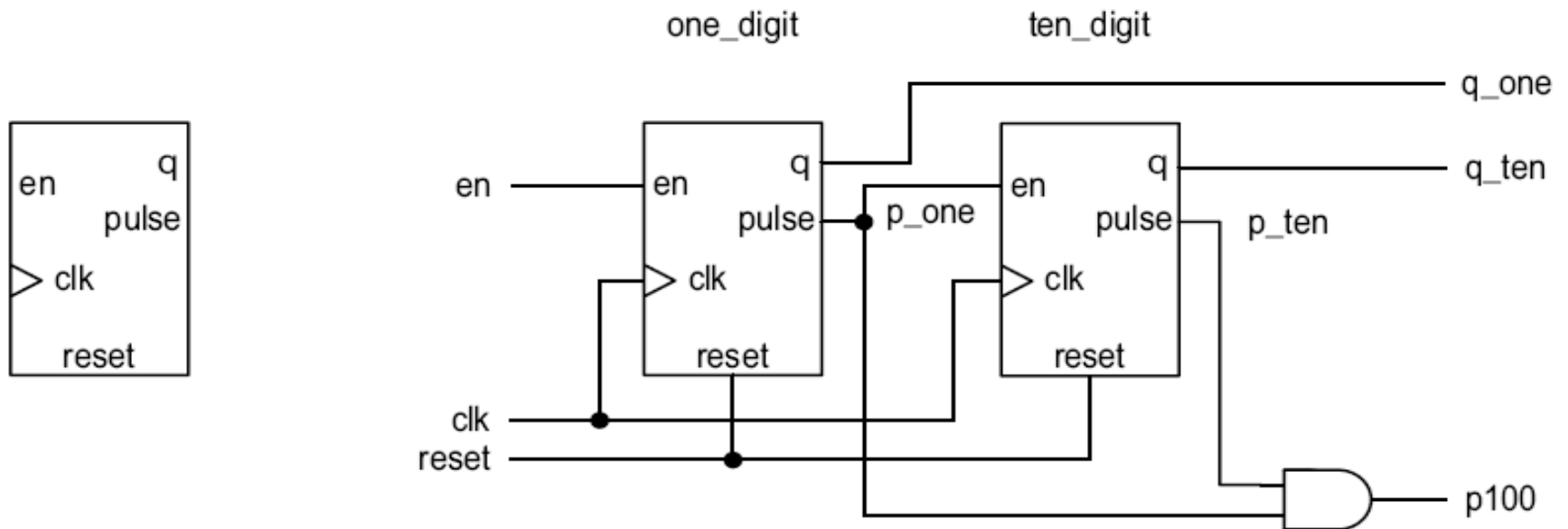- E.g., 2-digit decimal counter  
(00=>01=> . . . =>99 =>00 . . .)



```
library ieee;
use ieee.std_logic_1164.all;
entity hundred_counter is
    port(
        clk, reset: in std_logic;
        en: in std_logic;
        q_ten, q_one: out std_logic_vector(3 downto 0);
        p100: out std_logic
    );
end hundred_counter;
```

```
architecture vhdl_87_arch of hundred_counter is
    component dec_counter
        port(
            clk, reset: in std_logic;
            en: in std_logic;
            q: out std_logic_vector(3 downto 0);
            pulse: out std_logic
        );
    end component;
    signal p_one, p_ten: std_logic;
```



```
begin
  one_digit: dec_counter
    port map (clk=>clk, reset=>reset, en=>en,
              pulse=>p_one, q=>q_one);
  ten_digit: dec_counter
    port map (clk=>clk, reset=>reset, en=>p_one,
              pulse=>p_ten, q=>q_ten);
  p100 <= p_one and p_ten;
end vhdl_87_arch;
```

- The VHDL code is a textual description of a schematic

- Positional association
  - Appeared to be less cumbersome
  - E.g., order of port declaration in entity:


```
clk, reset, en, q, pulse
```

- Alternative component instantiation

```
one_digit: dec_counter
    port map (clk, reset, en, q_one, p_one);
ten_digit: dec_counter
    port map (clk, reset, p_one, q_ten, p_ten);
```

- Trouble if the order later changes in entity declaration

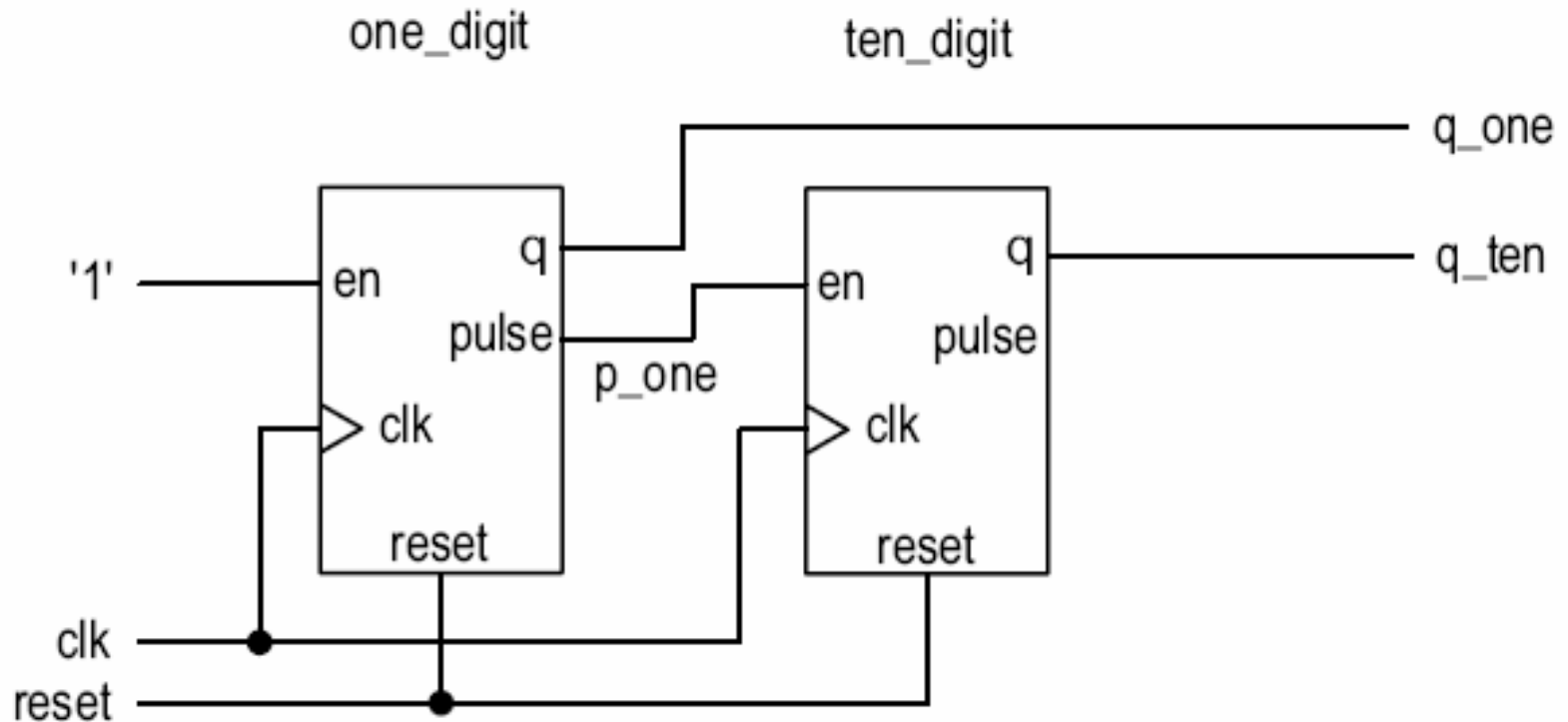- Mapping of constant and unused port
  - E.g.,



```
one_digit: dec_counter
    port map (clk=>clk, reset=>reset, en=>'1',
              pulse=>p_one, q=>q_one);
ten_digit: dec_counter
    port map (clk=>clk, reset=>reset, en=>p_one,
              pulse=>open, q=>q_ten);
```

- Good synthesis software should
  - remove the unneeded part
  - perform optimization over the constant input

# 3. Generics

- Mechanism to pass info into an entity/component
- Declared in entity declaration and then can be used as a constant in port declaration and architecture body
- Assigned a value when the component is instantiated.
- Like a parameter, but has to be constant

- e.g., parameterized binary counter
  - Note that the generic is declared before the port and thus can be used in port declaration

```
entity para_binary_counter is
    generic (WIDTH: natural);
    port (
        clk, reset: in std_logic;
        q: out std_logic_vector(WIDTH-1 downto 0)
    );
end para_binary_counter;
```

```

architecture arch of para_binary_counter is
    signal r_reg, r_next: unsigned(WIDTH-1 downto 0);
begin
    process (clk, reset)
    begin
        if (reset='1') then
            r_reg <= (others=>'0');
        elsif (clk'event and clk='1') then
            r_reg <= r_next;
        end if;
    end process;
    r_next <= r_reg + 1;
    q <= std_logic_vector(r_reg);
end arch;

```

- e.g., to use the parameterized counter

```
library ieee;
use ieee.std_logic_1164.all;
entity generic_demo is
    port (
        clk, reset: in std_logic;
        q_4: out std_logic_vector(3 downto 0);
        q_12: out std_logic_vector(11 downto 0)
    );
end generic_demo;
```



```

architecture vhdl_87_arch of generic_demo is
    component para_binary_counter
        generic (WIDTH: natural);
        port (
            clk, reset: in std_logic;
            q: out std_logic_vector(WIDTH-1 downto 0)
        );
    end component;
begin
    four_bit: para_binary_counter
        generic map (WIDTH=>4)
        port map (clk=>clk, reset=>reset, q=>q_4);
    twe_bit: para_binary_counter
        generic map (WIDTH=>12)
        port map (clk=>clk, reset=>reset, q=>q_12);
end vhdl_87_arch;

```

- e.g., parameterized mod-n counter
  - Count from 0 to n-1 and wrap around
  - Note that WIDTH depends on N


```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;
entity mod_n_counter is
    generic (
        N: natural;
        WIDTH: natural
    );
    port (
        clk, reset: in std_logic;
        en: in std_logic;
        q: out std_logic_vector(WIDTH-1 downto 0);
        pulse: out std_logic
    );
end mod_n_counter;
```

```

architecture arch of mod_n_counter is
    signal r_reg: unsigned(WIDTH-1 downto 0);
    signal r_next: unsigned(WIDTH-1 downto 0);
begin
    -- register
    process (clk, reset)
    begin
        if (reset='1') then
            r_reg <= (others=>'0');
        elsif (clk'event and clk='1') then
            r_reg <= r_next;
        end if;
    end process;
    -- next-state logic
    process (en, r_reg)
    begin
        r_next <= r_reg;
        if (en='1') then
            if r_reg=(N-1) then
                r_next <= (others=>'0');
            else
                r_next <= r_reg + 1;
            end if;
        end if;
    end process;
    -- output logic
    q <= std_logic_vector(r_reg);
    pulse <= '1' when r_reg=(N-1) else
        '0';
end arch;

```

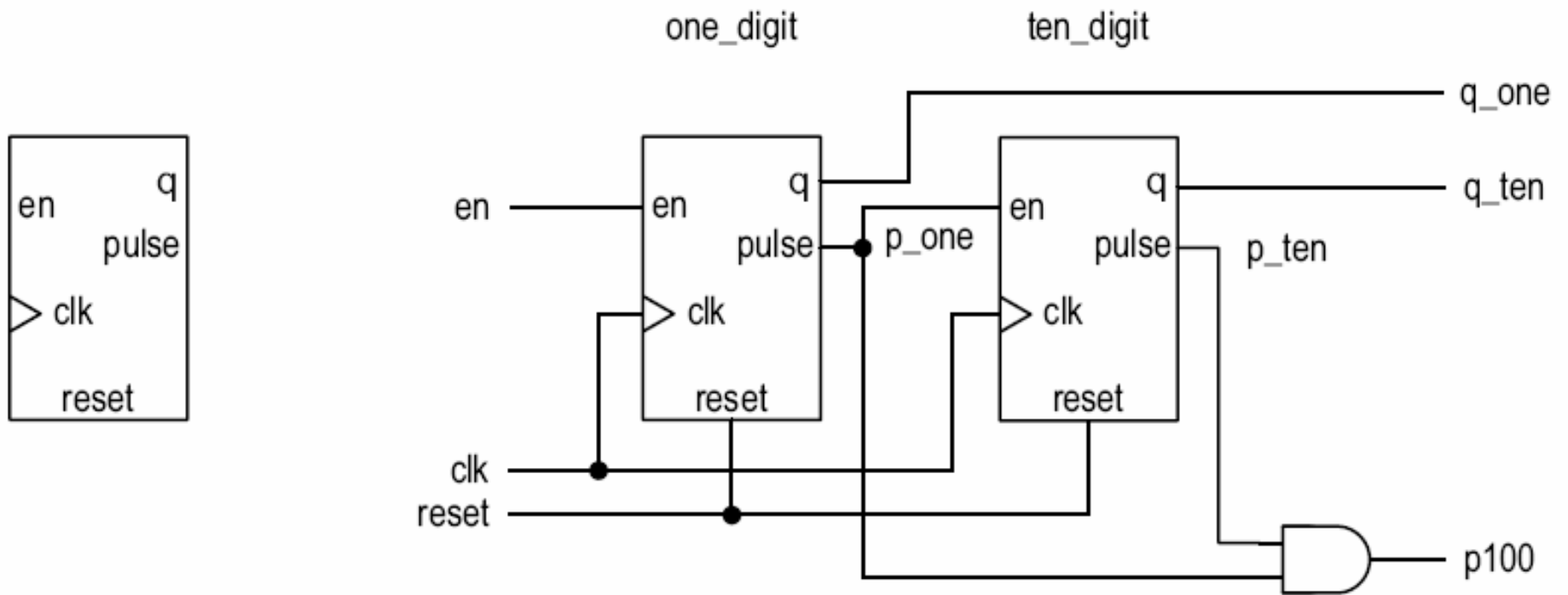- E.g., the 2-digit decimal counter again



```

one_digit: mod_n_counter
    generic map (N=>10, WIDTH=>4)
    port map (clk=>clk, reset=>reset, en=>en,
              pulse=>p_one, q=>q_one);
ten_digit: mod_n_counter
    generic map (N=>10, WIDTH=>4)
    port map (clk=>clk, reset=>reset, en=>p_one,
              pulse=>p_ten, q=>q_ten);
p100 <= p_one and p_ten;

```


- Another useful application of generic: passing delay information

```
y <= a + b after Tpd ns;
```

 
# 4. Configuration

- Bind a component with an entity and an architecture
- Flexible and involved.
- Only simple binding of entity and architecture is needed in synthesis
  - Entity: like a socket in a printed circuit board
  - Architecture: like an IC chip with same outline
- Not supported by all synthesis software

- Application of binding:
  - E.g., adder with different speed:  
Fast but large adder or small but slow adder
  - E.g., Test bench descriptions at different stages





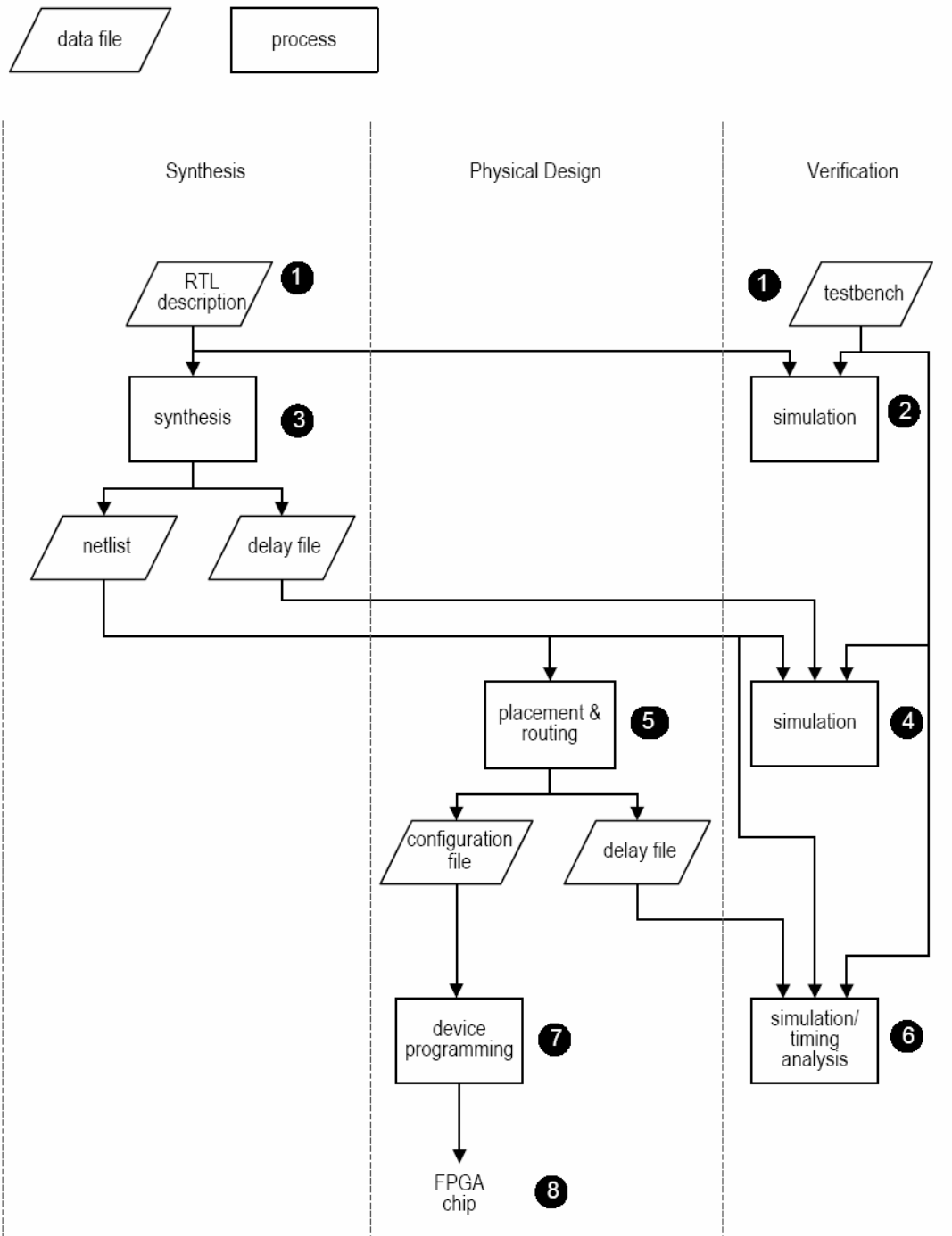

- Type of configuration:
  - Configuration declaration (an independent design unit)
  - Configuration specification (in architecture body)
- Default binding: (no configuration)
  - Component bound to an entity with identical name
  - Component ports bound to entity ports of same names
  - Most recently analyzed architecture body bound to the entity

- Configuration declaration
  - An independent design unit
  - Simplified syntax

```
configuration conf_name of entity_name is
  for architecture_name
    for instance_label: component_name
      use entity lib_name.bound_entity_name(bound_arch_name);
    end for;
    for instance_label: component_name
      use entity lib_name.bound_entity_name(bound_arch_name);
    end for;
    .
    .
    .
  end for;
end;
```

- E.g., create two architecture bodies for the decade counter (one up and one down)

```
architecture down_arch of dec_counter is
-- next-state logic
process(en,r_reg)
begin
    r_next <= r_reg;
    if (en='1') then
        if r_reg=0 then
            r_next <= to_unsigned(TEN-1,4);
        else
            r_next <= r_reg - 1;
        end if;
    end if;
end process;
-- output logic
q <= std_logic_vector(r_reg);
pulse <= '1' when r_reg=0 else
        '0';
```

```

library ieee;
use ieee.std_logic_1164.all;
entity hundred_counter is
    port(
        clk, reset: in std_logic;
        en: in std_logic;
        q_ten, q_one: out std_logic_vector(3 downto 0);
        p100: out std_logic
    );
end hundred_counter;

begin
    one_digit: dec_counter
        port map (clk=>clk, reset=>reset, en=>en,
            pulse=>p_one, q=>q_one);
    ten_digit: dec_counter
        port map (clk=>clk, reset=>reset, en=>p_one,
            pulse=>p_ten, q=>q_ten);
    p100 <= p_one and p_ten;
end vhdl_87_arch;

```

```

configuration count_down_config of hundred_counter is
  for vhdl_87_arch
    for one_digit: dec_counter
      use entity work.dec_counter(down_arch);
5    end for;
    for ten_digit: dec_counter
      use entity work.dec_counter(down_arch);
    end for;
  end for;
) end;

```

- Configuration specification
  - Included in the declaration section of architecture body
- Syntax:

```
for instance_label: component_name
    use entity lib_name.bound_entity_name(bound_arch_name);
for instance_label: component_name
    use entity lib_name.bound_entity_name(bound_arch_name);
```

- E.g.,

```
architecture vhdl_87_config_arch of hundred_counter is
    component dec_counter
        port(
            clk, reset: in std_logic;
            en: in std_logic;
            q: out std_logic_vector(3 downto 0);
            pulse: out std_logic
        );
    end component;
    for one_digit: dec_counter
        use entity work.dec_counter(down_arch);
    for ten_digit: dec_counter
        use entity work.dec_counter(down_arch);
    signal p_one, p_ten: std_logic;
begin
```



- Component instantiation and configuration in VHDL 93
  - Remove component and configuration declaration
  - Usually satisfactory for RT-level synthesis
  - Syntax:

```
instance_label:  
    entity lib_name.bound_entity_name(bound_arch_name)  
        generic map (. . .)  
        port map (. . .);
```

- E.g.,

```
architecture vhdl_93_arch of hundred_counter is
    signal p_one, p_ten: std_logic;
begin
    one_digit: entity work.dec_counter(up_arch)
        port map (clk=>clk, reset=>reset, en=>en,
            pulse=>p_one, q=>q_one);
    ten_digit: entity work.dec_counter(up_arch)
        port map (clk=>clk, reset=>reset, en=>p_one,
            pulse=>p_ten, q=>q_ten);
    p100 <= p_one and p_ten;
end vhdl_93_arch;
```

# 5. Other constructs for developing large system

- Library
- Subprogram
- Package

# Library

- A virtual repository to stored analyzed design units
- Physical location determined by software
- Design units can be organized and stored in different libraries

- Default library: work

- E.g.,

```
one_digit: entity work.dec_counter(up_arch)
```

- Non-default library has to be declared:

- syntax:

```
library lib_name , lib_name , ... , lib_name;
```

- E.g., library ieee;

- E.g.,

```
library c_lib;  -- make c_lib visible
configuration clib_config of hundred_counter is
  for vhdl_87_arch
    for one_digit: dec_counter
      use entity c_lib.dec_counter(down_arch);  -- c_lib
    end for;
    for ten_digit: dec_counter
      use entity c_lib.dec_counter(down_arch);  -- c_lib
    end for;
  end for;
end;
```

# Subprogram

- Include function and procedure
- Made of sequential statement
- Is not a design unit; must be declared
- Aimed for software hierarchy not hardware hierarchy
- We only use function
  - Shorthand for complex expression
  - “House-keeping tasks; e.g., type conversion

- Syntax of function

```
function func_name(parameter_list) return data_type is  
    declarations;  
begin  
    sequential statement;  
    sequential statement;  
    . . .  
    return (expression);  
end;
```



- E.g.,

```
architecture arch of . . .
  -- declaration
  function maj(a, b, c: std_logic) return std_logic is
    variable result: std_logic;
  begin
    result := (a and b) or (a and c) or (b and c);
    return result;
  end maj;
  signal i1, i2, i3, i4, x, y: std_logic;
begin
  . . .

  x <= maj(i1, i2, i3) or i4;
  y <= i1 when maj(i2, i3, i4)='1' else
  . . .
```

- E.g.,

```
function to_boolean(a: std_logic) return boolean is
    variable result: boolean;
begin
    if a='1' then
        result := true;
    else
        result := false;
    end if;
    return result;
end to_boolean;
```

- E.g.,  $\lceil \log_2 n \rceil$

```
function log2c(n: integer) return integer is
    variable m, p: integer;
begin
    m := 0;
    p := 1;
    while p < n loop
        m := m + 1;
        p := p * 2;
    end loop;
    return m;
end log2c;
```

# Package

- Organize and store declaration information, such as data types, functions etc.
- Divided into
  - Package declaration
  - Package body (implementation of subprograms)
- Both are design units

- Syntax

```
package package_name is
    declaration item;
    declaration item;
    . . .
end package_name;
```

```
package body package_name is
    subprogram;
    subprogram;
    . . .
end package_name;
```

- E.g.,

```
-- package declaration
library ieee;
use ieee.std_logic_1164.all;
package util_pkg is
5   type std_logic_2d is
       array(integer range <>, integer range <>) of std_logic;
       function log2c (n: integer) return integer;
end util_pkg ;
```

*--package body*

```
package body util_pkg is  
    function log2c(n: integer) return integer is  
        variable m, p: integer;  
    begin  
        m := 0;  
        p := 1;  
        while p < n loop  
            m := m + 1;  
            p := p * 2;  
        end loop;  
        return m;  
    end log2c;  
end util_pkg;
```

- Improved mod-n counter

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;
use work.util_pkg.all;
entity better_mod_n_counter is
    generic(N: natural);
    port(
        clk, reset: in std_logic;
        en: in std_logic;
        q: out std_logic_vector(log2c(N)-1 downto 0);
        pulse: out std_logic
    );
end better_mod_n_counter;

architecture arch of better_mod_n_counter is
    constant WIDTH: natural := log2c(N);
    signal r_reg: unsigned(WIDTH-1 downto 0);
    signal r_next: unsigned(WIDTH-1 downto 0);
begin
```



# 6. Partition

- Physical partition:
- Division of the physical implementation
- Each subsystem is synthesized independently
- Partition too small: loose optimization opportunity
- Partition too large: require too much resource
  - e.g.,  $O(n^3)$  algorithm 1000 gates for 1 sec;
  - 35 hours ( $50^3$  sec) for one 50,000 gate circuit
  - 21 min ( $10 \cdot 5^3$  sec) for 10 5,000 gate circuit
- 5000 to 50,000 gates for today's synthesizer

- Logical partition:
  - Help development and verification process for human designers
  - Logical partitions can be merged later in synthesis
- Some circuit should be isolated as independent modules
  - Device-dependent circuit: e.g., memory modules
  - “Non-Boolean” circuit: tri-state buffer, delay-sensitive circuit, clock distribution network, synchronization circuit.