 


## Basic Language Concepts: Synthesis

## Synthesis from VHDL Descriptions

```
entity my_ckt is
port(x, y, w :in bit;
      v, z : out bit)
end entity my_ckt;

architecture behavioral of my_ckt is
begin
--
-- some code here
--
end architecture behavioral;
```




- Produce (infer) a correct hardware implementation
  - Note that multiple alternative implementations are feasible
- Synthesis process depends on
  - Hardware primitives
  - Synthesis goals, e.g., area vs. speed
- What are the challenges/issues?

```

library IEEE;
use IEEE.std_logic_1164.all;
entity synth is
port (A, B, C, D: in integer;
      Sel : in std_logic_vector(1 downto 0);
      Z : out integer);
end entity synth;

architecture behavioral of synth is
begin
with Sel select
Z <=  A+B when "00",
      C + D   when "10",
      x"00000000" when others;
end architecture behavioral;

```

 

- We need to infer
  - Bit widths
  - Number of functional units
- What about control?
  - Is there an implied priority order among options?
- What is the baseline against which reconcile options?
  - Language defines the semantics

- Inference from declarations
- Inference from concurrent signal assignment statements
- In all cases, inference is grounded in language semantics
  - For example, the definition of an integer as comprising 32-bits



## Inference from Declarations

---

```
signal result: std_logic_vector (12 downto 0);
signal count: integer;
signal index: integer range 0 to 18;

type state_type is (state0, state1, state2, state3);
signal next_state: state_type;
```

- How are signals implemented?
  - As wires
  - As latches of flip flops
  - Choice depends on how a signal is used
- Inference from data types
  - For simulation, type definition determines a range of values
  - For synthesis, type definition determines bit widths

ECE 4170 (5)



## Inference from Declarations (cont.)

---

- Bit width required for a signal can be determined explicitly or implicitly
  - Programmer defined
  - Via program analysis
- Hints go a long way towards minimizing hardware
- Enumerated types implicitly define the bit width of a signal
- What can you do?

ECE 4170 (6)

## Inference from Simple Concurrent Signal Assignment Statements

- Take a *signal-centric* view
  - Consider signals with a single driver
- Behavior corresponds to that of a combinational circuit
  - When inputs (RHS) change the output is recomputed
  - Model produces one signal assignment statement for every signal in the circuit
- Operator inferencing
  - Operations and corresponding gate types
  - Interconnection between operators
- Delay information is ignored
  - Determined from the library primitives

## Inference from Simple CSAs


```

library IEEE;
use IEEE.std_logic_1164.all;


entity concurrent is
port (s, t, u, w: in std_logic;
      v: out std_logic);
end entity concurrent;

architecture dataflow of concurrent is
signal s1, s2 : std_logic;
begin
L1: s1 <= s and t and u and w;
L2: s2 <= (s and t) and (u and w);
L3: v <= s1 or s2;
end architecture dataflow;
  
```

*Synthesized gate level implementation*

 

*FPGA implementation*

 



Technology mapping

- Operator precedence controls the depth of the circuit
  
## Inference from Simple CSAs (cont.)

```


architecture dataflow of full_adder is
  signal s1, s2, s3: std_ulogic;
begin
  sum <= in1 xor in2 xor c_in;
  c_out <= (in1 and c_in) or (in2 and c_in) or (in1 and in2);
end architecture dataflow;
  
```


 
## Inference from Conditional CSAs


```

architecture behavioral of mux4 is
  begin
  z <=
    in0 when s0 = '0' and s1 = '0' else
    in1 when s0 = '0' and s1 = '1' else
    in2 when s0 = '1' and s1 = '0' else
    in3 when s0 = '1' and s1 = '1' else
    '0';
end architecture behavioral;
  
```




- Any change on input signals causes re-computation of the output signal → combinational logic
- Implied priority order!
  - Priority logic may be optimized for mutually exclusive branches
- Six variable boolean equation and 4 input LUTs
  - Effectively produces a gate level implementation of a multiplexor
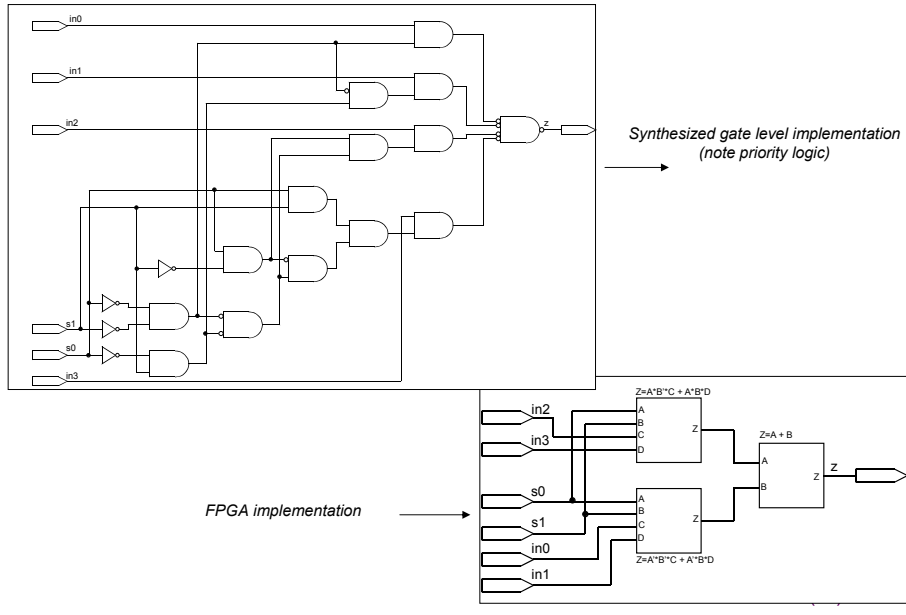
## Inference from Conditional CSAs (cont.)



## Example: Priority Encoder

 

architecture behavior of priority is  
**begin**

**z** <= "00" when datain (0) = '1' and valid = '1' else  
**"10"** when datain (2) = '1' and valid = '1' else  
**"01"** when datain (1) = '1' and valid = '1' else  
**"11"** when datain (3) = '1' and valid = '1' else  
**"00"**;

**end architecture behavior;**

- Note generation of priority logic
- Must be mapped to LUTs

## Synthesis of Comparison Logic

- Comparisons that make sense in a simulation may not be meaningful for synthesis
  - For example, comparisons with don't care symbols are assumed to return false!
- Equality tests for other than 0/1 return false
- Note: consider these implementations when writing synthesizable VHDL code

## Example: Synthesis and Comparison Logic


architecture behavior of priority is  
begin

```

z <= "00" when datain = "--1" and valid = '1' else
"10" when datain = "-100" and valid = '1' else
"01" when datain = "--10" and valid = '1' else
"11" when datain = "1000" and valid = '1' else
"00";
    
```

} These tests (with don't care) always return false


end architecture behavior;

 
 
## Inference from Selected CSAs

- All choices are evaluated and only one must be true
- No priority logic implied
- Example
  - Note how output bits are set
  - Two gate (LUT) implementation

```
with datain select
result <= "00" when "0001",
         "01" when "0010",
         "10" when "0100",
         "11" when "1000",
         "XX" when others;
end architecture behavioral;
```



ECE 4170 (15)

## Inference from Selected CSAs

- The “unaffected” keyword (VHDL’93 only)

```
with datain select
result <= "00" when "0001",
         "01" when "0010",
         "10" when "0100",
         "11" when "1000",
         unaffected when others;
```

- For this value of the select expression the output is unaffected
- The output retains its previous value



A latch is inferred!

ECE 4170 (16)





## Synthesis Hints/Issues Using CSAs

---

- Simulation - synthesis mismatches
  - Delay statements are ignored for synthesis
    - Simulated timing may not match timing of synthesized result
  - Comparison logic
    - Results may differ
- Do not utilize initialization in declarations: use explicit resets
  - Mimic normal hardware design process
- Provide hints in declarations
- Use of the “unaffected” keyword may cause latches to be inferred
- Optimize the “when others” clause: use of don’t care logic

ECE 4170 (17)



## Synthesis Hints/Issues Using CSAs (cont.)

---

- Use parentheses to control circuit depth and therefore speed
- Selected signal assignment vs. conditional signal assignment statements
  - Former causes less logic to be inferred
  - Consider whether order of evaluation matters or not

ECE 4170 (18)

- Declarations can be rich source of information for synthesis
- Language semantics define how one can infer logic for the implementation of each signal assignment statement
  - The inference of priority logic
  - Use of non-synthesizable concepts, e.g., don't care values
- Programming style has a major impact on quality of results
  - Synthesis compilers seek powerful analysis techniques to infer beyond the obvious